

conversion

UNIVERSITY OF CALIFORNIA AT BERKELEY

COLLEGE OF ENGINEERING

DEPARTMENT OF ELECTRICAL ENGINEERING AND COMPUTER SCIENCES

COMPUTER SCIENCE DIVISION


Fall 1996

CS 150 Digital Design

Midterm 1

This is a closed-book, closed-note exam. No calculators. You have 75 minutes to finish the paper.

 1. Given the following FSM circuit diagram:



cycle	f1	f0
0		
1		
2		
3		
4		
5		

Initially both FFs hold logic 0.

(a) [7 points] in the table above, fill in the value of the outputs **f0 f1**.

(b) [3 points] Draw the wave form for **f0** and **f1** below: (draw the clock cycle as a wave of alternating highs and lows)

conversion

CLK


f0

f1

(c) [2 points] Draw the state transition diagram for the above FSM:

(d) [Optional - extra credit, 5 points] convert the above implementation into a "one-hot-encoded" implementation. For this part, add a reset input signal (RST). Don't forget to generate the outputs!


2. [4 points]

 

conversion

For the circuit shown, assume that the register setup time requirement is 1 ns and the clk to Q delay for the register is 1ns. What is the maximum delay possible through the adder and still guarantee correct operation at 100MHZ?

 3. [6 points] Derive the truth table for the combinational logic circuit shown below:



abc	f
000	
001	
010	
011	
100	
101	
110	
111	


4.[6 points] For the boolean logic operation $(a + b + c)(d + e + f)(g + h + i)$,

(a) Draw a circuit schematic that implements the equation using only 3-input gates:

(b) Draw a circuit schematic for the same equation using only 2-input gates:

 5. Considering the design of a simple 8-bit wide computer with:

- a single data operand register, ACC,
- a 64 X 8-bit ROM
- an 8-bit instruction register (IR)
- a 2-input 8-bit ALU with 2 bits of control (S) defined as follows:



Instructions are in the form of:

OP	ADDR
----	------

 with 2 bits for the OP field and 6 bits for the ADDR field.

(a) [12 point] Three instructions; ADD, SUB, and NOR, correspond to the instruction opcodes 00, 01, 10 respectively and work as follows:

$$ACC \leftarrow ACC \text{ OP } ROM[ADDR]$$

Draw a simple datapath for executing these instructions. Label all necessary control signals. Do not design the controller or the internal details of the ROM, ALU, and registers. Also, you do not need to show details of the instruction fetch or PC logic.

How many cycles do these instructions take to execute?

(b) [10 points] Draw another datapath with all the capabilities of the above one, plus with the ability to execute a new instruction with the following function:


$$ACC \leftarrow ROM[ROM[ADDR]]$$

conversion

Again, you do not need to design the controller. *Keep your design simple!*

How many cycles do these instructions take to execute?

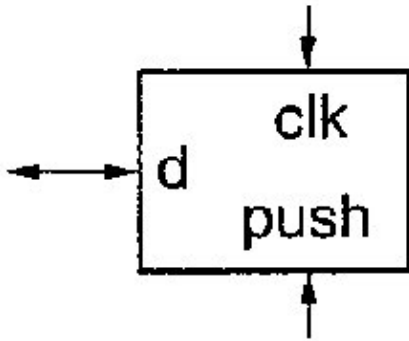6. [25 points] Consider the design of a 1-bit wide 4-element deep stack (FILO buffer), defined below:



On each cycle:

if push = 1

then the value presented on d is pushed on the stack

else if push = 0

then a value is popped from the stack and appears on d


Example:

cycle	push	d	stack values (at end of cycle)
0	1	A	AXXX
1	1	B	BAXX
2	1	C	CBAX
3	1	D	DCBA
4	1	E	EDCB
5	0	E	DCBB
6	0	D	CBBB

Where X = "unknown value"

Using only the following set of primitives:

conversion

 

draw the schematic for a circuit that implements the stack.

Circuit Diagram:

-end-