

Score summary (leave blank):	Name: <b>Solution</b>
P1: _____	SID: _____
P2: _____	Discussion section (day / time): _____
P3: _____	Lab section (day / time): _____
P4: _____	
P5: _____	
P6: _____	
Total: _____	

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**


**B. E. BOSER**

**Midterm 2**  
**Solution**

**EECS 42/100**  
**FALL 2006**

- *One 8.5" x 5.5" sheet with equations, two-sided.  
(originals only, handwritten; no computer output or photocopies, equations only,  
no problem solutions).*
- *No electronic devices (store calculators and phones in hallway).*
- *Copy your answers into marked boxes on exam sheets.*
- *Simplify numerical and algebraic results as much as possible.  
**Up to 10 points penalty for results that are not reasonably simplified.***
- *Mark your name and SID at the top of the exam and all extra sheets.*
- *Be kind to the graders and write legibly. No credit for illegible results.*
- *No credit for multiple differing answers for same problem.*

**Problem 1** [17 points]

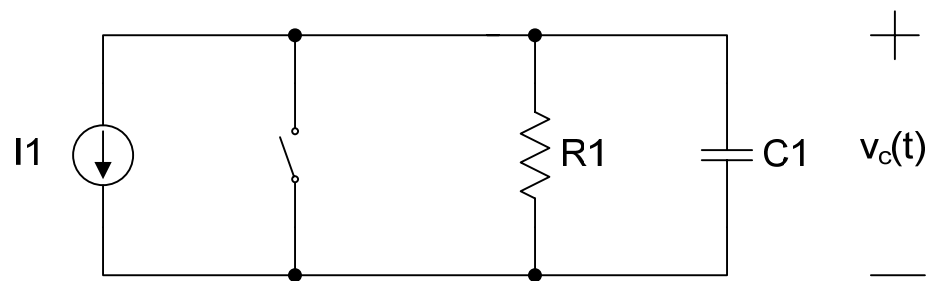


In the circuit shown above, the switch *opens* at  $t=0$ . Find an algebraic for  $v_c(t)$ ,  $t>0$ . Assume that the circuit has reached steady state at  $t=0$  (i.e. the node voltages are not changing just before the switch is closed). Given:  $I_1$ ,  $R_1$ ,  $C_1$ .

$$v_c(t) = -I_1 R_1 \left( 1 - e^{-t/R_1 C_1} \right)$$

**Partial credit:**

- Correct exponent: 5pts
- Correct at  $t=0$ : 5pts
- Correct at  $t \rightarrow \text{infinity}$ : 5pts
- Sign error: -3pts (each sign)

**Problem 2** [17 points]

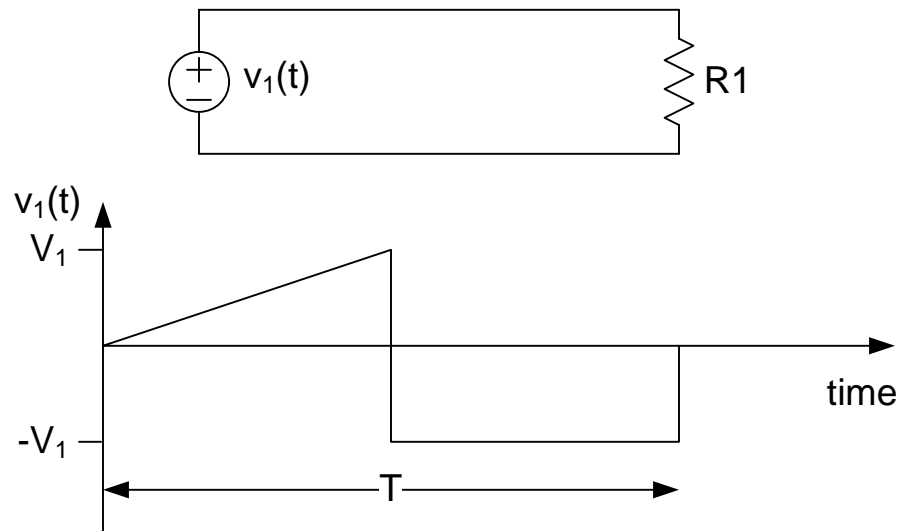

The voltage  $v_1(t)$  in the above circuit is periodic with period  $T$ . Find an algebraic expression for the average power dissipated in  $R_1$ .

Given:  $V_1$ ,  $T$ ,  $R_1$ .

$$P = \frac{V_1^2}{R_1} \left( \frac{1}{6} + \frac{1}{2} \right) = \frac{2}{3} \frac{V_1^2}{R_1}$$


$$P_1 = \frac{V_1^2}{R_1} \cdot \frac{1}{T} \cdot \int_0^{T/2} \left( \frac{t}{T/2} \right)^2 dt = \frac{V_1^2}{R_1} \cdot \frac{1}{T} \cdot \frac{(T/2)^3}{3 \cdot (T/2)^2} = \frac{V_1^2}{R_1} \cdot \frac{1}{6}$$

$$P_2 = \frac{V_1^2}{R_1} \cdot \frac{1}{2}$$

**Partial credit:**

- P1 correct: 12 pts
- P2 correct: 5pts
- Penalty for 2x more power: -3pts

**Problem 3** [17 points]

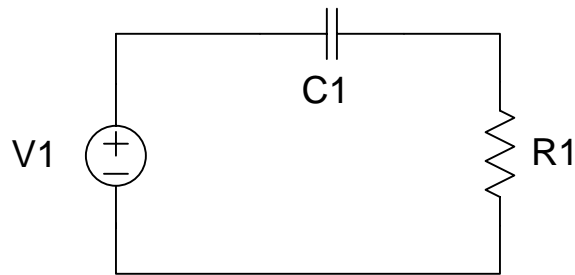

V1 is a sinusoidal source with frequency  $\omega$  and amplitude V1. Find algebraic expressions for the actual (i.e. the power dissipated by the circuit) and reactive power delivered by the source.

Given: V1,  $\omega$ , R1, C1.

$$P = \frac{V_1^2}{2} \cdot R \cdot \frac{(\omega \cdot C)^2}{1 + (\omega \cdot R \cdot C)^2}$$

$$Q = -\frac{V_1^2}{2} \cdot \frac{1}{\omega \cdot C} \cdot \frac{(\omega \cdot C)^2}{1 + (\omega \cdot R \cdot C)^2} = -\frac{V_1^2}{2} \cdot \frac{\omega \cdot C}{1 + (\omega \cdot R \cdot C)^2}$$

$$Z(j \cdot \omega) = R + \frac{1}{j \cdot \omega \cdot C} = \frac{1 + j \cdot \omega \cdot R \cdot C}{j \cdot \omega \cdot C} = \frac{j \cdot \omega \cdot C - \omega^2 \cdot R \cdot C^2}{-\omega^2 \cdot C^2} = R - \frac{j}{\omega \cdot C} = R + \frac{1}{j \cdot \omega \cdot C}$$


$$(|Z(j \cdot \omega)|)^2 = \frac{1 + (\omega \cdot R \cdot C)^2}{(\omega \cdot C)^2}$$

$$P = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos(\Phi) = V_{\text{rms}} \cdot \frac{V_{\text{rms}}}{|Z|} \cdot \frac{R}{|Z|} = \frac{V_1^2}{2} \cdot \frac{R}{(|Z|)^2}$$

**Partial credit:** (min penalty for any error: 2pts)

- P correct: 9pts
- Q correct: 9pts
- $|Z|^2$  correct: 6pts
- Correct eq for P, Q: 6pts

**Problem 4** [17 points]

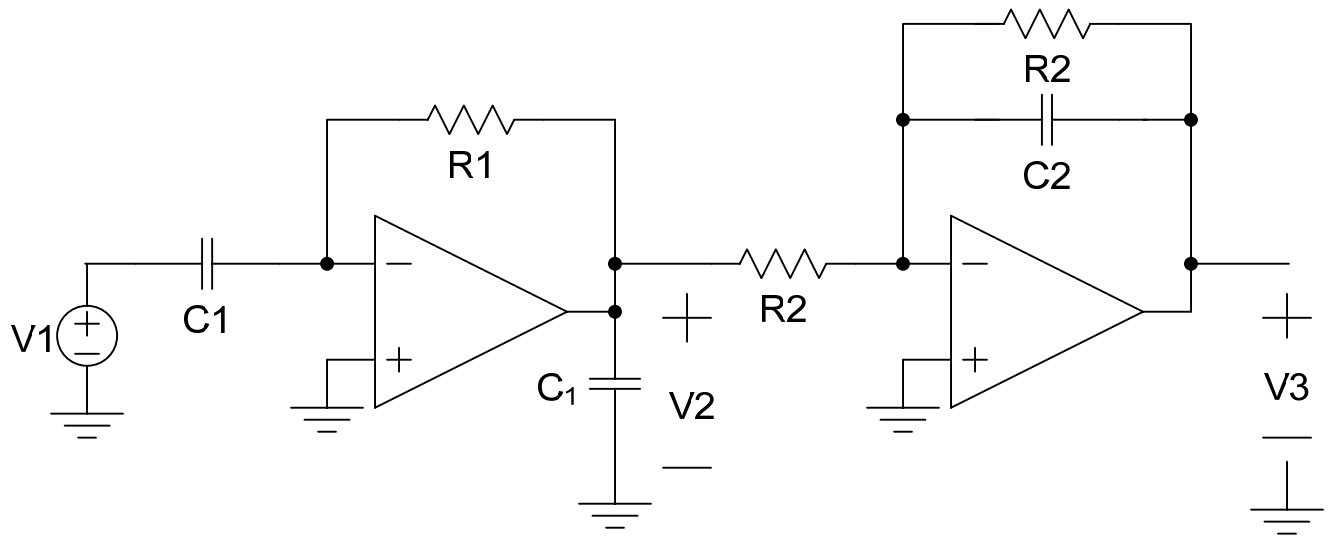

Derive an algebraic expression for  $H(j\omega) = \frac{V_3(j\omega)}{V_1(j\omega)}$ .

Given:  $R_1, C_1, R_2, C_2$  (note: there are two capacitors with value  $C_1$  and two resistors with value  $R_2$ ).

$$H(j \cdot \omega) = \frac{j \cdot \omega \cdot R_1 \cdot C_1}{1 + j \cdot \omega \cdot R_2 \cdot C_2}$$

$$i_1 = v_1 \cdot j \cdot \omega \cdot C$$

$$v_2 = -R_1 \cdot i_1 = -v_1 \cdot j \cdot \omega \cdot R_1 \cdot C_1$$

$$i_2 = \frac{v_2}{R_2}$$

$$v_3 = -\frac{R_2}{1 + j \cdot \omega \cdot R_2 \cdot C_2} \cdot \frac{1}{R_2} \cdot v_2$$

$$H(j \cdot \omega) = \frac{v_3}{v_1} = \frac{v_2}{v_1} \cdot \frac{v_3}{v_2} = -(j \cdot \omega \cdot R_1 \cdot C_1) \cdot \left( -\frac{1}{1 + j \cdot \omega \cdot R_2 \cdot C_2} \right)$$

**Partial credit:**


- $V_2/V_1$  correct: 8pts
- $V_3/V_2$  correct: 8pts
- Sign error: -4pts
- Left as double fraction: -3pts
- Nominator error: -8pts
- Denominator error: -8pts

**Problem 5** [17 points]

In the graph paper provided below draw the Bode plot for  $H_1(j\omega)$  in green,  $H_2(j\omega)$  in blue, and  $H_3(j\omega) = H_1(j\omega) \times H_2(j\omega)$  in red.

Use piece-wise linear approximations of the magnitude (do NOT “round” the corners).  
Note: neatness counts!
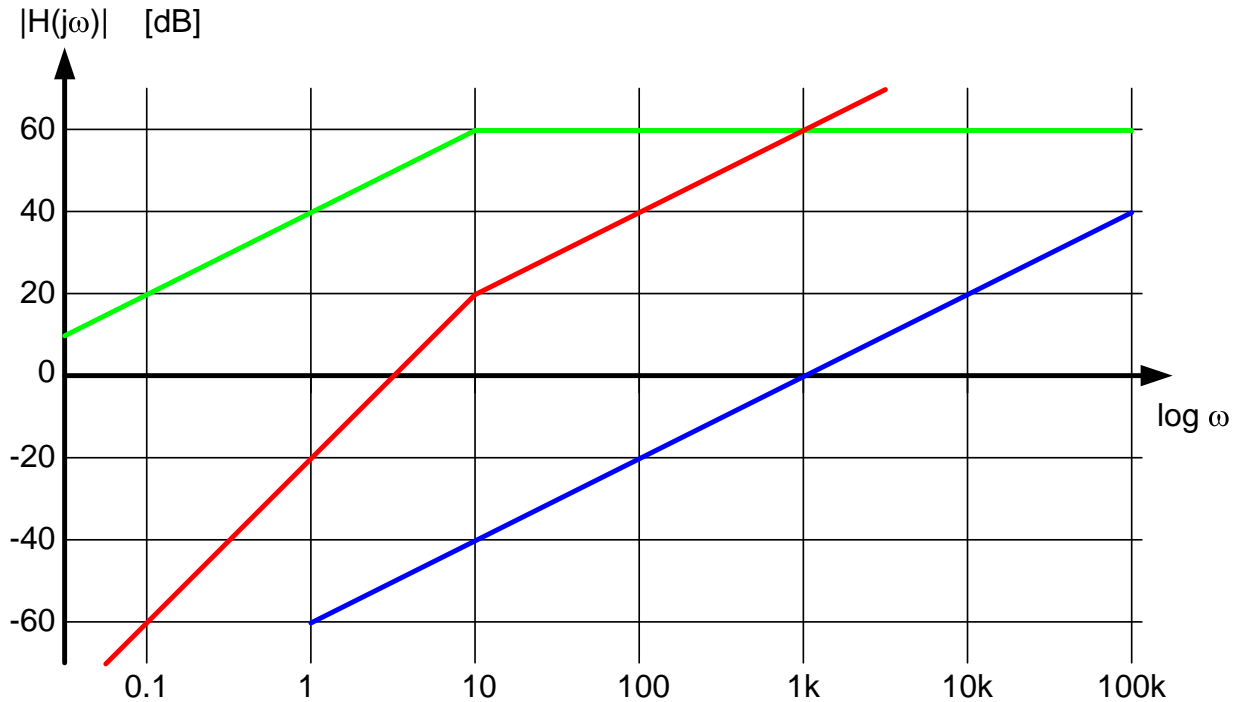
$$\text{Given: } H_1(j\omega) = \frac{100j\omega}{1 + \frac{j\omega}{10}}, \quad H_2(j\omega) = \frac{j\omega}{1000}$$



**Partial credit:** (max 15 pts for a solution that is only partially correct)


- $H_1$  correct: 8pts
  - a. Breakpoint wrong: -5pts
  - b. Slope wrong: -4pts (each slope)
  - c. Gain error: -4pts (i.e. shifted vertically)
- $H_2$  correct: 8pts
  - a. Slope wrong: -4pts
  - b. Gain error: -4pts (i.e. shifted)
- $H_3 = H_1 + H_2$ : 4pts
- Penalty for  $H_3 \neq H_1 + H_2$ : -5pts

**Problem 6** [17 points]

An electronic filter has the magnitude response shown below (beyond 1krad/s the magnitude response of the filter is zero). The filter is fed the following input:

$$V_{in}(j\omega) = 0.5 \cos(t) + 2 \sin(100t) + 3 \cos(10,000t)$$

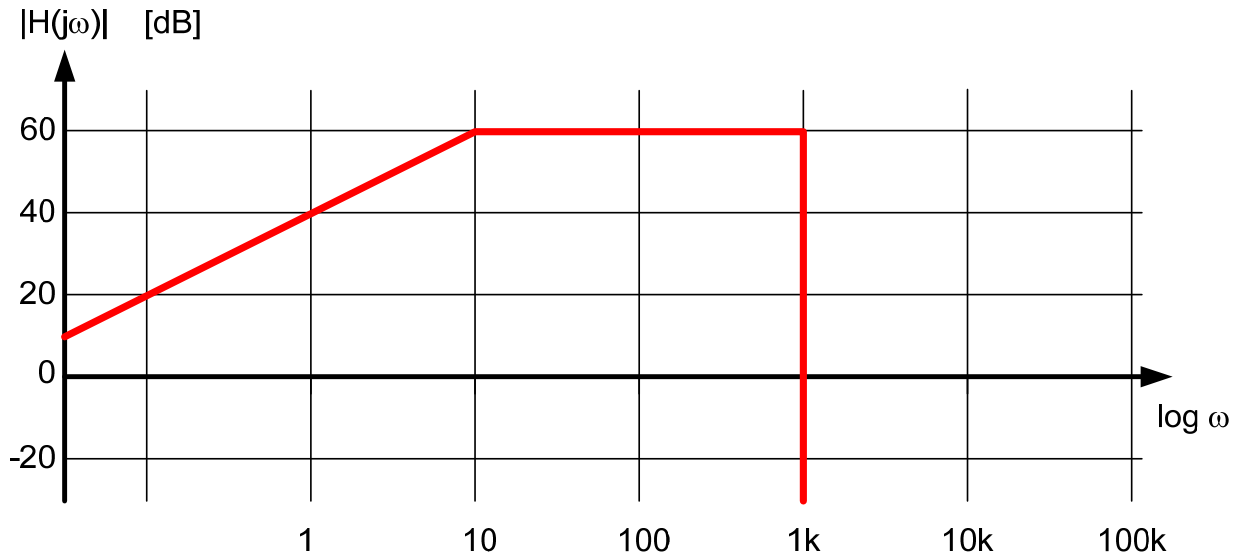Write an expression for the output voltage  $V_{out}(j\omega)$  of the filter (assume that the filter does not change the phase of the input).



$$V_{out}(j\omega) = 50 \cos(t) + 2000 \sin(100t)$$

**Partial credit:**

- Amplitude error: -6pts (each amplitude)
- Frequency error: -6pts (each frequency)
- Magnitude at 10k not zero: -6pts