

$$\textcircled{1} \text{ a) } g_m = \frac{\partial i_D}{\partial v_{DS}} \Big|_{Q_1} = \frac{C_{ox} W v_{sat}}{2} \left(\frac{1 + \lambda_n V_{DSAT}}{1 + \lambda_n V_{DS,SSAT}} \right) = \left(4 \times 10^{-7} F/cm^2 \right) (5 \times 10^{-4} cm) (10^7 cm/s) \left(\frac{1 + 0.075}{1 + (0.75)(0.05)} \right) = 10^{-3} S \left[\frac{1.075}{1.0375} \right] \approx 1.04 \text{ mS}$$

graphical technique : $g_m = \frac{\Delta i_D}{\Delta v_{DS}} \Big|_{Q_1}$ type in scale... should be 0.25mA
 $\approx \frac{0.5 \text{ mA}}{0.25 \text{ V}} \approx 2 \text{ mS}$

$$\textcircled{1} \text{ b) } r_o^{-1} = \frac{\partial i_D}{\partial v_{DS}} \Big|_{Q_1} = C_{ox} W v_{sat} (V_{DS} - V_{TN}) \left[\frac{\lambda_n}{1 + \lambda_n V_{DS,SSAT}} \right] = \left(4 \times 10^{-7} F/cm^2 \right) \cdot 5 \times 10^{-4} \text{ cm} \cdot 10^7 \text{ cm/s} \left[\frac{0.05}{1.03} \right] = 4.82 \times 10^{-5} \text{ S} \Rightarrow r_o = 20.75 \text{ k}\Omega$$

$$\textcircled{1} \text{ c) } g_m = \frac{\partial i_D}{\partial v_{DS}} \Big|_{Q_2} = C_{ox} W v_{sat} \left(\frac{V_{DS}}{V_{DS,SSAT}} \right) \left(1 - \frac{V_{DS}}{2V_{DS,SSAT}} \right) = 2 \times 10^{-3} \left(\frac{0.25}{0.75} \right) \left(1 - \frac{0.25}{2(0.75)} \right) \text{ S} = 0.55 \text{ mS}$$

graphical technique : $g_m = \frac{\Delta i_D}{\Delta v_{DS}} \Big|_{Q_2} = \frac{0.6 - 0.45 \text{ mA}}{1.75 - 1.5 \text{ V}} = 0.6 \text{ mS}$

$$\textcircled{1} \text{ d) } r_o^{-1} = \frac{\partial i_D}{\partial v_{DS}} \Big|_{Q_2} = C_{ox} W v_{sat} (V_{DS} - V_{TN}) \left[\frac{1}{V_{DS,SSAT}} - \frac{V_{DS}}{V_{DS,SSAT}^2} \right]; V_{DS} = 1.5 \text{ V}, V_{DS,SSAT} = 0.25 \text{ V}. \\ = 2 \times 10^{-3} (0.5) \left[\frac{1}{0.75} - \frac{0.25}{(0.75)^2} \right] = 8.9 \times 10^{-4} \text{ S} \Rightarrow r_o = 1.1 \text{ k}\Omega$$

$$r_o^{-1} \approx \frac{\Delta i_D}{\Delta v_{DS}} \Big|_{Q_2} \approx \frac{0.2 \text{ mA}}{0.25 \text{ V}} \Rightarrow r_o = 1.25 \text{ k}\Omega$$

$$\textcircled{2} \text{ a) } V_{out} = 2.5 \text{ V} \Rightarrow V_B = V_{out} + V_{BE} = 3.2 \text{ V}$$

$$\text{b) } V_{out} = 2.5 \text{ V}, R_E = 5 \text{ k}\Omega \Rightarrow -I_E = \frac{2.5 \text{ V}}{5 \text{ k}\Omega} = 500 \mu\text{A} \quad I_C = -\alpha_F I_E = 495 \mu\text{A}.$$

$$\text{c) common-collector amplifier} \Rightarrow R_{in} = r_n + \beta_0 (r_o \parallel R_E \parallel R_L). \quad r_{\pi} = \frac{\beta_0}{g_m} = \frac{100 (25 \text{ mV})}{500 \mu\text{A}} = 5 \text{ k}\Omega$$

$$R_{in} = 5 \text{ k}\Omega + 100 (100 \text{ k}\Omega \parallel 5 \text{ k}\Omega \parallel 2.5 \text{ k}\Omega) = 16.9 \text{ k}\Omega \quad r_o = \frac{V_A}{I_C} = \frac{50 \text{ V}}{0.5 \text{ mA}} = 100 \text{ k}\Omega.$$

$$\text{d) } R_{out} = g_m^{-1} + R_S \parallel \beta_0 = \frac{25 \text{ mV}}{0.5 \text{ mA}} + \frac{5 \text{ k}\Omega}{100} = 50 \text{ }\Omega + 50 \text{ }\Omega = 100 \text{ }\Omega.$$

$$\text{e) } A_v = 1 \text{ (exact expression)} \quad \frac{1}{1 + \frac{r_{\pi}}{(r_o \parallel R_E) (\beta_0 + 1)}} = \frac{1}{1 + \frac{5 \text{ k}\Omega}{(100 \parallel 5) (101)}} = 0.99$$

$$\text{f) } \begin{array}{c} \text{Circuit diagram showing } V_S, R_S, R_{in}, R_{out}, R_L, V_{out}, V_{BE}, V_{DS}, \text{ and } R_{DS}. \\ \text{vout} = \frac{R_{in}}{R_S + R_{in}} \left(\frac{R_{out}}{R_S + R_{in}} \right) \left(\frac{R_L}{R_{out} + R_L} \right) = \left(\frac{16.9}{5 + 16.9} \right) \left(\frac{2.5}{100 + 2.5} \right) = 0.93 \end{array}$$

$$\text{g) } |v_{out}|_{max} = 5 - V_{CEsat} = 4.9 \text{ V}. \quad |v_{out}|_{min} = 0 \text{ V} [\text{but with } I_C \downarrow, \text{ parameters will change}]$$

$$\text{hand limit.} \quad \therefore |v_{o}|_{max} = (4.9 - 2.5) / 0.93 = 2.55 \text{ V}$$

$$\text{a) } I_C = \frac{q D_n A_E}{W_B} \cdot n_{PB}(0) \quad n_{PB}(0) = \frac{I_C W_B}{q D_n A_E} = \frac{2 \times 10^{-5} \text{ A} \cdot 1 \times 10^{-5} \text{ cm}}{(1.6 \times 10^{-19} \text{ C})(20 \text{ cm}^2/\text{s})(25 \times 10^{-8} \text{ cm}^2)} = 2.5 \times 10^{14} \text{ cm}^{-3}$$

$$\text{b) } n_{PB}(0) = n_{PB,0} e^{V_{BE}/V_{th}} \Rightarrow V_{BE} = V_{th} \ln \left[n_{PB}(0)/n_{PB,0} \right] = 25 \text{ mV} \ln \left[2.5 \times 10^{14} / n_{PB,0} \right]$$

$$n_{PB,0} = n_{PB}(0) e^{-V_{BE}/V_{th}} = 2.5 \times 10^{14} \text{ cm}^{-3} e^{-692.5/25} = 233$$

$$= n_i^2 / N_A \Rightarrow N_A = \frac{10^{20}}{233} = 4.3 \times 10^{17} \text{ cm}^{-3}$$

$$\text{c) } I_B = \frac{q D_p A_E}{W_E} P_{BE} (-x_{ce}) = \frac{1.6 \times 10^{-19} \cdot 5 \cdot 25 \times 10^{-8} \cdot (0.05) (2.5 \times 10^{14})}{7 \times 10^{-6}} = 357 \text{ nA}$$

$$\beta_F = \frac{I_C}{I_B} \approx 56$$