

UNIVERSITY OF CALIFORNIA, BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Sciences

EE 105: Microelectronic Devices and Circuits

Fall 2009

MIDTERM EXAMINATION #2

10/29/2009

Time allotted: 75 minutes

NAME: _____

STUDENT ID#: _____

INSTRUCTIONS:

- 1. SHOW YOUR WORK. (Make your methods clear to the grader!)**
- 2. Clearly mark (underline or box) your answers.**
- 3. Specify the units on answers whenever appropriate.**
- 4. Unless specified otherwise, include EARLY effect in your analysis.**

SCORE:1 _____ / 16

2 _____ / 16

3 _____ / 18

Total _____ / 50

PHYSICAL CONSTANTS

<u>Description</u>	<u>Symbol</u>	<u>Value</u>
Electronic charge	q	1.6×10^{-19} C
Boltzmann's constant	k	8.62×10^{-5} eV/K
Thermal voltage at 300K	$V_T = kT/q$	0.026 V

PROPERTIES OF SILICON AT 300K

<u>Description</u>	<u>Symbol</u>	<u>Value</u>
Band gap energy	E_G	1.12 eV
Intrinsic carrier concentration	n_i	10^{10} cm^{-3}
Dielectric permittivity	ϵ_{Si}	1.0×10^{-12} F/cm


USEFUL NUMBERS

$$V_T \ln(10) = 0.060 \text{ V at } T=300\text{K}$$

$$\exp(30) \sim 10^{13}$$

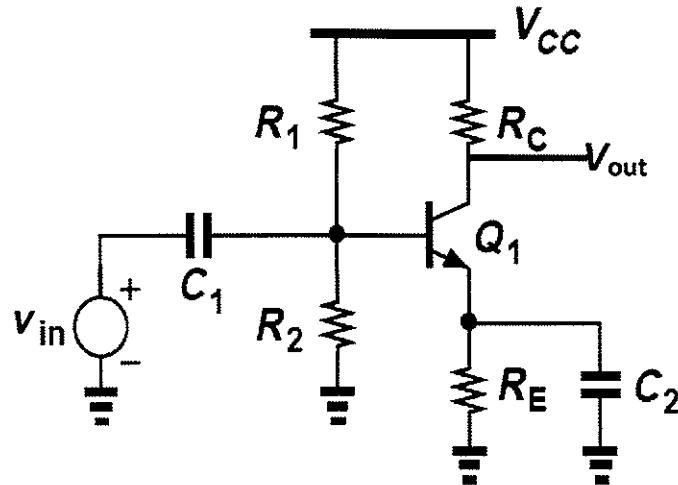Problem 1: BJT Amplifiers [16 pts]

Consider the BJT amplifier shown below. Ignore Early effect for all cases.



- a) [2 pts] How does R_1 and R_2 help the amplifier?

to minimize β variation

- b) [2 pts] What is the purpose of having R_E ?

minimize the effect of variation in R_1 and R_2 .

- c) [6 pt] What are the input and output resistances?


$$Z_{in} = R_1 \parallel R_2 \parallel r_\pi$$

$$Z_{out} = R_c$$

d) [3 pts] What is the small signal voltage gain?

$$A_V = - \frac{R_E}{1/g_m} = - g_m R_E$$

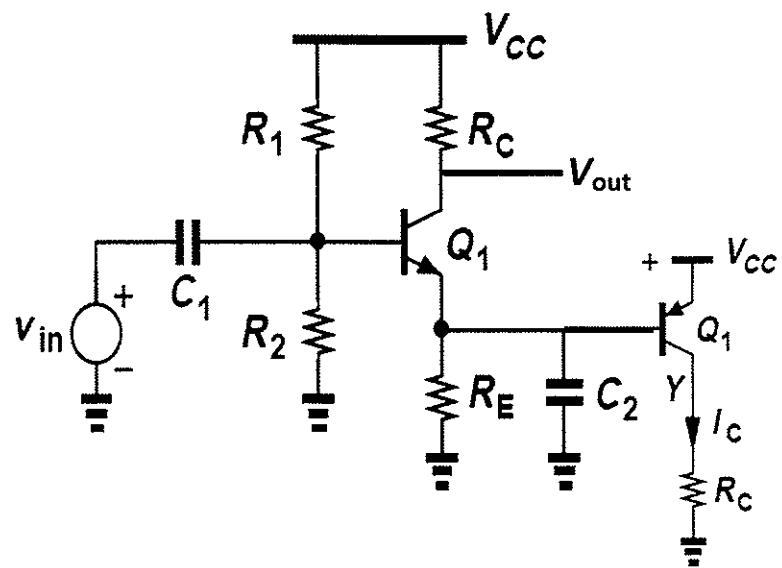
e) [3 pts] Now consider that a PNP transistor is added to the emitter of the amplifier as shown below. What will be the small signal voltage gain?



$A_V = - g_m R_E$ because the PNP transistor
is shorted by C_2 .

PROB 2. BJT Amplifiers and Cascodes [16 pts].

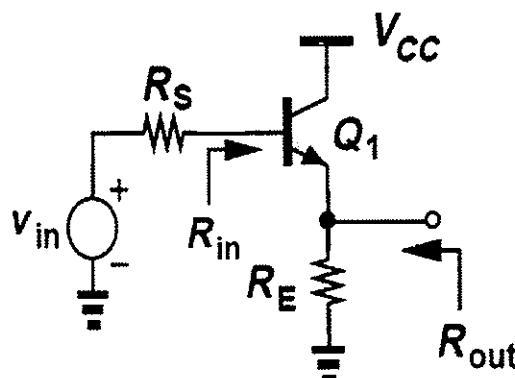- a) [6 pts] What is the gain of the following amplifier? Where would you use such an amplifier?
Why? Ignore the early effect.



$$A_v = \frac{R_E}{1/g_m + R_E} \ll 1$$

it can be used as a buffer stage
between a CE stage and a small load.


Reason: Putting a CE stage directly to a small load degrades the gain. This particular stage gives high input impedance and low output resistance; thereby matching the

- b) [2 pts] How do cascodes help in amplifier design?

impedance between CE stage and a small load.

Cascodes boost the output impedance thereby increasing the gain.

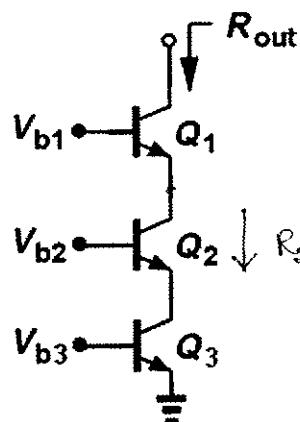- c) [4 pts] What is the **maximum** output impedance of the following cascade?




$$R_{out} = r_{o1} + (1 + g_m r_{o1}) \left\{ r_{\pi_1} || R_2 \right\} \approx g_m r_{o1} (r_{\pi_1} || R_2)$$

$$R_2 = r_{o2} + (1 + g_m r_{o2}) (r_{\pi_3} || r_{\pi_2})$$

$$\approx g_m r_{o2} (r_{\pi_3} || r_{\pi_2})$$

$$\text{Since, } R_2 \gg r_{\pi_2}, \quad R_2 || r_{\pi_1} \approx r_{\pi_1} \quad \therefore R_{out} \approx g_m r_{o1} r_{\pi_1}$$

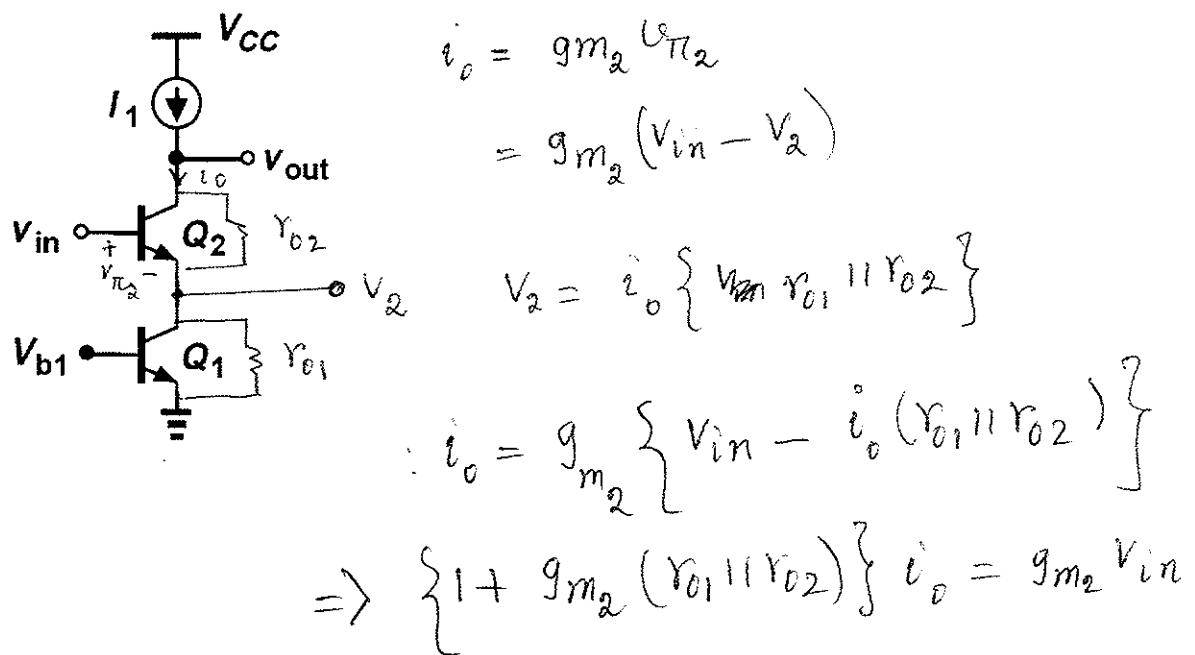- d) [4 pt] Explain why the following is not a good cascade. How will you change the design to obtain a larger small signal gain?



$$\therefore G_m = \text{overall gain} = \frac{i_o}{v_{in}}$$

$$G_m = \frac{g_{m2}}{1 + g_{m2} (r_{o1} \| r_{o2})}$$

Hence overall gain is very small.


An easy way to solve this problem is to inter change V_{b1} and V_{in}

$$\therefore A_v = - g_{m1} \{ r_{o2} + (1 + g_{m2} r_{o2}) (r_{o1} \| r_{T1}) \}$$

$$A_v \approx - g_{m1} g_{m2} r_{o2} (r_{o1} \| r_{T1})$$

PROB 3. Current mirrors and Frequency Response. [18 pts]

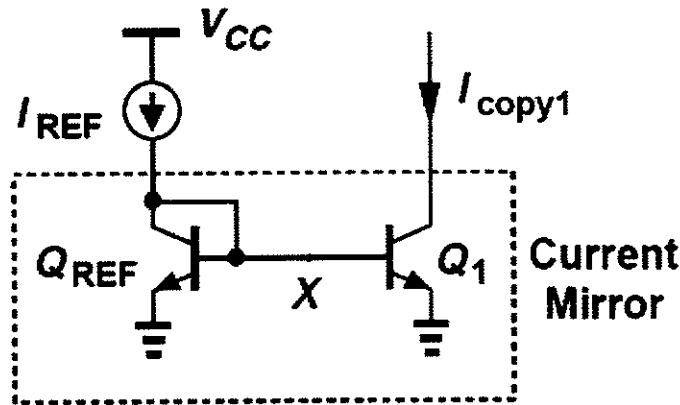
- a) [3 pts] Neglecting base currents find $I_{\text{copy}1}$ as a function of I_{REF}



$$V_x = V_T \ln \left(\frac{I_{\text{copy}1}}{I_{S1}} \right) = V_T \ln \left(\frac{I_{\text{REF}}}{I_{S\text{REF}}} \right)$$


$$\therefore E_{\text{COPY}_1} = \frac{I_{S1}}{I_{S\text{REF}}} I_{\text{REF}}$$

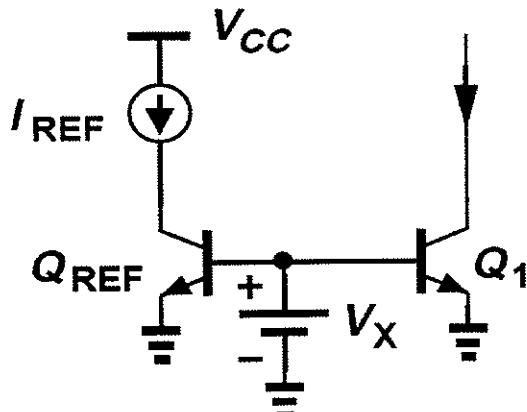- b) [3 pts] Why is the following not a good mirror?



Since V_x is fixed, I_{REF} a change in temp will affect $I_{\text{copy}1}$. Note that without the diode connection Q_{REF} and Q_1 are completely independent. V_c for Q_{REF} can be different than V_c at Q_1 .

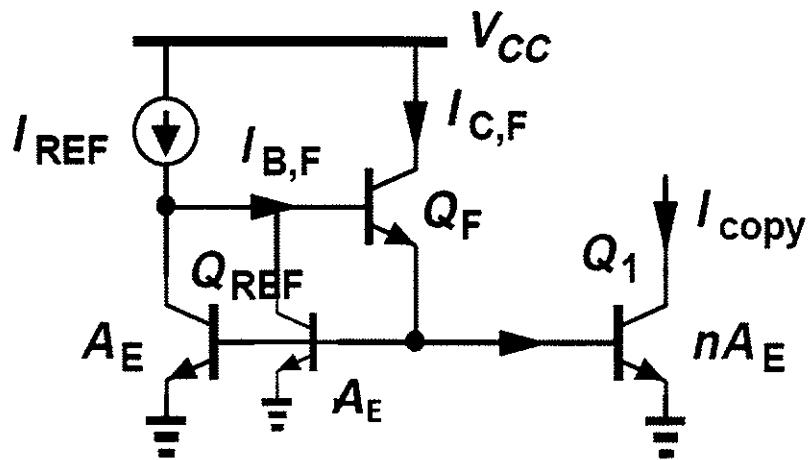c) [6 pts] For the following, derive an expression for I_{copy} as a function of I_{Ref} **including the base currents**.



$$I_{\text{REF}} = I_{\text{BF}} + 2 I_{\text{C}_{\text{REF}}} \quad - \textcircled{1}$$

$$I_{\text{C},F} \approx I_{\text{EF}} = \frac{2 I_{\text{copy}}}{n\beta} + \frac{I_{\text{copy}}}{\beta}$$

$$I_{\text{BF}} = \frac{I_{\text{copy}}}{\beta^2} \left[\frac{2}{n} + 1 \right] \quad - \textcircled{2}$$


$$I_{\text{C}_{\text{REF}}} = \frac{I_{\text{copy}}}{n} \quad - \textcircled{3}$$

From $\textcircled{1}$, $\textcircled{2}$ and $\textcircled{3}$

$$I_{\text{REF}} = I_{\text{copy}} \left[\frac{1}{\beta^2} \left\{ \frac{2}{n} + 1 \right\} + \frac{2}{n} \right]$$

$$\boxed{I_{\text{copy}} = \frac{n I_{\text{REF}}}{2 + \frac{1}{\beta^2} (n+2)}}$$

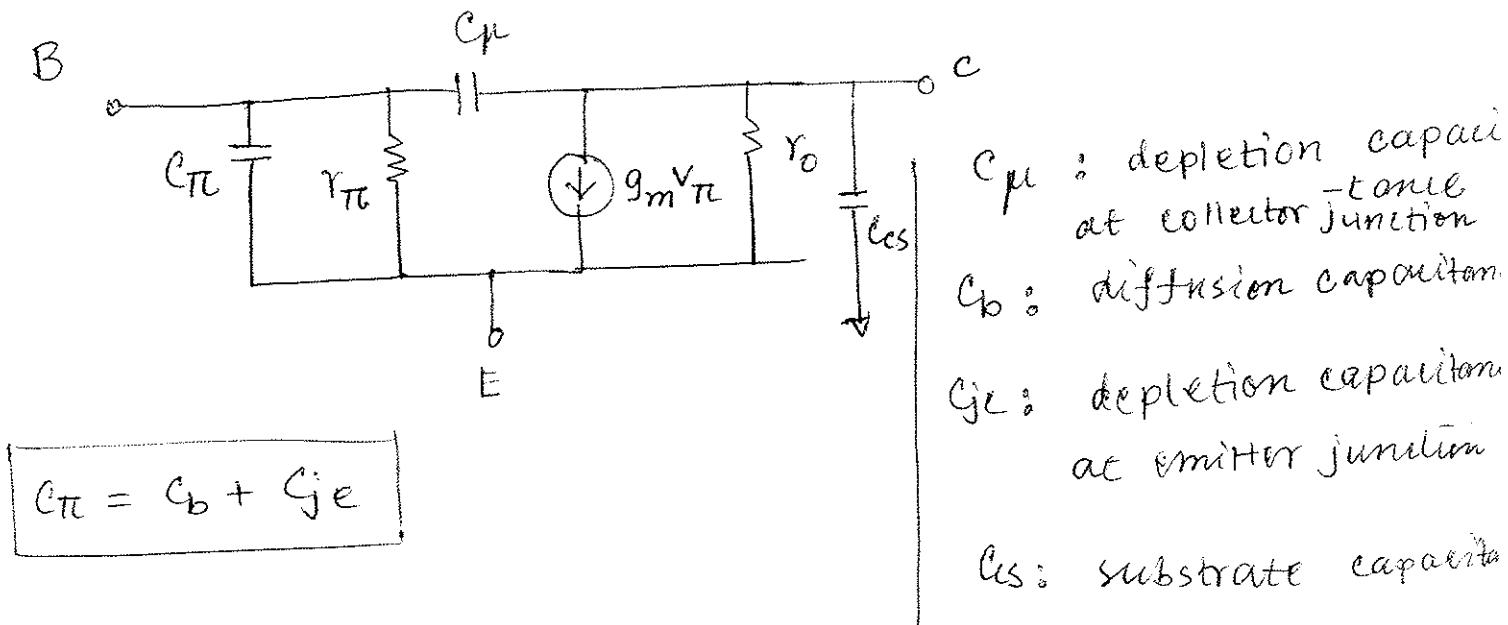- d) [2pts] Draw the high frequency model of a CE stage. Mention physical origins for each of the capacitances in this model.




C_{pe} : depletion capacitors at collector junction

C_b : diffusion capacitors

C_{je} : depletion capacitors at emitter junction

C_{cs} : substrate capacitors

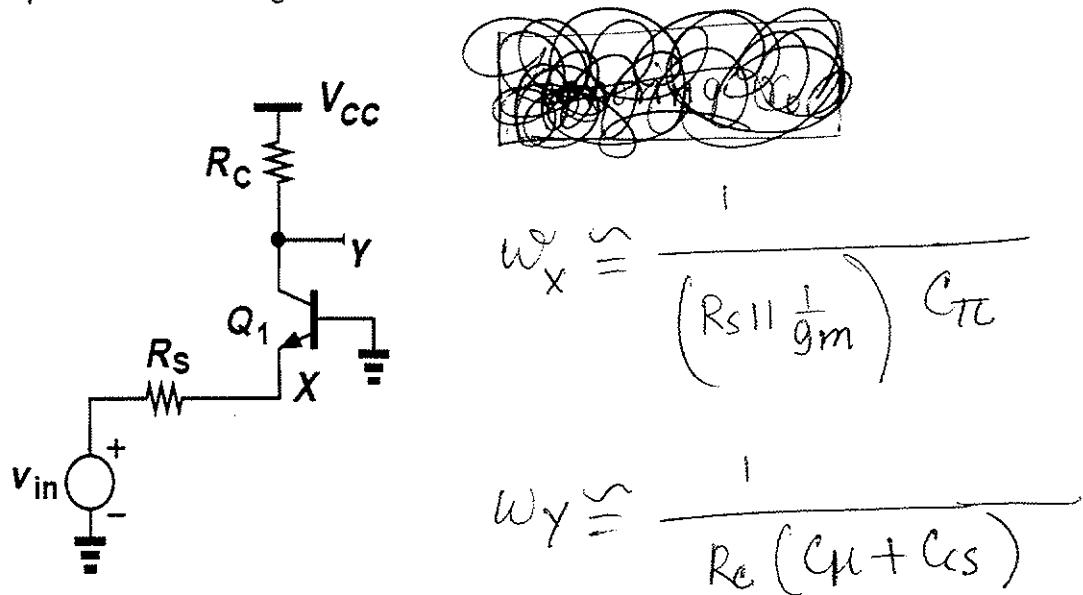- e) [4 pts] Find out the poles of the following circuit at nodes X and Y.



Note that looking into Y:

$$R = R_c \parallel (r_o + (1+g_m r_o) R_s) \approx R_c$$