

**EECS 105, Fall 1993
Midterm #2
Professor R. T. Howe**

Ground Rules:

- Closed book and notes; one formula sheet (both sides)
- Do all work on exam pages
- Answers accurate to within 10% will receive full credit
- Default bipolar transistor parameters:

$$\text{nnp: } (\beta)_n = 100, V_{An} = 50 \text{ V}, I_{Sn} = 10^{-16} \text{ A.}$$

$$\text{pnp: } (\beta)_p = 50, V_{Ap} = 25 \text{ V}, I_{Sp} = 10^{-16} \text{ A.}$$


- Default MOS transistor parameters:

$$\text{NMOS: } (\mu)_n C_{ox} = 50 (\mu)\text{AV}^{-2}, (\lambda)_n = 0.02\text{V}^{-1}, V_{Tn} = 1 \text{ V.}$$

$$\text{PMOS: } (\mu)_p C_{ox} = 25 (\mu)\text{AV}^{-2}, (\lambda)_p = 0.02\text{V}^{-1}, V_{Tp} = -1 \text{ V.}$$

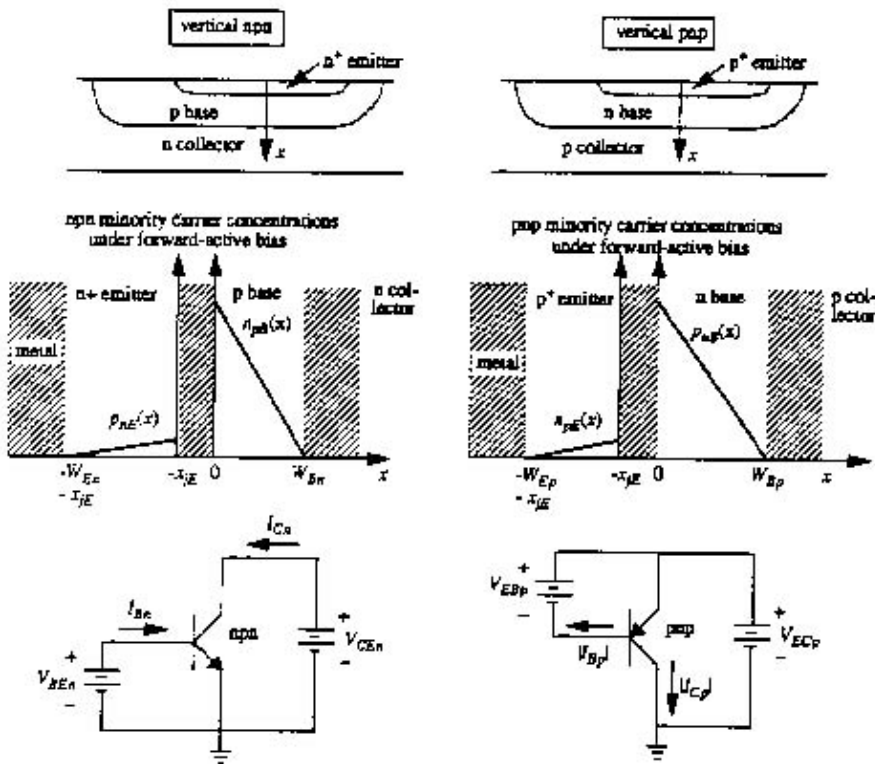Problem #1. Matched Complementary Bipolar Transistor Design [12 points]

The cross sections, minority carrier concentrations, and circuit schematics are shown for matched npn and pnp vertical BJTs, operated in the forward-active region.



Given: all doping levels are matched and the emitter areas are identical

- $N_{dE}(\text{nnp}) = N_{aE}(\text{pnp})$
- $N_{aB}(\text{nnp}) = N_{dB}(\text{pnp})$
- $N_{dC}(\text{nnp}) = N_{aC}(\text{pnp})$
- $A_E(\text{nnp}) = A_E(\text{pnp})$

Given: the bias voltages for the two transistors are matched and both are in the forward-active region

- $V_{BE n} = V_{EB p}$
- $V_{CE n} = V_{EC p}$

(a) [5 pts.] In order for the npn and the pnp transistors to have *matched collector currents*, $I_{Cn} = |I_{Cp}|$, determine the numerical value of the *base width of the pnp*, W_{Bp} .


Given: the base width of the npn is $W_{Bn} = 0.2$ (μ)m, the electron diffusion coefficient (diffusivity) is $D_n = 20 \text{ cm}^2\text{s}^{-1}$, and the hole diffusivity is $D_p = 10 \text{ cm}^2\text{s}^{-1}$ -- these are valid for the emitter, base, and collector of each transistor.

(b) [5 pts.] In order for the npn and the pnp transistors to *matched base currents*, $I_{Bn} = |I_{Bp}|$, determine the numerical value of the *emitter width of the pnp*, W_{Ep} . This part is independent of part (a).

Given: the emitter width of the npn is $W_{En} = 0.1$ (μ)m, and $D_n = 20 \text{ cm}^2\text{s}^{-1}$, $D_p = 10 \text{ cm}^2\text{s}^{-1}$.

(c) [2 pts.] Which transistor has the smaller Early voltage, V_A ? Explain why in one sentence.

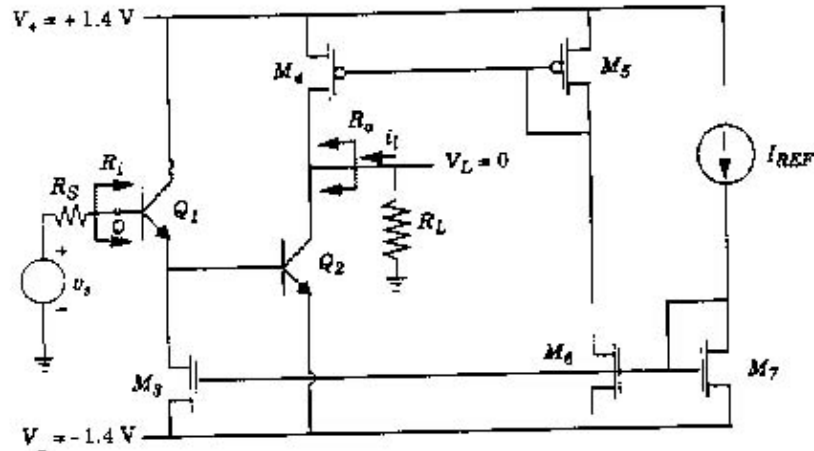
Problem #2. Two-Stage Transconductance Amplifier [24 points]



Given: $I_{REF} = 100 \text{ } (\mu\text{A})$, $V_L = 0 \text{ (DC)}$, $R_S = 1 \text{ k}(\Omega)$, $R_L = 400 \text{ k}(\Omega)$
 MOSEFTs: $(W/L)_{3,5,6,7} = 10$ and $(W/L)_4 = 25$

- (a) [4 pts.] Find the collector currents I_{C1} and I_{C2} . You can neglect the base currents I_{B1} and I_{B2} , as is customary for hand calculations.
- (b) [4 pts.] Find the numerical value of the input resistance, R_i of this amplifier. If you couldn't answer part (a), you can assume that $I_{C1} = 50 \text{ } (\mu\text{A})$ and that $I_{C2} = 75 \text{ } (\mu\text{A})$ for this part.
- (c) [4 pts.] Find the numerical answer value of the output resistance, R_o of this amplifier. If you couldn't answer part (a), you can assume that $I_{C1} = 50 \text{ } (\mu\text{A})$ and that $I_{C2} = 75 \text{ } (\mu\text{A})$ for this part.
- (d) [4 pts.] Find the numerical value of the short-circuit transconductance G_m of the amplifier. Again, if you couldn't answer part (a), you can assume that $I_{C1} = 50 \text{ } (\mu\text{A})$ and that $I_{C2} = 75 \text{ } (\mu\text{A})$ for this part.
- (e) [5 pts.] Find the numerical value of the load current i_L , for a small-signal input voltage $v_s = 2 \text{ mV}$. If you couldn't solve parts (b), (c), and (d), assume for this part that $R_i = 80 \text{ k}(\Omega)$, $R_o = 500 \text{ k}(\Omega)$, and $G_m = 7.5 \text{ mS}$.
- (f) [3 pts.] What is the DC voltage at the base Q_1 ? You can assume that $V_{BE} = 0.7\text{V}$ for the transistors in the forward-active region.

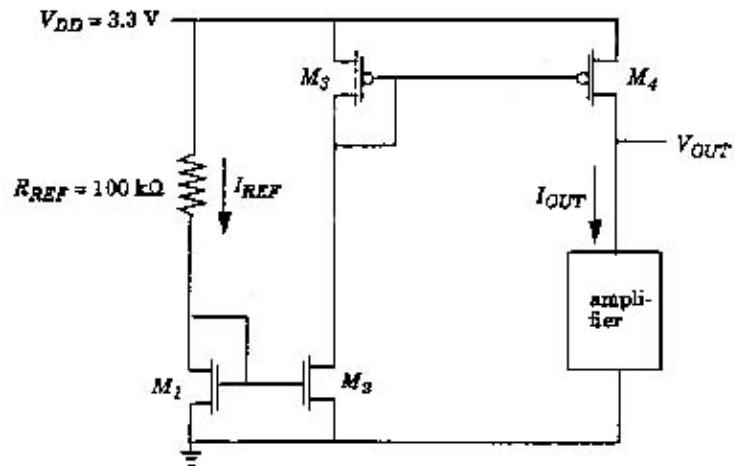Problem #3. Current-Source Design [14 points]



Given: $(W/L)_1 = (W/L)_2 = (W/L)_3$

(a) [5 pts.] Find $(W/L)_1$ such that $I_{REF} = 20$ (μ)A.

(b) [3 pts.] Find $(W/L)_4$ such that $I_{OUT} = 50$ (μ)A. If you couldn't solve part (a), assume that $(W/L)_1 = 10$.

(c) [3 pts.] Find the numerical value of r_{oc} for this current source, assuming that $I_{OUT} = 50$ (μ)A.

(d) [3 pts.] Assuming that the source-gate voltage for transistor M_4 is $V_{SG4} = 1.4$ V. What is the largest DC output voltage V_{OUT} for which transistor M_4 remains in the saturation region?

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley**

**If you have any questions about these online exams
please contact examfile@hkn.eecs.berkeley.edu.**