

**Microelectronic Devices and Circuits- EECS105**  
**Final Exam**

Wednesday, December 8, 1999

Costas J. Spanos

University of California at Berkeley

College of Engineering

Department of Electrical Engineering and Computer Sciences

Your Name: Official Solutions  
(last) (first)

Your Signature: \_\_\_\_\_

1. Print and sign your name on this page before you start.
2. You are allowed three, 8.5"x11" handwritten sheets. No books or notes!
3. Do everything on this exam, and make your methods as clear as possible.

Problem 1 \_\_\_\_\_ / 24  
 Problem 2 \_\_\_\_\_ / 28  
 Problem 3 \_\_\_\_\_ / 24  
 Problem 4 \_\_\_\_\_ / 24  
 TOTAL \_\_\_\_\_ / 100

AVG = 69  
 $\hat{\sigma} = 17.3$

MOS Device Data (you may not have to use all of these...):

$\mu_n C_{ox} = 50 \mu A/V^2$ ,  $\mu_p C_{ox} = 25 \mu A/V^2$ ,  $V_{Tn} = -V_{Tp} = 1V$ ,  $L_{min} = 2 \mu m$ ,  $V_{BS} = 0$ .  
 $\lambda_n = \lambda_p = 0.1 V^{-1}$  when  $L = 2 \mu m$ , and it is otherwise proportional to  $1/L$   
 $C_{ox} = 2.3 fF/\mu m^2$ ,  $C_{jn} = 0.1 fF/\mu m^2$ ,  $C_{jp} = 0.3 fF/\mu m^2$ ,  $C_{jsw n} = 0.5 fF/\mu m$ ,  
 $C_{jsw p} = 0.35 fF/\mu m$ ,  $C_{ovn} = 0.5 fF/\mu m$ ,  $C_{ovp} = 0.5 fF/\mu m$

npn Data  $I_S = 10^{-17} A$ ,  $\beta = 100$ ,  $V_A = 25V$ ,  $\tau_F = 50ps$ ,  $C_{je} = 15 fF$ ,  $C_{\mu} = 10 fF$   
pnnp Data  $I_S = 10^{-17} A$ ,  $\beta = 50$ ,  $V_A = 25V$ ,  $\tau_F = 50ps$ ,  $C_{je} = 15 fF$ ,  $C_{\mu} = 10 fF$


**Problem 1 of 4: Answer each question briefly and clearly. (4 points each, total 24)**

Mark in the table below the npn Bipolar Transistor in forward action mode the direction of flow, and the type of flow (drift or diffusion) of electrons, in each of the bulk and depletion regions.

drift	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
diffusion	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
→	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
←	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

(place a mark at the appropriate box to indicate your answer. You can choose more than one box if appropriate.)

Where is the maximum |E| field in a forward-biased junction? Please place a mark on the graph below.

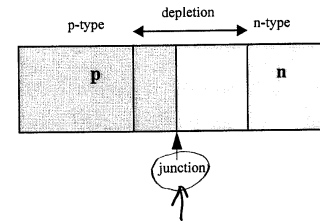

What happens to the drain current of an n-channel MOS transistor in saturation, when L and W increase proportionally? (i.e. L and W increase, but W/L stays constant. Assume that  $V_{GS}$ ,  $V_{BS}$  and  $V_{DS}$  stay constant. Do take  $\lambda$  into account!)


$$I_D = \frac{1}{2} \mu_n C_{ox} (V_{GS} - V_T)^2 \frac{W}{L} (1 + \lambda V_{DS})$$

constant

$\lambda \downarrow$  as  $L \uparrow$

$\Rightarrow I_D \downarrow$

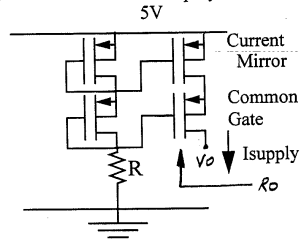
Name one advantage and one disadvantage of a MOS current source employing a CG buffer, versus one that does not employ one.



Advantage: High  $R_o$ ,  $I_{supply}$  depends on  $V_o$  less.


Disadvantage: Reduced  $V_o$  range

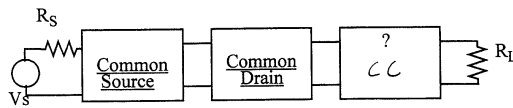The following multistage amplifier is meant to deliver a voltage signal to a relatively small ohmic load of  $1K\Omega$ . Mark your choice of the last stage, and write a brief justification.



A CC has very low output resistance (less than a CD) and a high input resistance. It makes a good final stage voltage buffer.

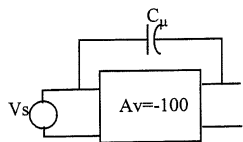
The following voltage amplifier has a voltage gain  $A_v = -100$ . What is the capacitance "seen" by the signal source, due to the added capacitor  $C_{in} = 1pF$  as shown?



$C_{in} = C_{in}(1 - A)$   
 $C_{in} = 1pF(1 - (-100))$   
 $C_{in} = 101pF$

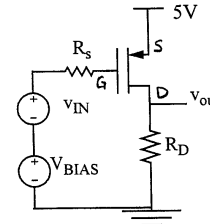**Problem 2 of 4 (28 points)**

The following p-channel common source amplifier uses a rather primitive current supply: it is a simple resistor  $R_D = 10k\Omega$  tied between drain and ground.  $L = 2\mu m$ ,  $\lambda_p = 0.1V^{-1}$ .



For each of the following questions, make sure that you show the expressions *before* you plug in the specific values. A correct expression is worth 70% of the credit, even if the numerical calculation is incorrect!

a) Find  $W/L$  so that when  $V_{BIAS} = 3.5$  and  $V_{in} = 0V$ , then  $V_{out} = 2.5V$ . Do take  $\lambda_p$  into account! Note that  $L = 2\mu m$ . (4 points)

$I_D = \frac{2.5V}{10k\Omega} = 250\mu A$        $I_D = \frac{1}{2} \cdot \frac{W}{L} \mu p Cox \cdot (V_{GS} - V_{TP})^2 (1 + \lambda_p V_{DS})$   
 $250\mu A = \frac{1}{2} \cdot \frac{W}{L} \cdot 25\mu A/V^2 \cdot (-1.5 - (-1))^2 (1 + 0.1 \cdot 2.5) \cdot \frac{W}{L}$   
 $\frac{2 \cdot 250\mu A}{25\mu A \cdot (1.05)^2 (1.25)} = \frac{W}{L} = 64$

$W/L = 128/2$

b) What is the minimum and the maximum output voltage for this amplifier? Make sure you mention the limiting reason for each case (i.e. transistor X falls out of saturation, or current source Y hits its minimum voltage drop, etc.). (4 points)

MAX  $V_{out} = 4.5V$       MAX Limited by: X falls out of saturation

MIN  $V_{out} = 0$       MIN Limited by: GND



f) What is the  $R_{in}$ ,  $A_v$ , and  $R_{out}$  of the new design? (4 points)

$$g_{m1} = \frac{2 \times 250 \mu A}{0.5} = \frac{1 \text{ mA}}{V}$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda_n I_{sup1}} = 40 \text{ k}\Omega$$

} The same as part c.

Parameter	Expression	Value
$A_v$	$-g_{m1} (r_{o1}    r_{o2})$	-20
$R_{in}$	$\infty$	$\infty$
$R_{out}$	$(r_{o1}    r_{o2})$	20 k $\Omega$

g) What is the minimum and the maximum output voltage of the new design? Make sure you mention the limiting reason for each case (i.e. transistor X falls out of saturation, or current source Y hits its minimum voltage drop, etc.). (4 points)

MAX  $V_{out} = 4.5$


MAX Limited by:  $m_1$  falls out of saturation

MIN  $V_{out} = 0.5$


MIN Limited by:  $m_2$  falls out of saturation
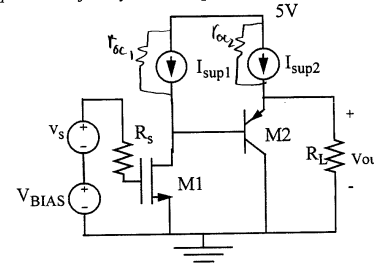
### Problem 3/4 (24 points)


The following is a two stage voltage amplifier employing a n-channel CS stage, and a pnp CC stage. Note that there are no numerical substitutions or calculations in parts a, b and c of this problem - just symbolic expressions!



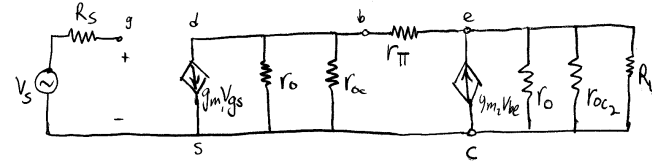a) Draw the small signal model for this amplifier (Make sure to properly mark the g, s and d nodes for M1, and b, c, and e nodes for M2. Include  $r_{oc1}$ ,  $r_{oc2}$  due to  $I_{sup1}$  and  $I_{sup2}$ , respectively). (6 points)




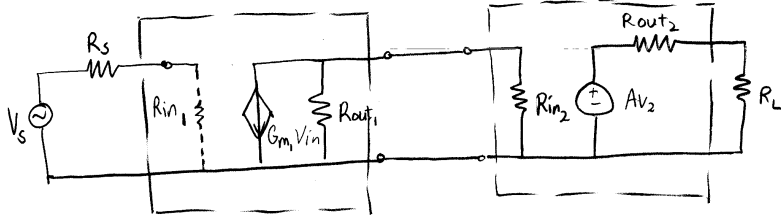b) Draw the two stage amp 2-port model (i.e. draw one 2-port of each stage and connect them properly together. CS is a transconductance amp, CC is a voltage amp). Write the *expressions* for the quantities shown below, in terms of the device parameters,  $r_{oc1}$ ,  $r_{oc2}$  and  $R_s$  and  $R_L$  as needed. (OK to use the simplified formulae). (6 points)



Parameter	Expression
$G_{m1}$	$g_{m1}$
$R_{in1}$	$\infty$
$R_{out1}$	$r_{o1} \parallel r_{oc1}$
$A_{v2}$	1
$R_{in2}$	$r_{\pi} + \beta_o (r_{o2} \parallel r_{oc2} \parallel R_L)$
$R_{out2}$	$\frac{1}{g_{m2}} + \frac{R_{out1}}{\beta_o}$

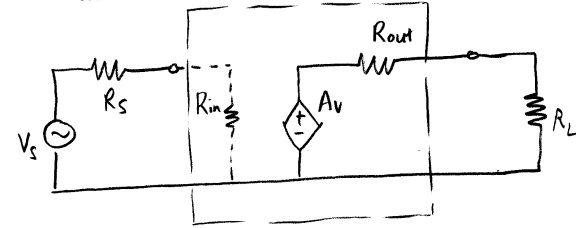c) Draw the overall voltage amp 2-port for the entire amp (i.e. draw one 2-port that represents the entire 2-stage amp), and derive *expressions* for the  $A_v$ ,  $R_{in}$ ,  $R_{out}$ , as well as  $v_{out}/v_s$  in terms of the device parameters, and  $r_{oc1}$ ,  $r_{oc2}$ ,  $R_s$  and  $R_L$ , as needed. (6 points)



$$A_v = -G_{m1} (R_{out1} \parallel R_{in2})$$

$$\frac{v_{out}}{v_s} = A_v \cdot \frac{R_L}{R_L + R_{out2}}$$

Parameter	Expression
$R_{in}$	$\infty$
$R_{out}$	$\frac{1}{g_{m2}} + \frac{R_{out1}}{\beta_o}$
$A_v$	$-g_{m1} (r_{o1} \parallel r_{oc1} \parallel [r_{\pi} + \beta_o (r_{o2} \parallel r_{oc2} \parallel R_L)])$
$v_{out}/v_s$	$-g_{m1} (r_{o1} \parallel r_{oc1} \parallel [r_{\pi} + \beta_o (r_{o2} \parallel r_{oc2} \parallel R_L)]) \cdot \frac{R_L}{R_L + \frac{1}{g_{m2}} + \frac{R_{out1}}{\beta_o}}$

d) Assume that  $V_{BIAS} = 1.5V$ , and that the minimum voltage across the current sources is  $0.5V$ . Find the maximum and minimum voltages at the drain of M1 and at the emitter of M2. Make sure you mention the limiting reason for each case (i.e. transistor X falls out of saturation, or current source Y hits its minimum voltage drop, etc.) (6 points)


- $V_{dmin} = V_{GS} - V_T = 1.5V - 1V = 0.5V \quad \therefore V_{emin} = 0.5V + 0.7V = 1.2V$
- $V_{dmax} \neq 4.5V$  because  $V_e = 4.5V + 0.7V = 5.2V > V_{DD}$   
 $V_{emax} = 4.5V \quad \therefore V_{dmax} = 4.5V - 0.7V = 3.8V$

Node	Min Voltage	Reason for Min Voltage	Max Voltage	Reason for Max Voltage
drain of M1	0.5V	$V_{psat}$ of M1	3.8V	Min voltage across $I_{SUP2}$ & $V_{EB}$ of M2
emitter of M2	1.2V	$V_{sat}$ of M1 & $V_{EB}$ of M2	4.5V	Min voltage across $I_{SUP2}$
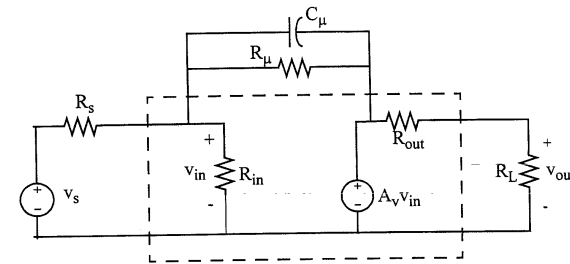
#### Problem 4/4 (24 points)

The following is the 2-port representation of a voltage amplifier, where the "Miller" elements  $C_\mu$  and  $R_\mu$  have been added as shown.


$A_v = -100$ ,  $R_s = 5k\Omega$ ,  $R_{in} = 5k\Omega$ ,  $R_{out} = 5k\Omega$ ,  $R_L = 5k\Omega$ ,  $C_\mu = 0.4pF$ ,  $R_\mu = 100k\Omega$ .



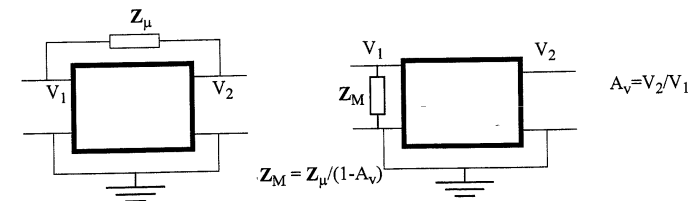
#### Miller Approximation Refresher:

Note that the Miller approximation applies to *any kind of complex impedance* connected between the nodes that exhibit voltage gain  $A_v$ . In general,  $Z_M = Z_\mu / (1 - A_v)$ . (Here a **bold** symbol indicates a complex number). As you know, for capacitors,  $Z_\mu = 1/j\omega C_\mu$ , so it turns out that  $C_M = C_\mu (1 - A_v)$ . Below you will be asked to apply the Miller approximation for capacitors, as well as for resistors....

Miller approximation refresher: these two circuits are almost equivalent.



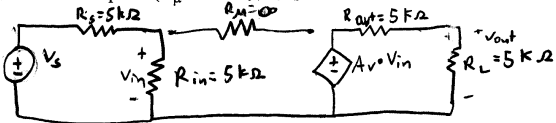a) For the voltage amplifier shown in the previous page, find the overall DC gain ( $v_{out}/v_s$ ) with no Miller resistor in place ( $R_\mu = \infty$ ). (5 points)



$$V_{out} = A_v \cdot V_{in} \cdot \frac{R_L}{R_L + R_{out}} \quad V_{in} = V_s \cdot \frac{R_{in}}{R_s + R_{in}}$$

$$V_{out} = A_v \cdot V_s \cdot \frac{R_{in}}{R_{in} + R_s} \cdot \frac{R_L}{R_L + R_{out}}$$

$$\frac{V_{out}}{V_s} = \frac{A_v \cdot R_{in} \cdot R_L}{(R_{in} + R_s)(R_L + R_{out})} = \frac{-100 \cdot 5k\Omega \cdot 5k\Omega}{(10k\Omega)(10k\Omega)} = -25$$

b) Find the overall DC gain expression and evaluate it when  $R_\mu = 100k\Omega$ . (5 points)

$$R_M = 100k\Omega \quad R_M = \frac{100k\Omega}{(1+100)} \approx 1k\Omega$$

$$R_{in} \parallel R_M = \frac{5k\Omega \cdot 1k\Omega}{6k\Omega} = 0.83k\Omega$$

$$\frac{V_{out}}{V_s} = \frac{A_v (R_{in} \parallel R_M) R_L}{(R_{in} \parallel R_M + R_s)(R_L + R_{out})} = \frac{-100 \cdot (0.83k\Omega)(5k\Omega)}{5.83k\Omega \cdot 10k\Omega} = -7.143$$

	Expression	Value for $R_\mu = 100k\Omega$
$v_{out}/v_s$	$\frac{A_v \cdot (R_{in} \parallel R_M) \cdot R_L}{(R_{in} \parallel R_M + R_s)(R_L + R_{out})} \quad R_M = R_\mu / (1 - A_v)$	-7.143

c) Find the  $\omega_{3db}$  of  $|v_{out}/v_s|$  when  $R_\mu$  is infinity and when  $R_\mu$  is  $100k\Omega$ . Hint: apply the Miller approximation to the resistor and the capacitor separately. It is not necessary to solve this considering the complex impedance of the resistor and capacitor taken together. (5 points)

$$C_M = 0.4 \text{ pF} \quad C_M = 101 \cdot C_\mu \approx 40 \text{ pF}$$

for  $R_M = \infty$

$$R = R_s \parallel R_{in} = 2.5k\Omega$$

$$R \cdot C_M = 10^{-7} \text{ sec} \Rightarrow \omega_{3db} = \frac{1}{10^{-7} \text{ sec}} = 10 \text{ Mrad/sec}$$

for  $R_M = 100k\Omega \quad R_M = 1k\Omega$

$$R = R_s \parallel R_{in} \parallel R_M = \frac{2.5k\Omega \cdot 1k\Omega}{3.5k\Omega} = 0.714$$

$$R \cdot C_M = 2.86 \times 10^{-8} \text{ sec} \Rightarrow \omega_{3db} = \frac{1}{2.86 \times 10^{-8} \text{ sec}} = 35 \frac{\text{Mrad}}{\text{sec}}$$

	Expression	Value in Mrad/sec
$\omega_{3db}$ for $R_\mu = \infty$	$\frac{1}{(R_s \parallel R_{in}) \cdot C_M} \quad C_M = C_\mu(1 - A_v)$ $R_M = R_\mu(1 - A_v)$	10
$\omega_{3db}$ for $R_\mu = 100k\Omega$	$\frac{1}{(R_s \parallel R_{in} \parallel R_M) C_M}$	35


d) Draw Bode plots on the same graph for  $|v_{out}/v_s|$  when  $R_{\mu}$  infinity and  $R_{\mu} = 100k\Omega$ . (5 points)

$$20 \cdot \log \left| \frac{v_{out}}{v_s} \right|_{dc, \infty} = 28 \text{ dB}$$

for  $R_{\mu} = \infty$

$$20 \cdot \log \left| \frac{v_{out}}{v_s} \right|_{dc, 100k} \approx 17 \text{ dB}$$

for  $R_{\mu} = 100k\Omega$

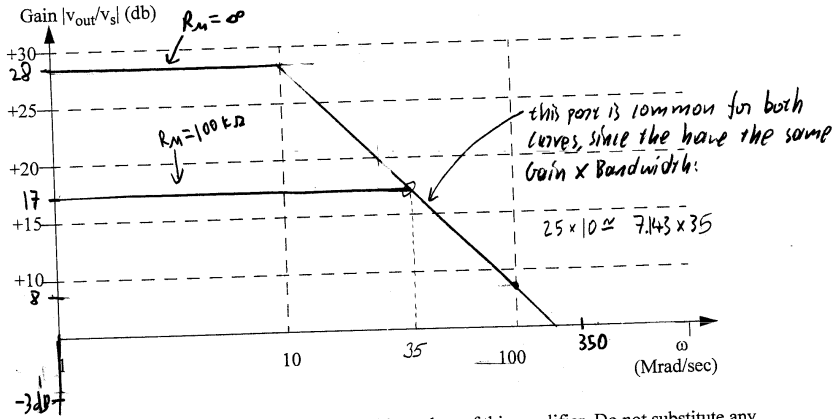

e) Derive an expression for the Gain X Bandwidth product of this amplifier. Do not substitute any values. Simplify this expression assuming that  $|A_v| \gg 1$ ,  $R_{\mu}/|A_v| \ll R_s$  and  $R_{\mu}/|A_v| \ll R_{in}$ . (4 points)

$$\text{Gain} = \frac{R_{in} \parallel (R_{\mu} / (1 - A_v))}{R_s + R_{in} \parallel (R_{\mu} / (1 - A_v))} \cdot \frac{A_v \cdot R_L}{R_{out} + R_L}$$

$$BW = \frac{1}{C_M \cdot \left( \frac{R_{\mu}}{|A_v|} \parallel R_s \parallel R_{in} \right)}$$

$$BW = \frac{1}{C_M \cdot (1 - A_v) \left( \frac{R_{\mu}}{|A_v|} \parallel R_s \parallel R_{in} \right)}$$

now apply assumptions:  $R_{in} \parallel \frac{R_{\mu}}{(1 - A_v)} \approx \frac{R_{\mu}}{A_v}$ ;  $1 - A_v \approx -A_v$

$$\text{Gain} = \frac{-R_{\mu} / A_v}{R_s} \cdot \frac{A_v \cdot R_L}{R_L + R_{out}}$$

$$BW = \frac{A_v}{A_v \cdot C_M \cdot R_{\mu}} = \frac{1}{C_M R_{\mu}}$$

$$\text{Gain} = \frac{-R_{\mu} \cdot R_L}{R_s (R_L + R_{out})}$$

$$\text{Gain} \cdot BW = \frac{-R_{\mu} \cdot R_L}{R_s (R_L + R_{out})} \cdot \frac{1}{C_M R_{\mu}}$$

~ That's All Folks! ~

$$= \frac{-R_L}{R_s (R_L + R_{out}) C_M}$$