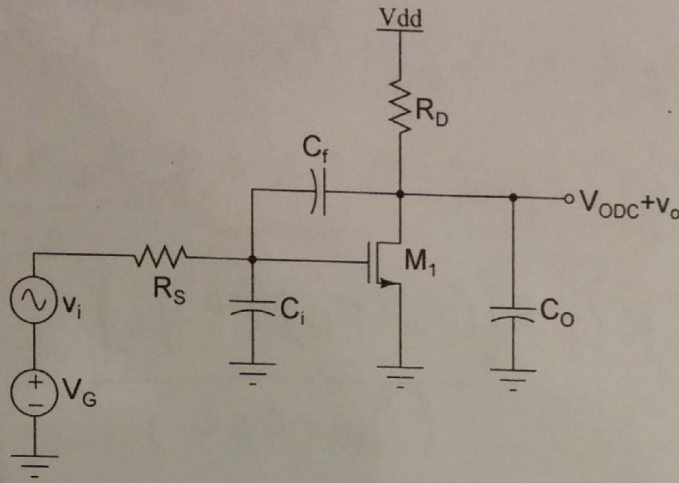


1. (60 points) **Frequency Response.** For the circuit shown below, assume  $M_1$  operates in saturation and has the following defining parameters:  $W, L, \mu_n, C_{OX}, V_{TH}$  and  $\lambda$ .




(a) (8 points) Express the small-signal parameters  $g_m$  and  $r_o$  for  $M_1$  for the DC bias condition  $V_G > V_{TH}$  in terms of the defining parameters and  $V_G$ .

$$I_D = \mu C_{OX} \frac{W}{L} (V_G - V_{TH})^2 (1 + \lambda V_{DS}) \rightarrow \textcircled{1}$$

$$g_m = \frac{2I_D}{V_G - V_{TH}} \rightarrow \textcircled{2}, \quad r_o = \frac{1}{\lambda I_D} \rightarrow \textcircled{3}$$

Substitute for  $I_D$  in  $\textcircled{2}$  and  $\textcircled{3}$

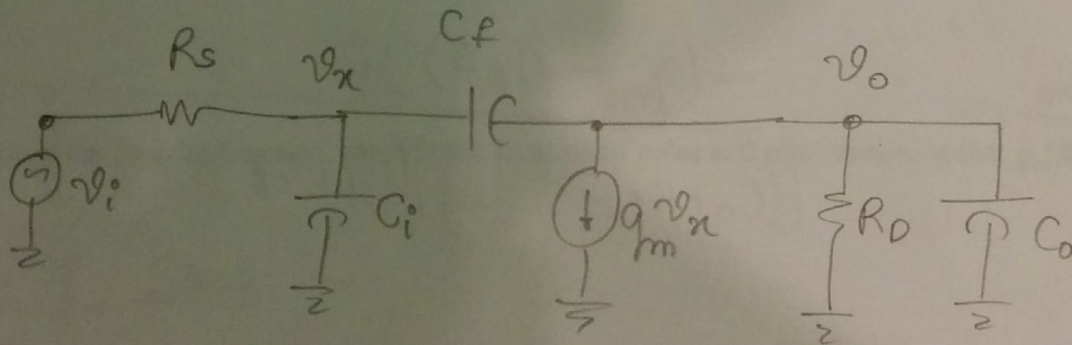(b) (8 points) Draw the small signal model for the circuit shown above.





Transfer function

$$R_L = 1/g_L \quad G_s = 1/R_s \quad s = j\omega$$

KCL at node  $V_o$

$$(v_o - v_n) C_f s + v_o g_L + v_o C_o s + g_m v_n = 0$$

$$v_o (C_o s + g_L + C_f s) - v_n C_f s + g_m v_n = 0$$

$$v_n = \frac{-v_o [(C_o + C_f) s + g_L]}{(g_m - C_f s)}$$

KCL at node  $V_n$

$$(v_n - v_i) G_s + v_n C_i s + (v_n - v_o) C_f s = 0$$

$$v_n [G_s + s(C_f + C_i)] - C_f s v_o = v_i G_s$$

$$-\left[ \frac{(g_s + s(C_f + C_i))(g_L + s(C_f + C_o))}{g_m - C_f s} + C_f s \right] v_o = v_i G_s$$

$$\frac{v_o}{v_i} = \frac{-(g_m - C_f s) G_i}{[(C_o + C_f) s + g_L] [(C_i + C_f) s + G_i] + C_f s (g_m - C_f s)}$$



- (c) (16 points) Determine the small signal transfer function  $H(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)}$ . Use only the capacitors explicitly shown. Assume  $r_o \gg R_L$  for simplicity.

$$\frac{v_o(j\omega)}{v_i(j\omega)} = \frac{-(g_m - C_f j\omega) g_s}{[(C_o + C_f)j\omega + g_L] [(C_i + C_f)j\omega + g_s] - j\omega C_f (g_m - C_f s)}$$

$$g_s = 1/R_s$$

$$g_L = 1/R_L$$

(see previous page)

- (d) (8 points) From the transfer function, identify the location of poles and zeros assuming that  $g_m R_L \gg 1$ .

Location of zero

$$g_m - j\omega C_f = 0$$

$$\omega_z = \frac{g_m}{C_f}$$



## locating the poles

Consider only denominator.

$$\Rightarrow [(C_o + C_f)s + g_L] [(C_i + C_f)s + g_S] + C_f s (g_m - C_f s)$$

$$\Rightarrow (C_o + C_f)(C_i + C_f)s^2 + [g_S(C_o + C_f) + g_L(C_i + C_f) + g_m C_f]s + g_S g_L - C_f^2 s^2$$

Converting back to  $R_L$  and  $R_S$

$$\Rightarrow R_S R_L (C_o C_i + C_o C_f + C_i C_f) s^2 + s [R_L(C_o + C_f) + R_S(C_i + C_f) + C_f g_m R_L R_S] + 1$$

$$\Rightarrow R_S R_L (C_o C_i + C_o C_f + C_i C_f) s^2 + s [R_L(C_o + C_f) + R_S(C_i + C_f(1 + g_m R_L))] + 1$$

Denominator of the form

$$s^2/p_1 p_2 + s \left[ \frac{1}{p_1} + \frac{1}{p_2} \right] + 1$$

Since  $g_m R_L \gg 1$   $\frac{1}{p_1} \approx R_S (C_i + C_f(1 + g_m R_L))$

$$p_1 = \frac{1}{R_S (C_i + C_f(1 + g_m R_L))}$$

← Same result as when  $C_f$  is split using Miller theorem.

Finding  $p_2$  : see last page.



- (e) (8 points) We know that at low frequencies, the output is 180° out of phase with respect to input. As the input frequency increases, there is additional phase added due to the pole(s) and zero(s). Now, what is the phase of  $H(j\omega) = v_o/v_i$  at very high frequencies? (hint: The zero also does something interesting)

We have  $\frac{(1 - s/z_1)}{(1 + s/p_1)(1 + s/p_2)}$  ( $s = j\omega$ )

net phase added

$$\angle v_o/v_i = -\tan^{-1}\left(\frac{\omega}{z_1}\right) - \tan^{-1}\left(\frac{\omega}{p_1}\right) - \tan^{-1}\left(\frac{\omega}{p_2}\right)$$

$$\angle v_o/v_i \rightarrow -270^\circ \text{ as } \omega \rightarrow \infty$$

- (f) (6 points) You will learn in later courses (if you still want to stay in EE ☺) that this kind of a zero is actually a bad thing. One way to get rid of it is with the circuit shown below. From the transfer function you obtained above, find only the new location of zero including  $R_F$  (hint: Just modify  $\frac{1}{j\omega C_F}$  to  $\frac{1}{j\omega C_F} + R_F$ )

$$\frac{1}{j\omega C_F} \rightarrow \frac{1}{j\omega C_F} + R_F \Rightarrow j\omega C_F \rightarrow \frac{j\omega C_F}{1 + R_F j\omega C_F}$$

Zero

$$g_m - \frac{j\omega C_F}{1 + R_F j\omega C_F} = 0 \Rightarrow g_m + (g_m R_F - 1)j\omega C_F = 0$$


$$\omega_z = \frac{g_m}{(1 - g_m R_F) C_F}$$

- (g) (6 points) Find the value of  $R_F$  that will cancel the bad zero completely.

To get rid of zero or push it to infinity


$$1 - g_m R_F = 0$$

$$R_F = \frac{1}{g_m}$$

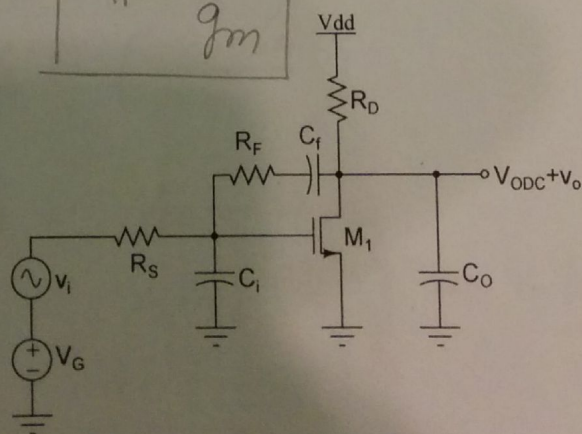



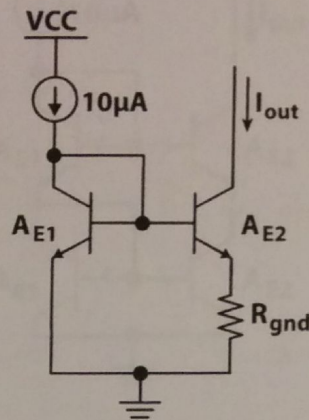2. (30 points). DC bias calculations. For the circuit shown below, assume  $R_{gnd}=0$ ,  $V_A=\infty$  and  $\beta$  is large enough to neglect the base current.



- (a) (6 points) Find the relation between  $A_{E1}$  and  $A_{E2}$ , so that  $I_{out}=1\text{mA}$ .

$\beta$  is large

$$\frac{A_{E2}}{A_{E1}} = \frac{1\text{mA}}{10\mu\text{A}} = 100 \Rightarrow \boxed{A_{E2} = 100A_{E1}}$$

- (b) (10 points) With your sizing in Part (a), you discover that the current  $I_{out}$  is only 90% of 1mA. After a lot of debugging, you discover that the ground connection of the mirror transistor is improper and has a resistance  $R_{gnd}$  as shown. Find the value of  $R_{gnd}$ .

$$I_{out} = 900\mu\text{A}$$

$\beta$  is large


$$V_{BE1} = V_T \ln\left(\frac{10\mu\text{A}}{I_S}\right)$$

$$V_{BE2} = V_T \ln\left(\frac{900\mu\text{A}}{100I_S}\right)$$

$$\begin{aligned} 900\mu\text{A} \times R_{gnd} &= V_{BE1} - V_{BE2} \\ &= V_T \ln\left(\frac{10\mu\text{A}}{I_S}\right) - V_T \ln\left(\frac{900\mu\text{A}}{100I_S}\right) \\ &= V_T \ln\left(\frac{1000}{900}\right) \end{aligned}$$
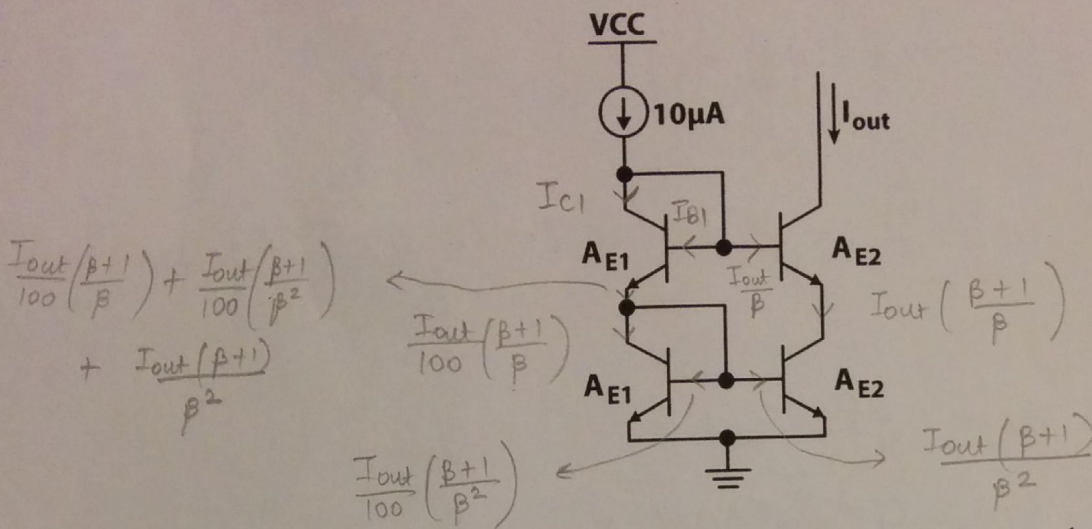
$$\Rightarrow \boxed{R_{gnd} = 3.04\Omega}$$





(c) (14 points) In order to boost the output impedance, we now utilize a cascode current source. With your sizing in (a) for  $A_{E2}$ ,  $V_A = \infty$  and  $\beta = 100$ , find the value of  $I_{out}$ . Note that  $\beta$  is finite. (Hint: Express the emitter, base and collector currents of each transistor in terms of  $I_{out}$ ).

$$A_{E2} = 100 A_{E1}, \quad \beta = 100$$

Mark the currents

$$I_{C1} = \left( \frac{\beta}{\beta+1} \right) \left[ \frac{I_{out}}{100} \left( \frac{\beta+1}{\beta} \right) + \frac{101 I_{out}}{100} \left( \frac{\beta+1}{\beta^2} \right) \right]$$

$$= \frac{I_{out}}{100} + \frac{101 I_{out}}{100\beta}$$

$$I_{B1} = \frac{I_{out}}{100\beta} + \frac{101 I_{out}}{100\beta^2}$$

$$I_{C1} + I_{B1} + \frac{I_{out}}{\beta} = 10 \mu A$$

$$\Rightarrow \frac{I_{out}}{100} \left( \frac{\beta+1}{\beta} \right) + \frac{101 I_{out}}{100} \frac{(\beta+1)}{\beta^2} + \frac{I_{out}}{\beta} = 10 \mu A$$

With  $\beta = 100$ ,

$$I_{out} \left[ \frac{101}{100^2} + \frac{101^2}{100^3} + \frac{1}{100} \right] = 10 \mu A$$

$$\Rightarrow \boxed{I_{out} = 330 \mu A}$$



Question 1d

$$\frac{1}{P_1 P_2} = R_L R_S (C_0 C_i + C_0 C_f + C_i C_f)$$

$$\frac{1}{P_1} \frac{1}{P_2} = R_S (C_i + C_f (1 + g_m R_L))$$

$$\frac{R_S (C_i + C_f (1 + g_m R_L))}{P_2} = R_L R_S (C_0 C_i + C_0 C_f + C_i C_f)$$

$$P_2 = \frac{C_i + C_f (1 + g_m R_L)}{R_L (C_0 C_i + C_0 C_f + C_i C_f)}$$

$$P_2 = \frac{1}{R_L \left( \frac{C_0 C_i + C_0 C_f + C_i C_f}{C_i + C_f (1 + g_m R_L)} \right)}$$

If we assume  $g_m R_L \gg 1$

$$P_2 = \frac{g_m R_L C_f}{R_L (C_0 (C_i + C_f) + C_i C_f)}$$

$$P_2 = \frac{g_m C_f}{(C_0 (C_i + C_f) + C_i C_f)}$$

∴