

UNIVERSITY OF CALIFORNIA AT BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Science
R. Brodersen

EE140

Midterm Exam

Oct. 15, 2003

Name: SOLUTIONS SID:

Use the following parameters:

$$V_{t0(\text{NMOS})} = V_{t0(\text{PMOS})} = 0.4\text{v}$$

$$k'_{(\text{NMOS})} = k'_{(\text{PMOS})} = 10\text{mA/V}^2 = 10^{-2}\text{ A/V}^2$$

$$F_f = 0.3\text{v}; \gamma = 1\text{V}^{1/2}; \lambda = 0.02$$

Assume all W/L = 10

(10pts) 1. 1.27 V.

(10pts) 4. 4.6 k Ω

(5pts) 2a. 5 V.

(10pts) 5. 1.1 k Ω

(5pts) 2b. 4 V.

(5pts) 6a. 3.3×10^{-3} s.

(5pts) 2c. -4 V.

(5pts) 6b. 50 Ω

(5pts) 3a. -9.1×10^{-3} s.

(5pts) 6c. .16


(5pts) 3b. 550 μ A Ω

(10pts) 7a. .5 mA

(5pts) 3c. -500

(10pts) 7b. 5×10^5

1.

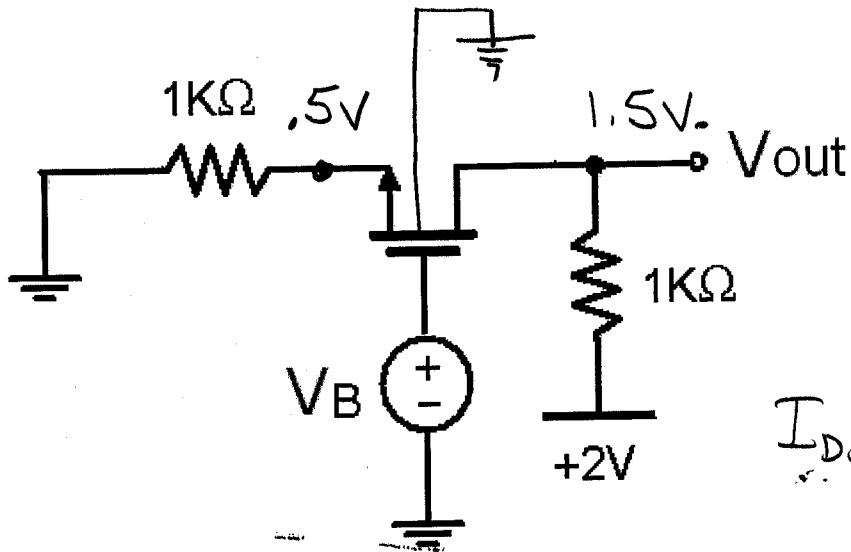

$$I_{DS} = \frac{0.5V}{1k\Omega} = 0.5mA$$

What is V_B so that $V_{out} = 1.5V$? $V_B = 1.27V$

SAME CURRENT FOR BOTH RESISTORS
THEREFORE SAME VOLTAGE DROP = .5V.

$$V_{SB} = .5 \quad V_T = V_{TO} + \sqrt{[2\phi_f + V_{SB}]^2 - (2\phi_f)^2}$$


$$= .4 + \sqrt{(.6 + .5)^2 - .6^2}$$

$$= .67$$

$$V_{DSAT} = \left(\frac{2I_{DS}}{k'nW_L} \right)^{1/2} = \left(\frac{2 \times 0.5 \times 10^{-3}}{10^{-2} \times 1^2 \times 10} \right)^{1/2} = .1$$

$$V_B = V_T + V_{DSAT} + .5 = .67 + .1 + .5 = 1.27$$

2.

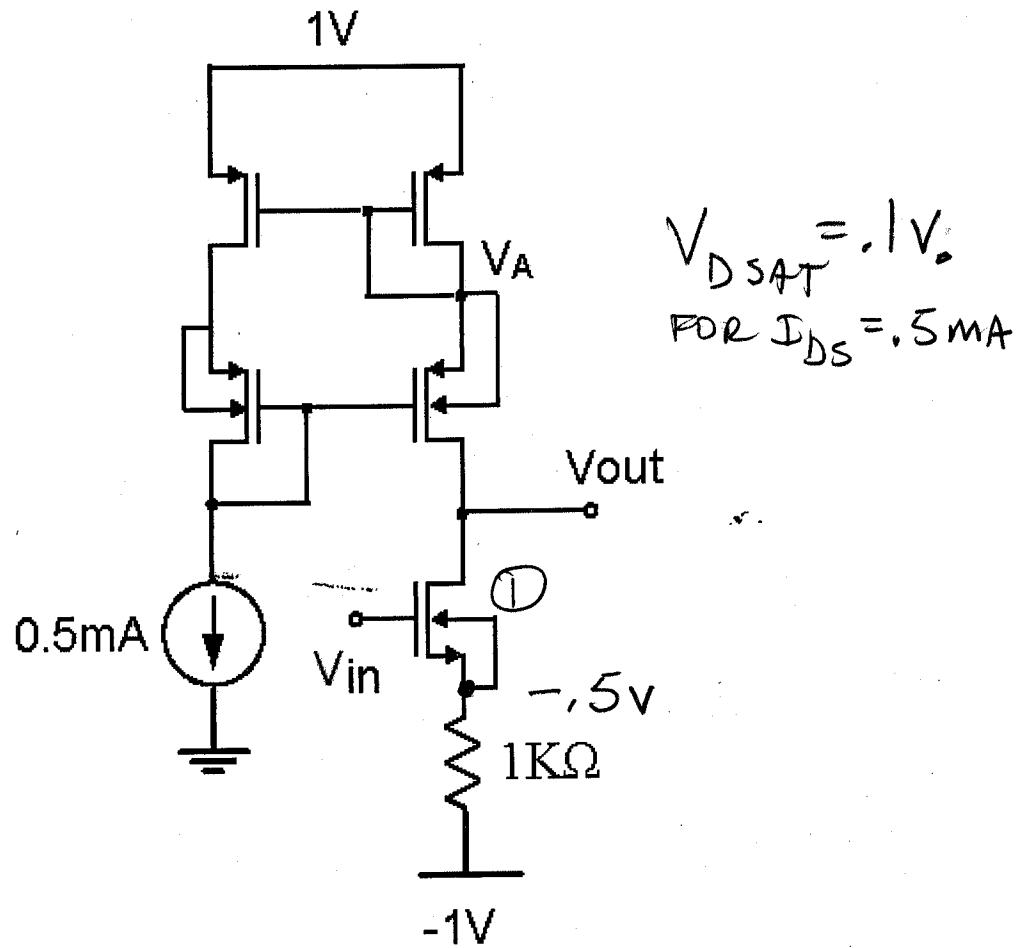

a. What is the voltage at V_A ?

$$V_A = | -V_T - V_{DSAT} |$$

$$= | -1.4 - .1 | = .5V$$


b. What is the maximum swing in the positive direction at V_{out} ?

$$V_{MAX, POS} = V_A - V_{DSAT} = .4V$$

c. What is the most negative swing at V_{out} ?

$$V_{MAX, NEG} = V_{S,1} + V_{DSAT} = -.5 + .1 = -.4V$$

3.

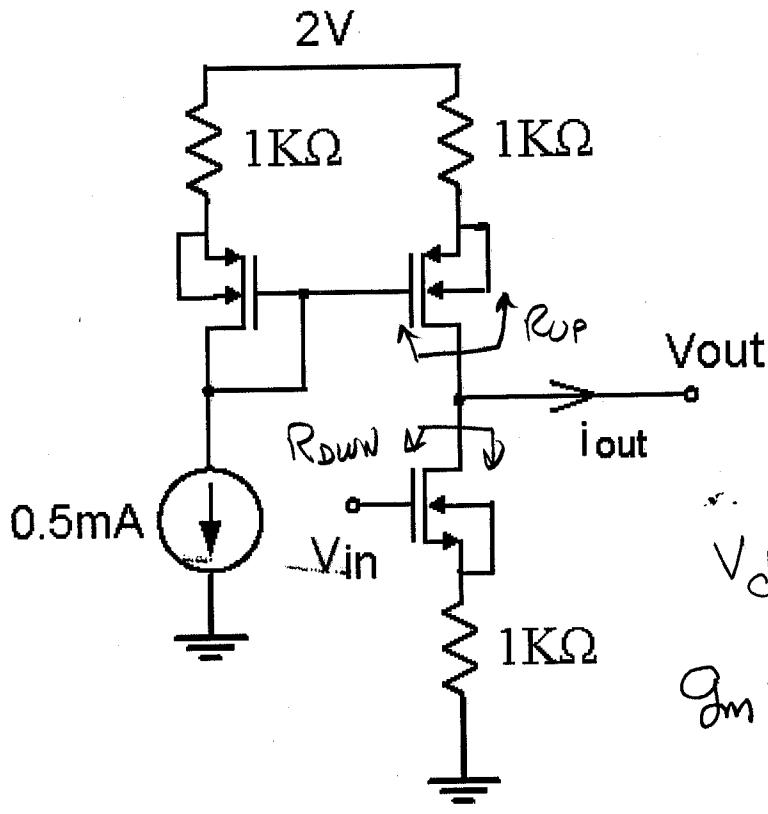

$$r_o = \frac{1}{2g_m} = 10\Omega$$

$$V_{dsAT} = 1\text{V}$$

$$g_m = 2 \frac{I_{DS}}{V_{dsAT}} = 10^{-2} \text{ s.}$$

a. What is $G_m = i_{out} / v_{in}$?

$$g_m = \frac{-g_m}{1 + g_m(1\text{k}\Omega)} = \frac{-10^{-2}}{1 + 10^{-2}} = -9.1 \times 10^{-3}$$

b. What is R_{out} ?

$$R_{UP} = r_o (1 + g_m (1\text{k}\Omega)) = 10^5 \times 10^{-2} \times 10^3 = 1.1 \times 10^6 \Omega$$


$$R_{DOWN} = S_{AME} = 1.1 \times 10^6$$

$$R_{OUT} = 550 \text{ k}\Omega$$

c. What is A_v ?

$$A_v = G_m R_{OUT} = 9.1 \times 10^{-3} \times 5.5 \times 10^5 = -500$$

4.

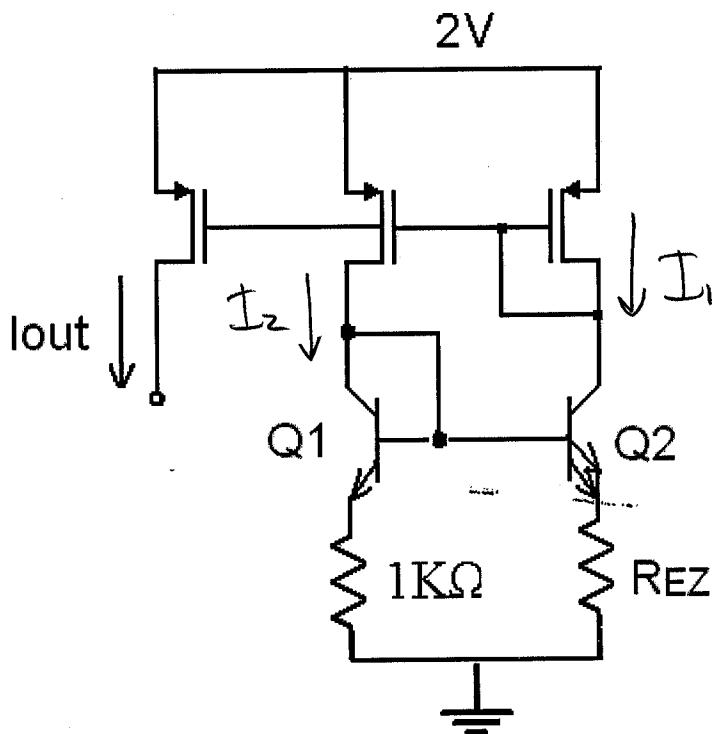

For the bipolar:

$$A_E = 1 \text{ for } Q1$$

$$A_E = 4 \text{ for } Q2$$

$$V_{th} = 26mV$$

$$I_1 = I_{out} = I_2$$

BY CURRENT SOURCE CONNECTION

$$I_{s2} = 4 I_{s1}$$

What is the value of R_{EZ} that sets $I_{out} = 10\mu A$?

$$R_{EZ} = 4.6k\Omega$$


$$V_{BE1} + I_1 R_{EZ} = V_{BE2} + I_2 R_{EZ}$$

$$V_{BE1} = V_{TH} \ln \frac{I_1}{I_{s1}}$$

$$V_{BE2} = V_{TH} \ln \frac{I_2}{I_{s2}} = V_{TH} \ln \frac{I_1}{4I_{s1}}$$

$$R_{EZ} = 1k\Omega + \frac{V_{TH} \ln 4}{10\mu A} = 4.6k$$

5.

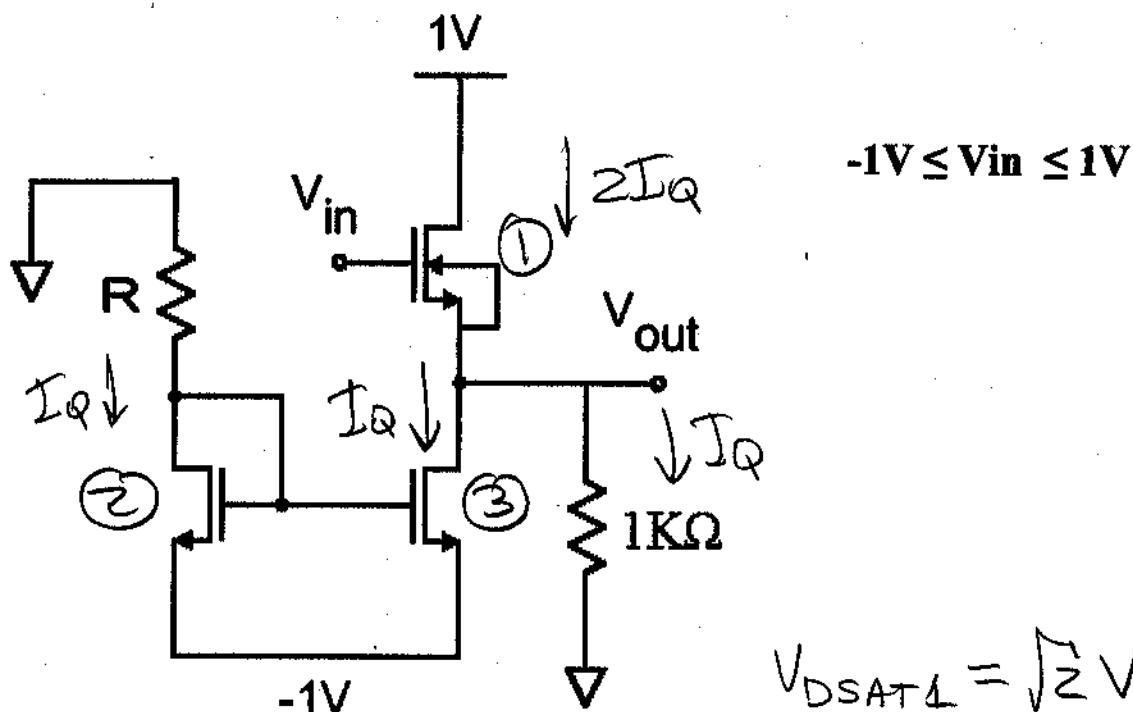

$$V_{DSAT4} = \sqrt{2} V_{DSAT3}$$

What is the value of R which gives the maximum efficiency?

$$R =$$

(Hint: Find an expression for R before you plug in numbers)

V_{MAX+} is $1 - V_{TO} - V_{DSAT1}$ which is LESS THAN $V_{MAX-} = 1 - V_{DSAT3}$ ($V_{DSAT1} > V_{DSAT3}$)

so $I_Q = \frac{1 - V_{TO} - V_{DSAT1}}{1k}$

ITERATING: $\begin{array}{|c|c|} \hline I_Q^{IN} & I_Q^{OUT} \\ \hline 1mA & .4mA \\ .4mA & .47mA \\ .47mA & .46mA \\ \hline \end{array}$


$$I_Q = \left[.6 - \left(\frac{2 \cdot 2I_Q}{1k/W_L} \right)^{1/2} \right] 10^{-3}$$

$$= \left[.6 - [40I_Q]^{1/2} \right] 10^{-3}$$

$$R = \frac{1 - V_{TO} - (20I_Q)^{1/2}}{0.46 \times 10^{-3}} \quad | = 1.1k\Omega$$

$$I_Q = .46 \times 10^{-3}$$

6.

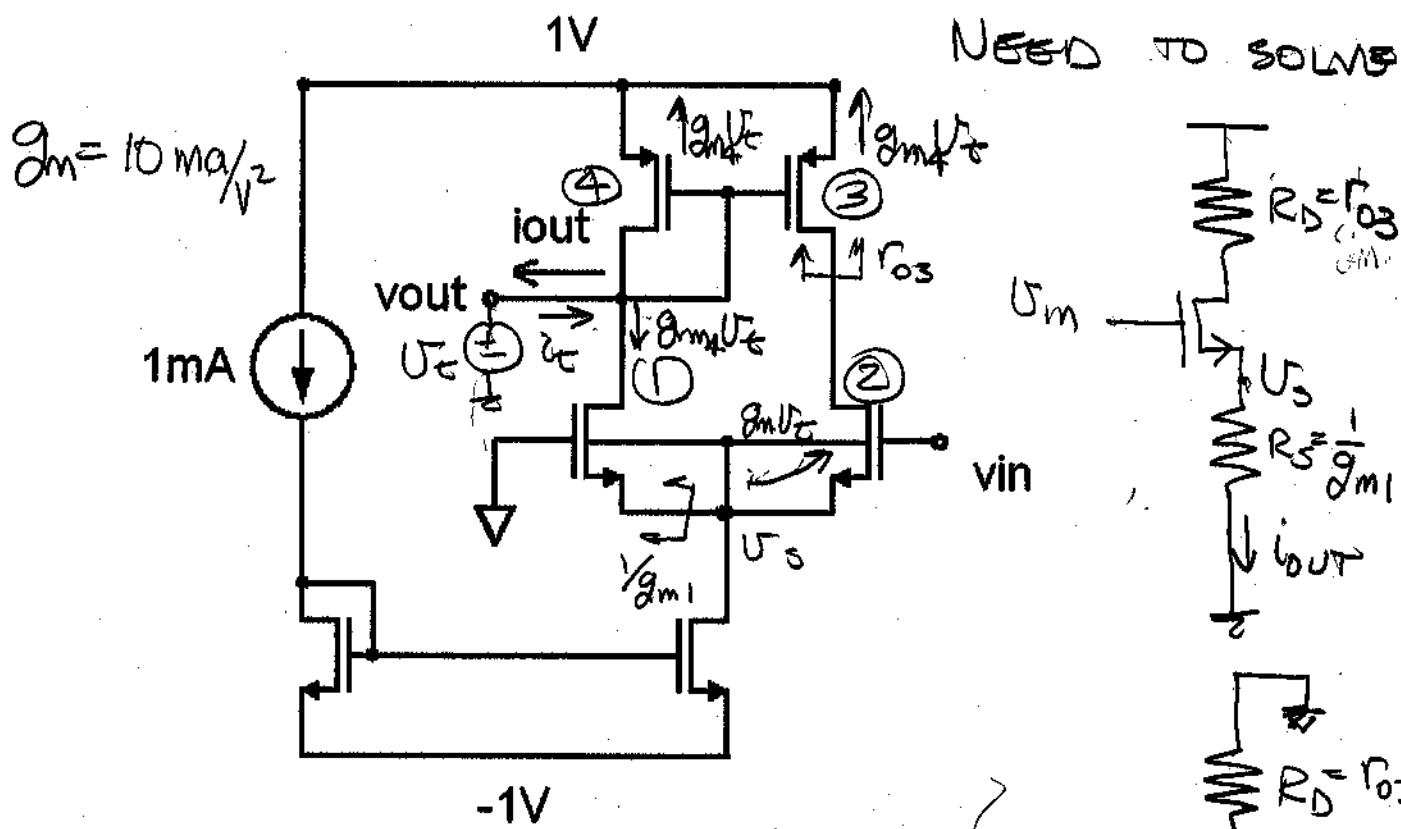

a. What is G_m ? $i_{out} = g_m (U_{in} - U_S) \sqrt{\frac{r_{o2}}{r_{o2} + R_D + R_S}}$

$$U_S = i_{out} R_S$$

$$i_{out} = g_{m2} U_m \left(\frac{r_{o2}}{r_{o2} + R_D + R_S} \right) - g_{m2} R_S \left(\frac{r_{o2}}{r_{o2} + R_D + R_S} \right) i_{out}$$

$$G_m = \frac{g_{m2}}{3} = 3.3 \text{ mA/V}^2$$



b. What is R_{out} ?

$$i_t = 2g_{m4} U_t + \frac{U_t}{r_{o1}} \approx 2g_{m4} U_t$$


$$R_{out} = \frac{1}{2g_{m4}} = 50\Omega$$

c. What is A_v ?

$$A_v = G_m R_{out} = \frac{1}{6}$$

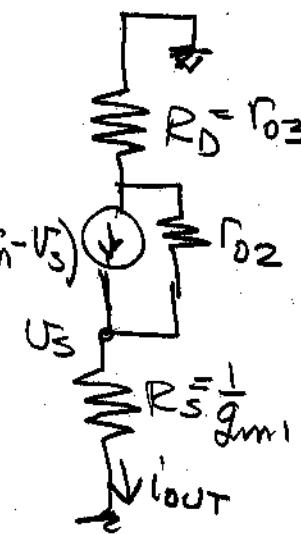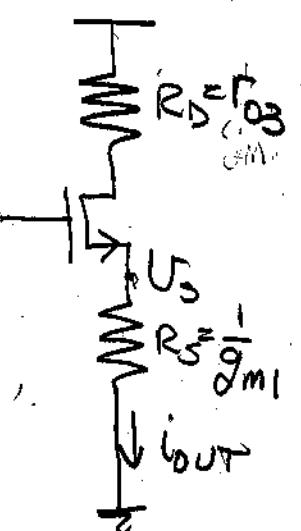

7.

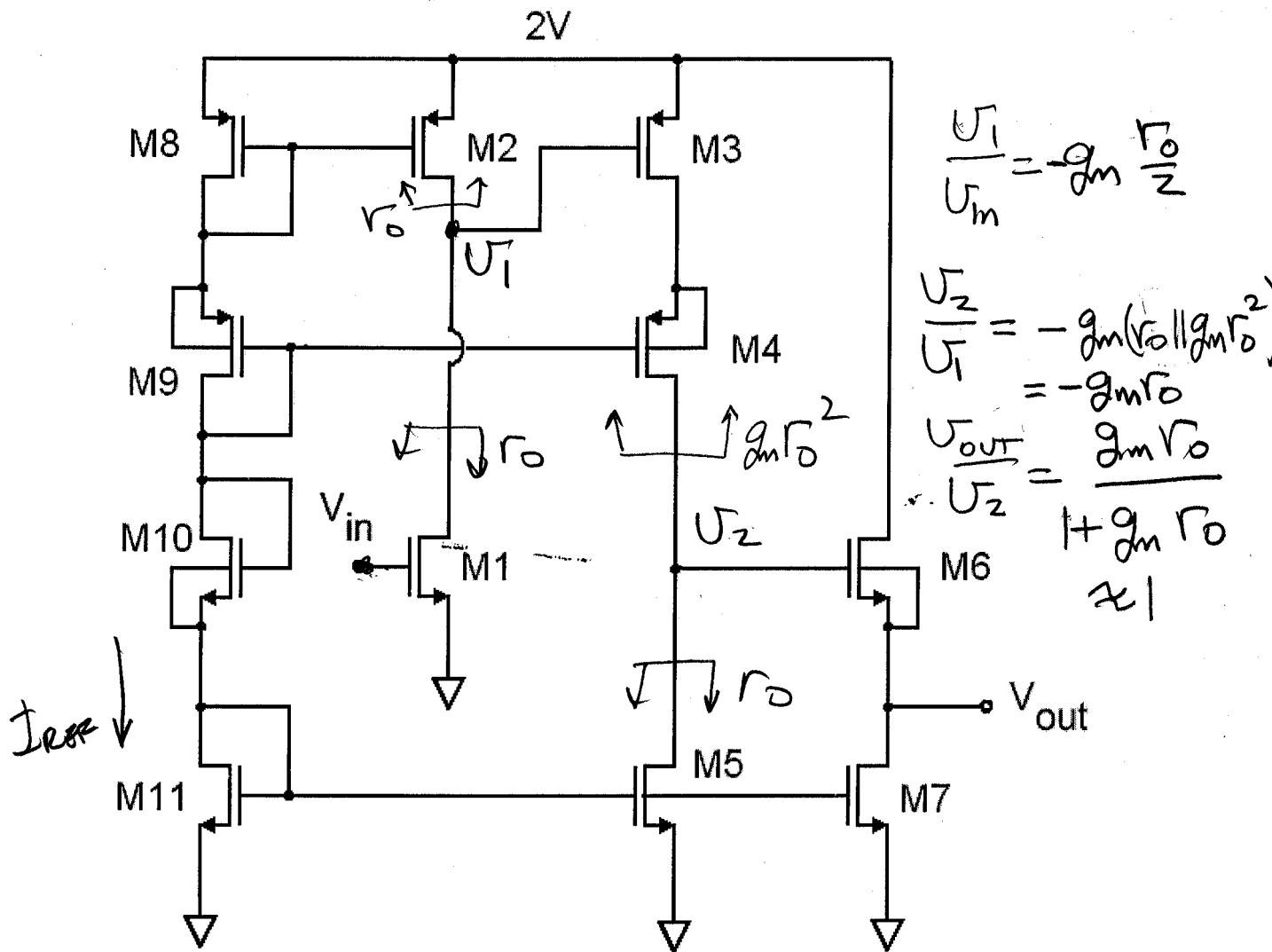

a. What is the I_{DS} of transistor M6? $Z_V = 4(V_T + V_{DSAT})$

$$V_{DSAT} = .5 - .4 = .1$$

$$I_{DS} = .5 \text{ mA}$$

b. Assume that $g_m = 0.01$, $r_o = 100\text{k}\Omega$, $g_{mb}=0$, for all the transistors.
What is V_{out}/V_{in} ?

$$\frac{V_{out}}{V_{in}} = \frac{(g_m R_o)^3}{Z} = \frac{10^6}{Z} = 5 \times 10^5$$