

NAME

SOLUTIONS

FALL 1996

$$k_n = k_p = 10^{-4} \text{ A/V}^2$$

$$\gamma_n = \gamma_p = 0$$

$$\lambda_n = \lambda_p = .01$$

$$V_{Tn} = V_{Tp} = 1 \text{ V}$$

$$a) \frac{3.6}{6.2} \text{ VOLTS}$$

$$b) \frac{1.7}{3.7} \text{ VOLTS}$$

$$2) a) \frac{1.7}{3.7} \text{ VOLTS}$$

$$V_{MAX} \frac{3.7}{6} \text{ VOLTS}$$

$$b) \frac{10^6}{100}$$

$$3) a) \frac{100}{100}$$

$$(V/V)_{M2} \frac{100}{100}$$

$$b) \frac{V_{MIN}}{V_{MAX}} \frac{-2.9}{+2.9}$$

$$+2.9$$

$$4) R \frac{600 \Omega}{1000 \text{ pf}}$$

$$5) C_c \frac{1000 \text{ pf}}{25 \mu \text{ A}}$$

$$6) I_{REF} \frac{25 \mu \text{ A}}{97 \text{ k RAD/SEC}}$$

$$7) a) \frac{97 \text{ k RAD/SEC}}{9.4 \text{ M RAD/SEC}}$$

$$b) \frac{9.4 \text{ M RAD/SEC}}{9.4 \text{ M RAD/SEC}}$$

$$8) a) \frac{5 \text{ KUN} - 5 \text{ UN}}{710}$$

$$b) \frac{V_{out}}{V_{in}} \frac{710}{1.5 \Omega}$$

$$c) R_{in} \frac{1.5 \Omega}{1.5 \Omega}$$

$$C_{gd} = 1 \text{ ff}$$

$$C_{db} = 10 \text{ ff}$$

$$C_{gs} = 100 \text{ ff}$$

$$C_{gb} = 5 \text{ ff}$$


$$C_{sb} = 10 \text{ ff}$$

$$9) \frac{4.0 \text{ RAD/SEC}}{20 \text{ VOLTS/\mu SEC}}$$

$$10) a) \frac{20 \text{ VOLTS/\mu SEC}}{90 \text{ DEGREES}}$$

$$b) \frac{90 \text{ DEGREES}}{90 \text{ DEGREES}}$$

1)

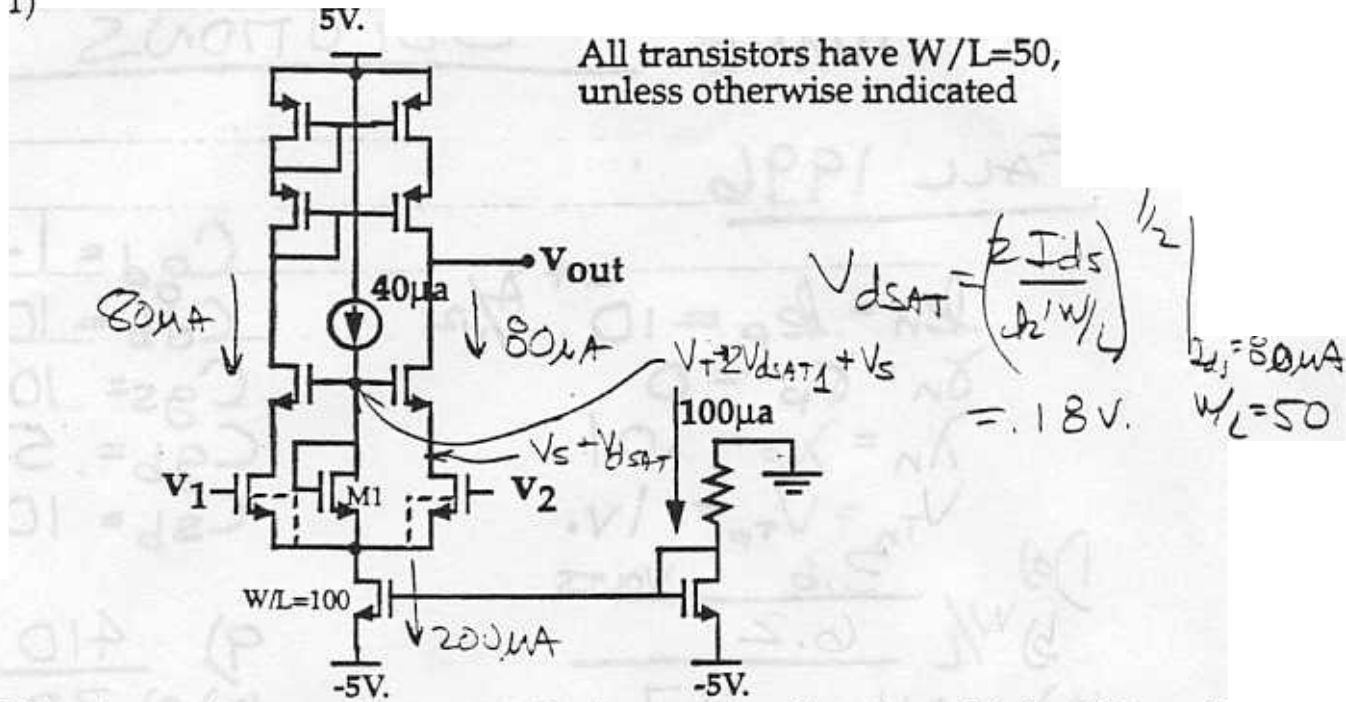

a) What is maximum value at v_{out} in the positive direction which still has all transistors in saturation?

$$V_o = 5 - (V_T + 2V_{dsAT}) = 3.64$$

b) Choose the W/L of $M1$ to maximize the swing at v_{out} in the negative direction which has all transistors in saturation?


$$V_T + V_{dsAT, M1} = V_T + 2V_{dsAT}$$

$$V_{dsAT, M1} = 0.36V$$

$$\left(\frac{2 \cdot 40 \times 10^{-6}}{10^{-4} (W/L)_1} \right)^{1/2} = 0.36$$

$$\underline{W/L = 6.2}$$

2)

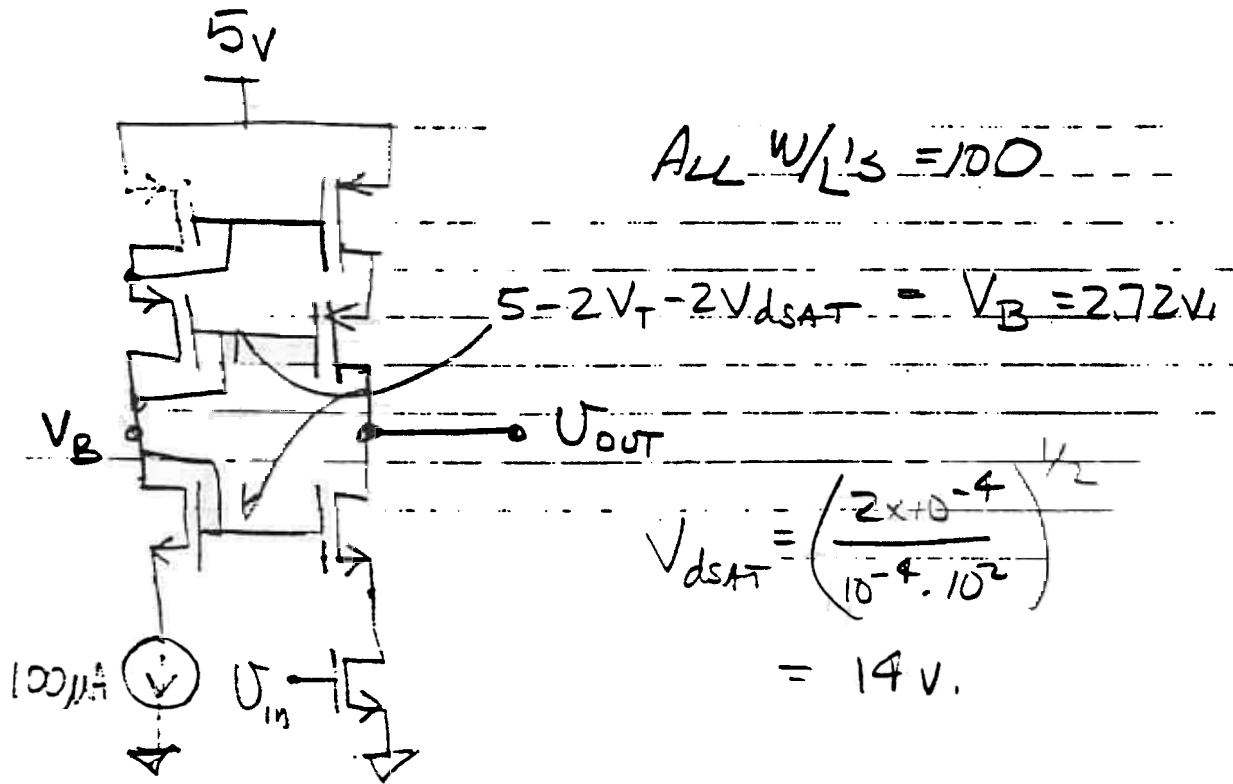

WHAT IS THE RANGE OF DC VOLTAGES AT U_{OUT} OVER WHICH THE GAIN IS MAXIMUM?

$V_{MIN} \underline{1.72} \quad V_{MAX} \underline{3.72}$

$V_{MIN} = V_B - V_T = 1.72V$


$V_{MAX} = V_B + V_T = 3.72V.$

b) WHAT IS THAT MAXIMUM GAIN? 10^6

$R_{out} = \frac{r_o(g_m r_o)}{2}$

$A_v = g_m R_{out} = \frac{(g_m r_o)^2}{2} = \frac{2 \mu^2 W/L I_{DS}}{2 \lambda^2 I_{DS}}$

$= 10^6$

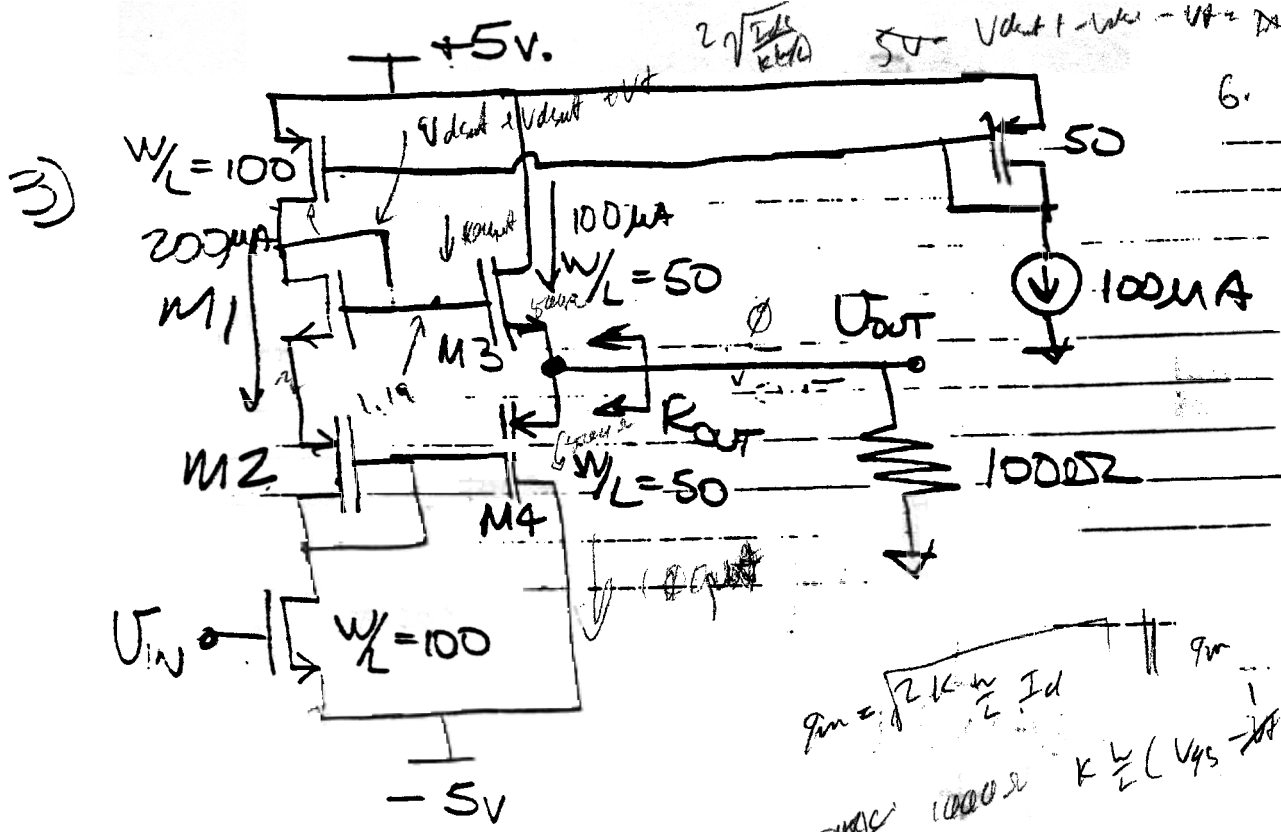

a) Assume V_{in} is set so the output is at 0 volts, what are the W/L 's of $M1$ & $M2$ so that the output resistance, $R_{out} = 500\Omega$?

$$R_{out} = \frac{1}{2g_m} = 500\Omega$$

$$g_m \cdot 1000\Omega = (2k'(W/L)I_{ds3})^{1/2} = 10^3$$

$$I_{ds3} = 10^{-4} A = 100\mu A$$


$$(W/L)_{M1} = 2 \left(\frac{W}{L}\right)_{M3} \quad \text{FOR } I_{ds1} = 2 I_{ds3}$$

= 100. Same for $M2$ & $M4$

$M1$	100
$M2$	100

b) Assume W/L of $M1$ & $M2 = 50$, then what are the maximum positive and minimum negative voltages (devices can go into linear region) if V_{in} goes between +5V to -5V. $V_{min} = -2.93V$ $V_{max} = +2.93V$

Symmetrical

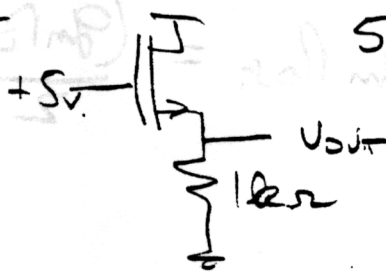


$$5 - V_t - V_{dsat} = V_{out}$$

$$4 - \left(\frac{2V_{out}}{10^3 k' W/L}\right)^{1/2} = V_{out}$$

$$4 - V_{out}^{1/2} (1.63) = V_{out}$$

ITERATE $\rightarrow V_{out} = 2.93$

4)

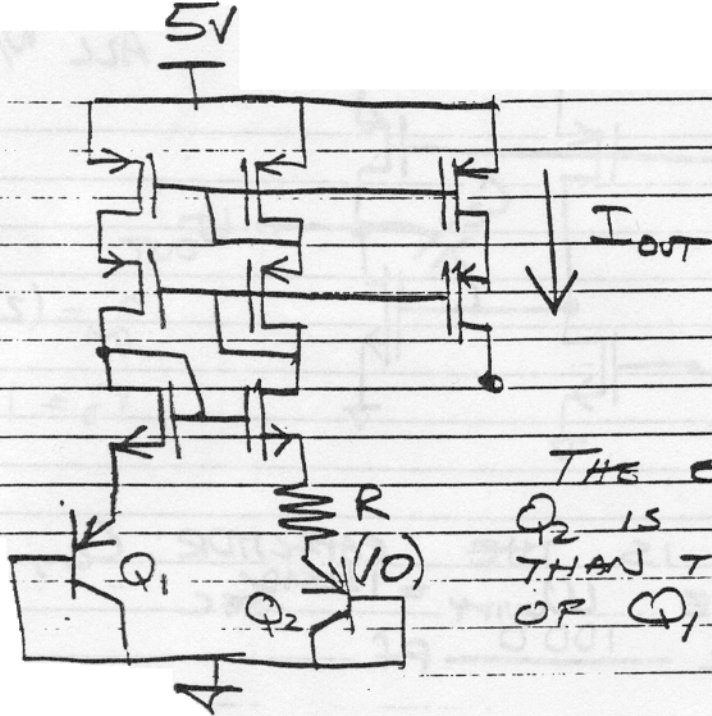

All $w/L = 100$


THE EMITTER OF Q_2 IS 10 TIMES LARGER THAN THE EMITTER OF Q_1 .

WHAT IS THE VALUE OF R SO THAT $I_{OUT} = 100 \mu A$ 600 Ω

$$V_T \ln I \quad V_T \ln I + IR$$

$$\frac{V_T}{2} \ln 10 \quad I \quad R \quad \frac{V_T \ln 10}{I} = \frac{0.026 \ln 10}{10^{-4}}$$

$$= 600 \Omega$$

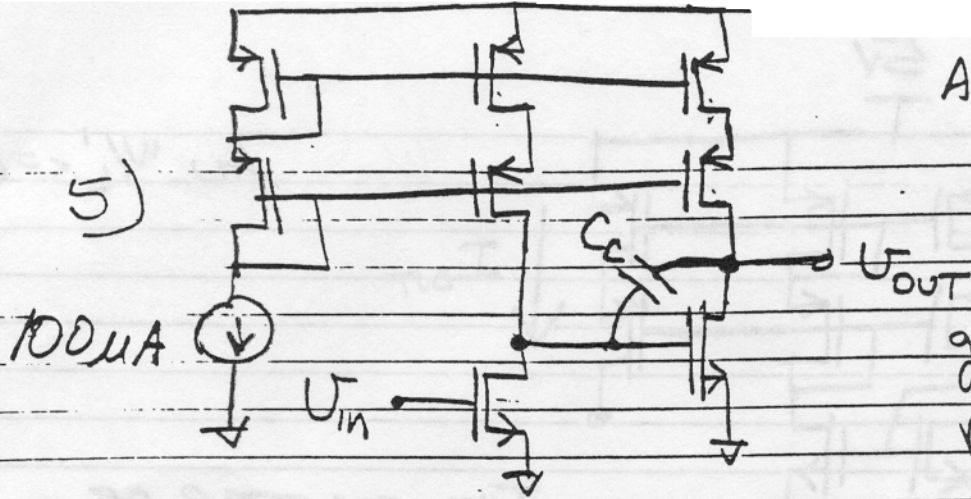

ALL W/L 'S = 50

$$g_m = (2 \cdot 10^{-4} \cdot 50 \cdot 10^{-9})^{1/2} = 10^{-3}$$

$$r_o = 10^6$$

WHAT IS THE CAPACITOR, C_c , WHICH WILL GIVE $\omega_{unity} = 1 \text{ kRAD/SEC}$
 $C_c = \frac{1000}{10^6} \text{ pf}$

($\omega_{UNITY} = \text{OPEN LOOP UNITY GAIN FREQUENCY}$)


$$a_o (g_m r_o)^2 = 10^6$$

$$\omega_c = \frac{(g_m r_o)^2}{10^6} = \frac{1}{r_o (g_m r_o C_c)}$$

$$C_c = \frac{g_m}{10^6} = 10^{-9} \text{ f}$$

1

11

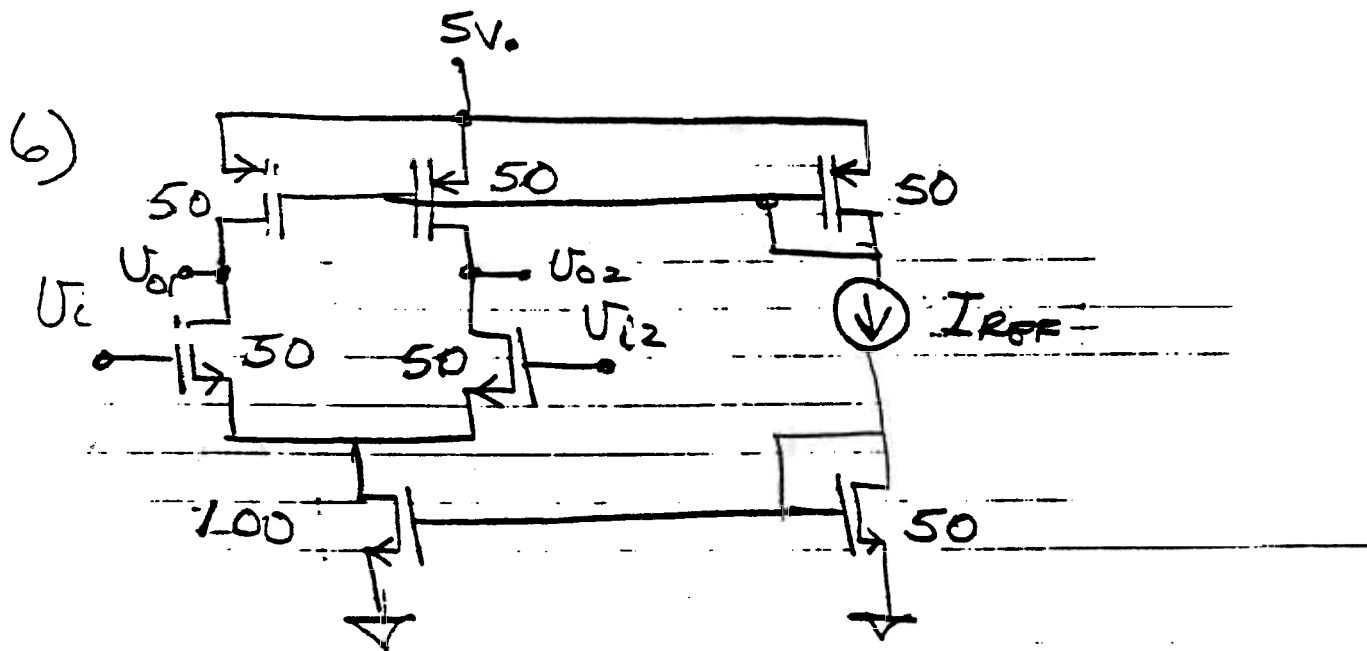

WHAT IS THE CURRENT, I_{REF} , WHICH GIVES A COMMON MODE REJECTION RATIO (CMRR) OF 60dB?

$$CMRR = \frac{A_{dm}}{A_{cm}} = \frac{g_{m2} \frac{r_{o4}}{2}}{g_{m2} r_{o4}} \cdot \frac{1}{1 + 2g_{m2} r_{o1}}$$


$$r_{o1} = \frac{r_{o4}}{2}$$

$$= \frac{1 + g_{m2} r_{o4}}{2} \approx \frac{g_{m2} r_{o4}}{2} = 10^3$$

$$\frac{(2 \mu A / I_{DS})^{1/2}}{I_{DS}} = 2 \times 10^3$$

$$I_{DS} = 25 \mu A$$

Problem 7)

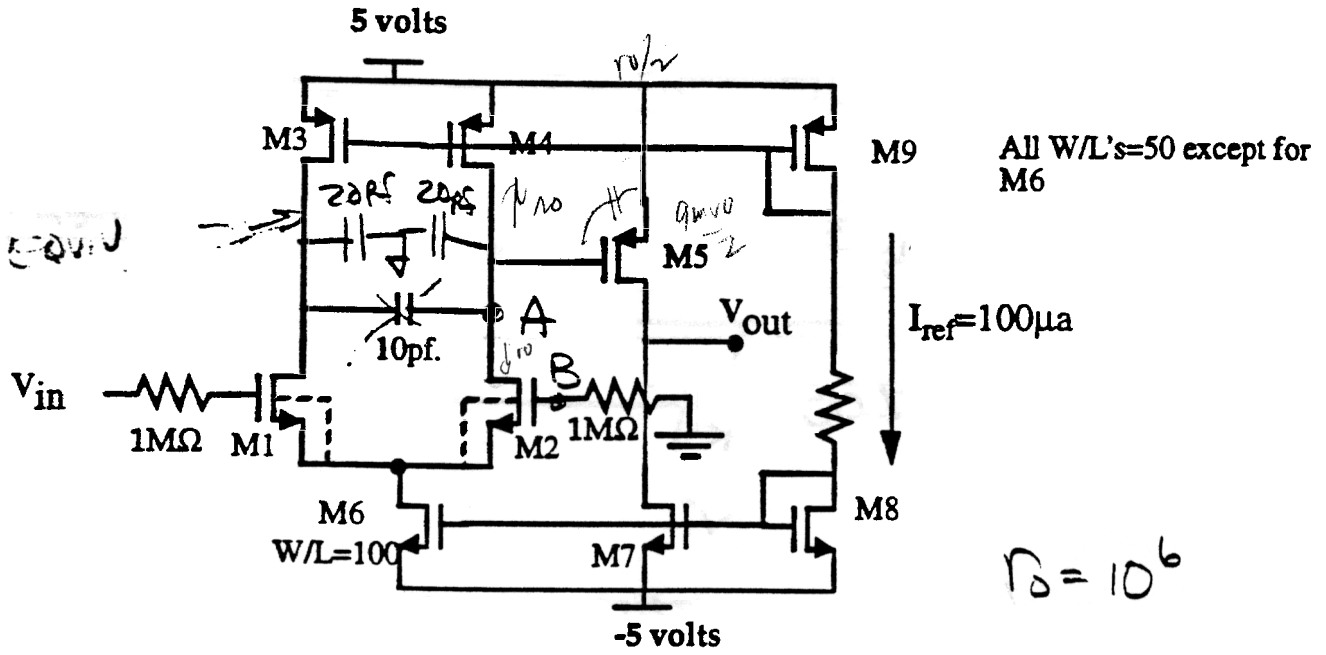

a) Where is the first pole of v_{out}/v_{in} ?

97 krad/sec

Node A

$$C_A = (C_{gs5} + C_{gd5} \frac{g_{m10}}{2} + 20 \text{ pF})$$

$$= 20.6 \text{ pF}$$

$$\omega_1 = \frac{1}{\frac{r_D}{2} C_A} = \frac{2}{10^6 \cdot 20.6 \text{ pF}} = 97 \times 10^3$$


b) Where is the second pole?

9.4 Mrad/sec

Node B

$$\omega_2 = \frac{1}{\frac{r_D}{2} (C_{gs2} + C_{gb2} + C_{gd2})} = \frac{1}{\frac{10^6}{2} (106 \text{ fF})}$$


$$= 9.4 \text{ Mrad/sec}$$

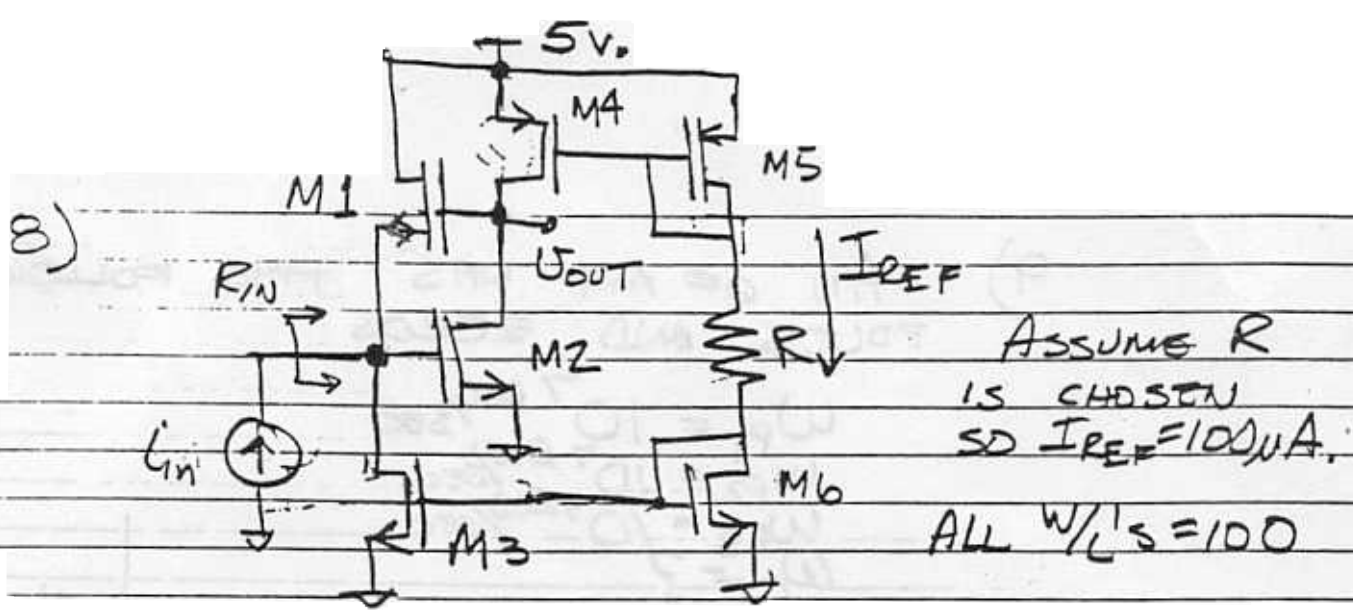

ANALYZE THIS CIRCUIT CONSIDERING $M1 \& M3$ AS THE PROVIDING FEEDBACK AND $M2 \& M4$ AS THE BASIC AMPLIFIER

a) WHAT KIND OF FEEDBACK IS THIS SHUNT-SHUNT

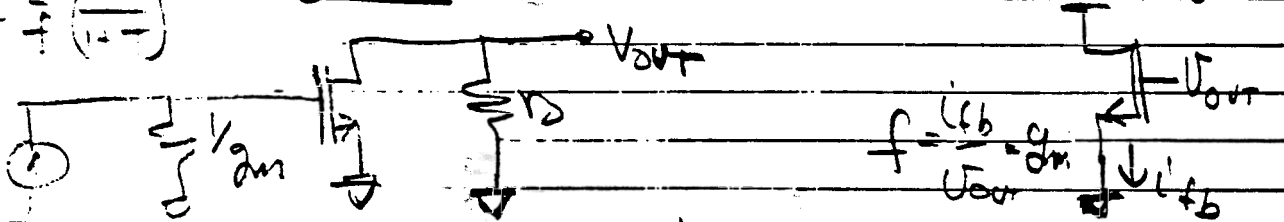b) WHAT IS THE CLOSED LOOP GAIN, $\frac{V_{out}}{V_{in}}$
 $\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{1}{A_{OL}}} = 10 \Omega$



c) WHAT IS R_{IN} 1 Ω

$$A_{OL} = \left(\frac{1}{g_m} \right) \left(g_m \frac{r_D}{2} \right) (g_m) = \frac{g_m r_D}{2} = 500 \gg 1$$


$$g_m = (2 \cdot 10^{-4} \cdot 100 \cdot 100 \mu A) = 1.4 \times 10^{-3}$$

$$R_{IN} = \frac{\frac{1}{g_m}}{1 + T} = \frac{\frac{1}{g_m}}{g_m \frac{r_D}{2}} = \frac{2}{g_m r_D} = \frac{2}{1.4 \times 10^{-3} \cdot 10^6} = 1 \Omega$$


9) AN OP AMP HAS THE FOLLOWING POLES AND ZEROS

$$\begin{aligned} \omega_{p1} &= 10^7 \text{ RAD/SEC} \\ \omega_{p2} &= 10^7 \text{ RAD/SEC} \\ \omega_{p3} &= 10^9 \text{ RAD/SEC} \\ \omega_c &=? \end{aligned}$$

AND THE OPEN LOOP GAIN $a_0 = 10^5$

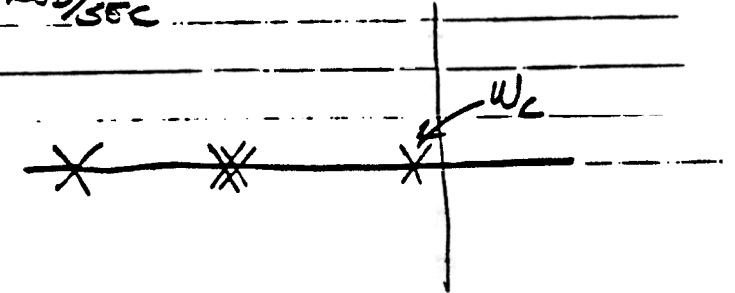

IF THE OP AMP IS CONNECTED AS FOLLOWS

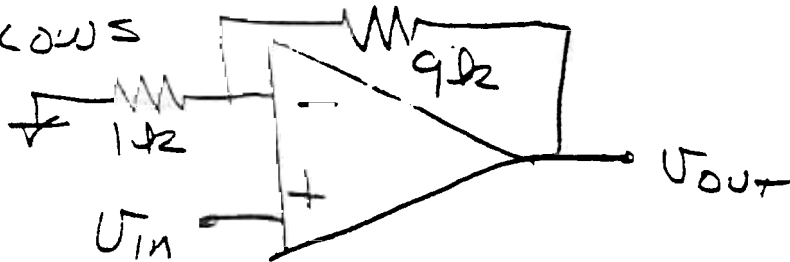


AT WHAT FREQUENCY SHOULD A COMPENSATION POLE BE ADDED SO THAT THE PHASE MARGIN IS 45° ? ω_c RAO/SEC 410 RAO/SEC

$$T = a_0 f = 10^5 \cdot (.1) = 10^4$$

10^4

1

410

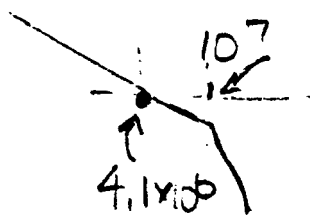


CONTRIBUTION FROM EACH POLE AT 10^7 SHOULD BE 22.5°

$$\tan^{-1} \frac{\omega}{10^7} = 22.5^\circ$$

$$\begin{aligned} \omega &= 10^7 \tan 22.5^\circ \\ &= 4.1 \times 10^6 \end{aligned}$$

Problem 10)

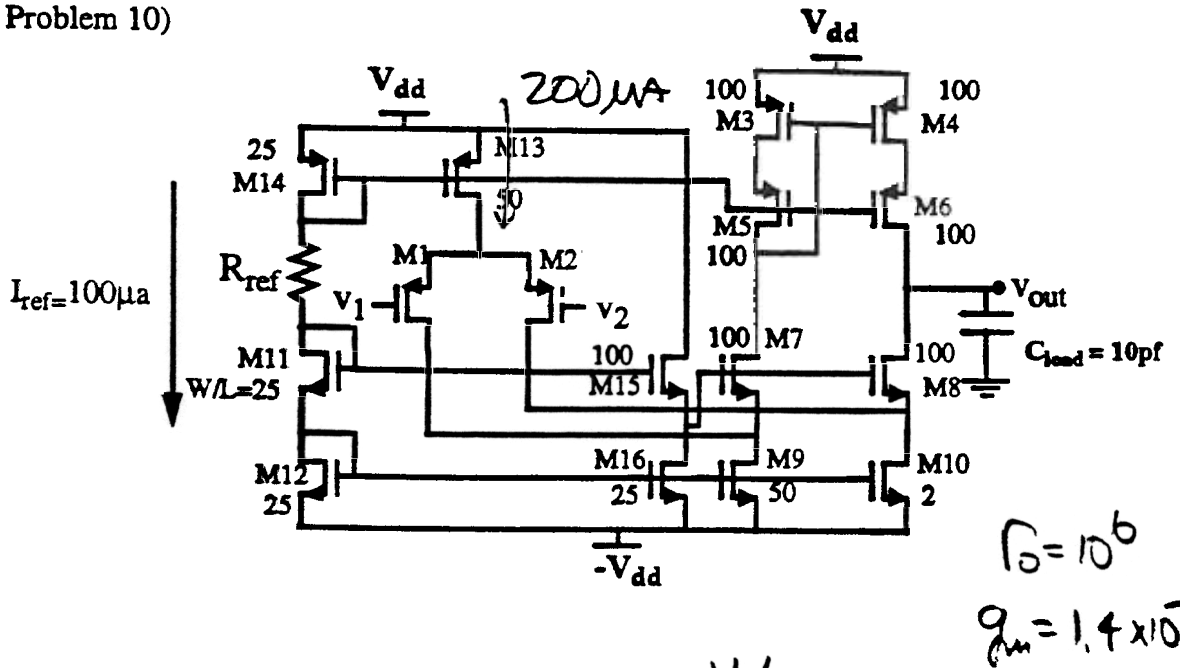

a) What is the minimum slew rate of this circuit? 20 V/μs

$$\frac{dV}{dt} = \frac{I}{C_{load}} = \frac{2 \times 10^{-4}}{10^{-11}} = 20 \text{ V}/\mu\text{s}$$

b) What is the phase margin of this circuit? 90°

$$R_{out} = r_o (g_m r_o) \parallel r_o \left(\frac{r_o}{2} \right) = .47 \times 10^9 \Omega$$

$$210 \cdot a_o = 1.2 \times 10^8$$

$$\omega_d = \frac{1}{.47 \times 10^9 \cdot 10^{-11}} = 210 \text{ rad/sec}$$

1

90°

$\omega_{NO} = 10^{10}$

$$\omega_{NO} \approx \frac{1}{\frac{1}{g_m} (12 \text{ fF})} = \frac{1.4 \times 10^3}{1.2 \times 10^{-13}} \approx 1 \times 10^{10}$$

$$\phi_o = g_m R_{out} = 1.4 \times 10^3 \cdot .47 \times 10^9 = 6.6 \times 10^5$$