

NAME SOLUTIONS

SHOW YOUR WORK

1 a SHUNT-SHUNT (2)

b $1/R_3$ (3)

do

c $R_1 || R_3 \left(\frac{1}{1+R_1/R_3} \right) \frac{R_2(R_1 || R_3)}{1 + R_2(R_1/R_3)R_3}$ (3)

d $R_1 || R_3 / (1 + R_1/R_3 R_2)$ (3)

2 a SERIES-SHUNT (2)

b 1 (3)

c 2.9×10^5 (3)

d 5Ω (3)

3 _____ (10)


4 C_c 1.1 pf (8)

5 ω_{3dB} 35 kRAD/SEC (8)

6 ω_{3dB} 4 kRAD/SEC (5)

ω_{90} 4 kRAD/SEC (5)

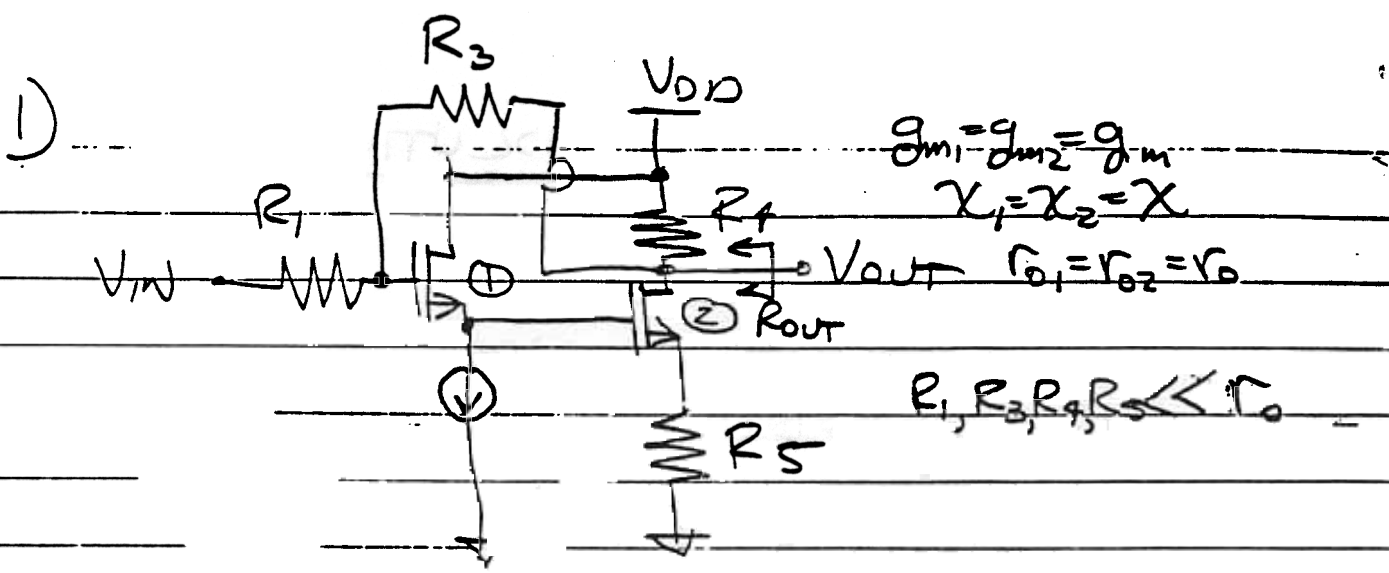
7 $\frac{.4 \text{ MRAD}}{\text{SEC}}$ 50 MRAD/SEC 9 GRAD/SEC (8)



a) WHAT KIND OF FEEDBACK IS THIS
SHUNT-SHUNT


b) WHAT IS f ? $\frac{i_{fb}}{V_{out}} = \frac{1}{R_3}$

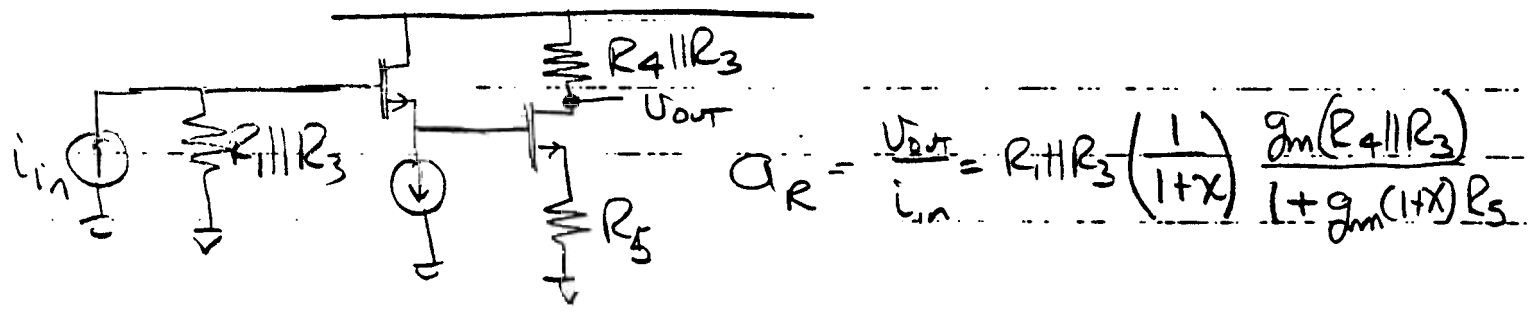c) WHAT IS THE GAIN OF THE
BASIC AMPLIFIER WITH LOADING?



d) WHAT IS R_{out} ?


$$\frac{R_4 || R_3}{1 + a_{Rf}}$$

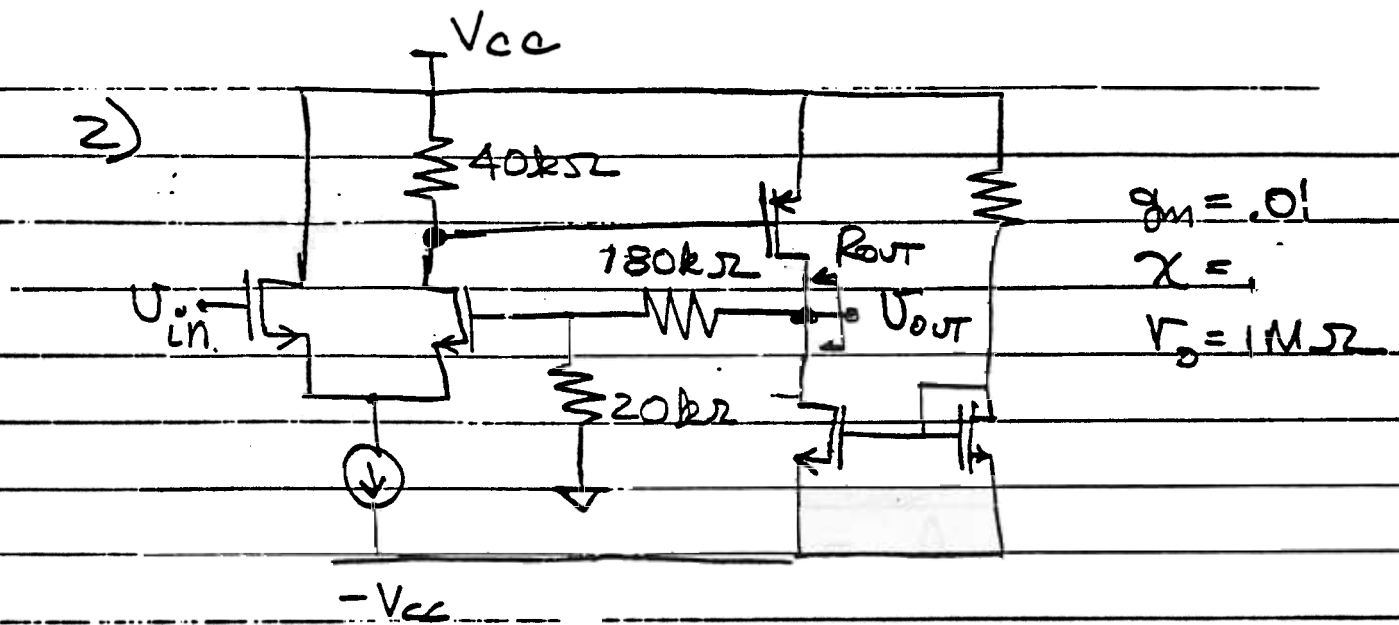

a) WHAT KIND OF FEEDBACK? SERIES-SHUNT

b) WHAT IS F ? .1

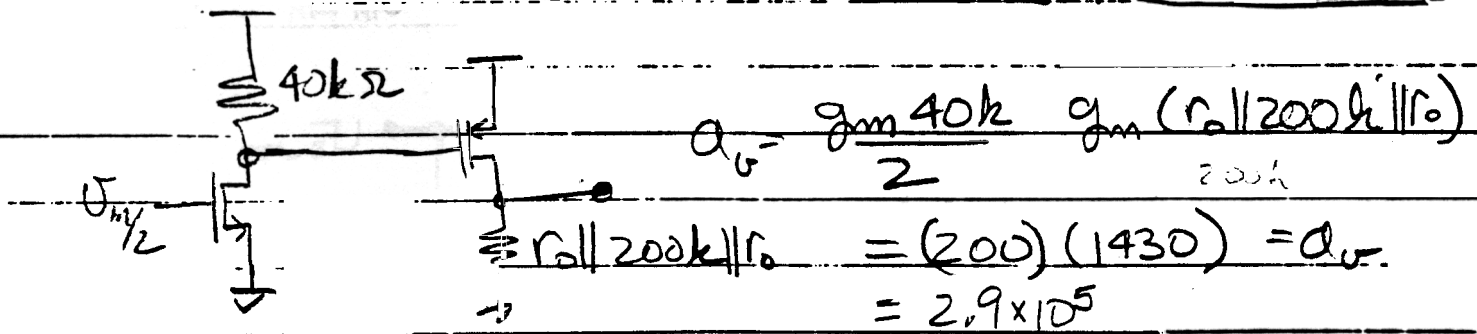c) WHAT IS THE GAIN OF THE BASIC AMPLIFIER WITH LOADING? 2.9×10^5



d) WHAT IS THE OUTPUT RESISTANCE, R_{out} ?
 5Ω

$$\frac{143k}{(1 + .1 a_v)} = \frac{143k}{2.9 \times 10^4} = 5$$

3) DESIGN A CIRCUIT WHICH MEETS THE FOLLOWING SPECIFICATIONS

$$R_{in} = 10k\Omega$$

$$R_{out} < 1\Omega$$

$$A_v = \frac{V_{out}}{V_{in}} = 2$$

ASSUME YOU CANT USE MORE THAN 6 $10k\Omega$ RESISTORS AND 3 TRANSISTORS WITH THE FOLLOWING SPECIFICATIONS (NMOS)


$$I_m = 0.1$$

$$V_0 = 1V$$


$$X = 0$$

$$\frac{V_{out}}{i_m} = \frac{1}{f}$$
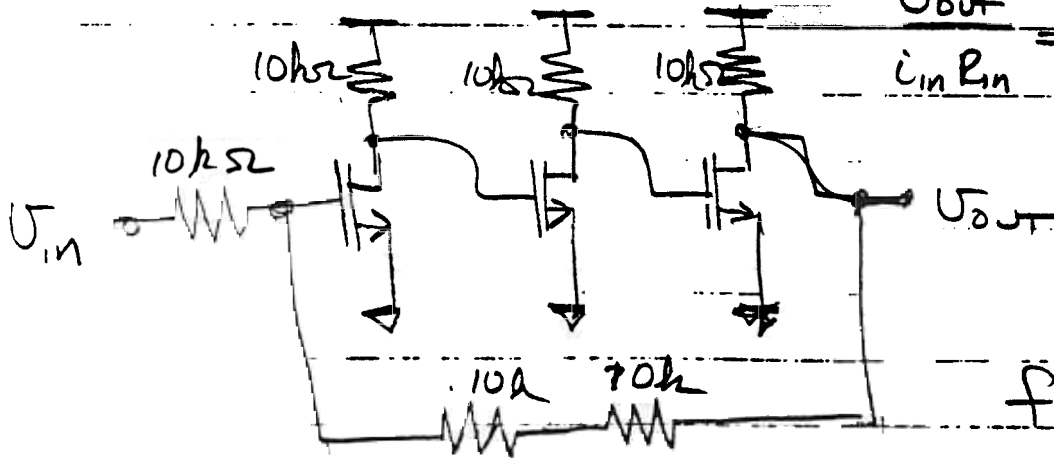
$$\frac{V_{out}}{i_m R_{in}} = \frac{1}{f R_{in}} = \frac{20k\Omega}{10k\Omega} = 2$$



$$f = \frac{1}{5k}$$

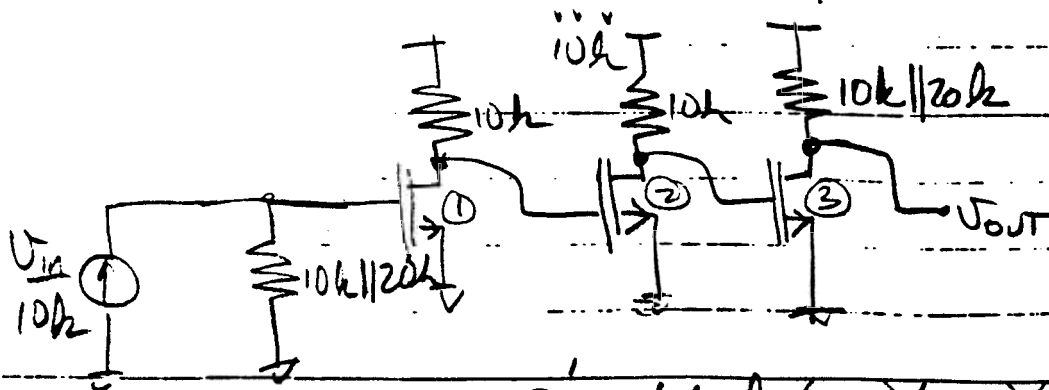


$$T = A_v f$$

$$R_{out} = \frac{3.3k}{1+T}$$

$$= \frac{3.3k}{8.7 \times 10^5} = 3.8m\Omega$$

$$A_v = 6.6k (100)(100)(66)$$

4)

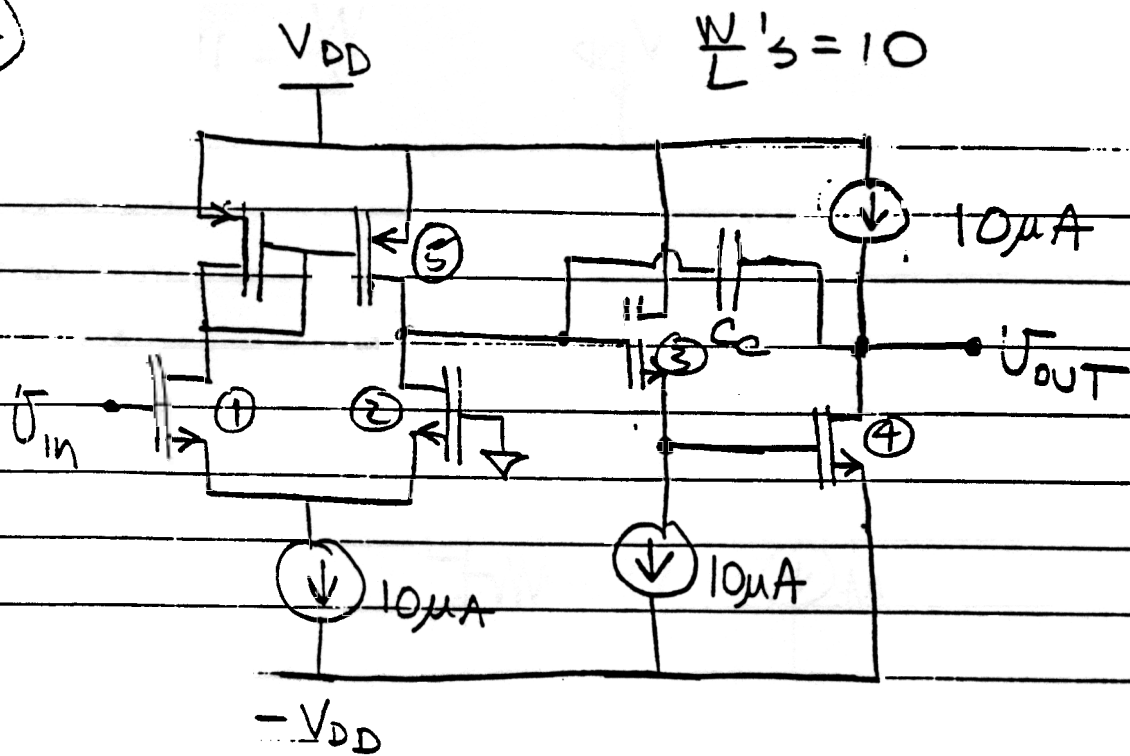

$$C_{gd} = 0.1 \text{ pF}$$

$$k'_n = k'_p = 100 \mu\text{A}/\text{V}^2$$

$$C_{gs} = 1 \text{ pF}$$

$$C_{db} = 0.1 \text{ pF}$$

$$V_{Tn} = V_{Tp} = 1 \text{ V}$$

$$C_{sb} = 0.1 \text{ pF}$$

$$\lambda_n = \lambda_p = 0.1$$

$$\gamma_n = \gamma_p = 0$$

CALCULATE THE VALUE OF C_c WHICH WILL GIVE A 3dB FREQUENCY OF 1KHz.
 $C_c = 1.1 \text{ pF}$

$$g_{m4} = \left(2 \mu_n \frac{W}{L} \right)^{1/2} = \left(2 \times 10^{-4} \times 10 \times 10^{-6} \times 10 \right)^{1/2} = 1.41 \times 10^{-4}$$

$$r_{o4} = \frac{1}{0.1 \times 10^{-5}} = 1 \text{ M}\Omega$$


$$r_{o2} = r_{o5} = \frac{1}{0.1 \times 5 \times 10^{-6}} = 2 \text{ k}\Omega$$

$$C_m = C_c (1 + g_{m4} r_{o4})$$

$$1 \text{ KHz} = \frac{1}{2\pi \times (r_{o5} \parallel r_{o2}) C_m}$$

$$C_c = \frac{1}{2\pi \times 10^3 \times 10^6 (g_{m4} r_{o4})}$$

$$= 1.1 \text{ pF}$$

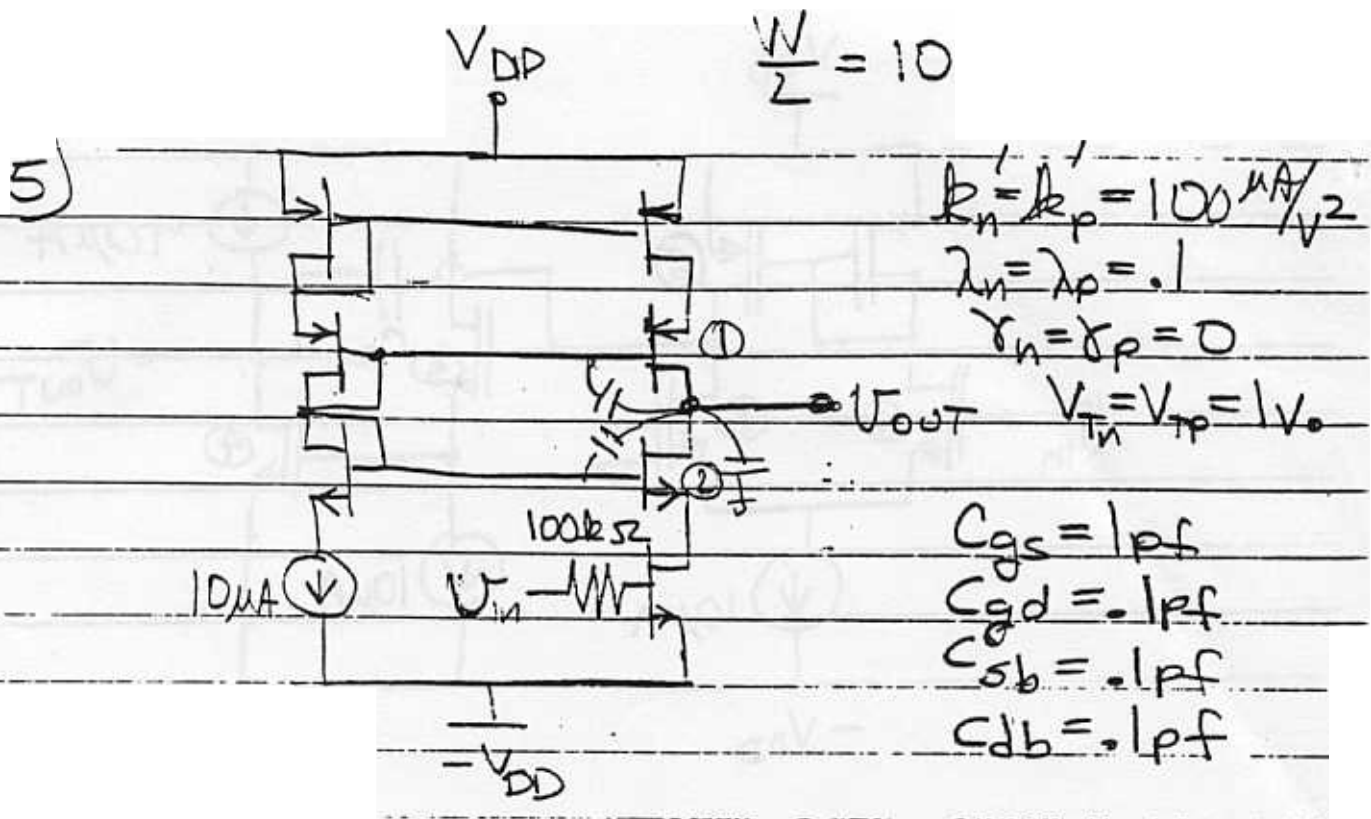

WHAT IS THE 3dB FREQ. OF THIS CIRCUIT? 35 KRAD/SEC

$$g_m = 1A \times 10^{-4}$$

$$R_{out} = \frac{r_o (g_m r_o)}{2} = 70 \times 10^6 \Omega$$

$$r_o = \frac{1}{10^{-5} \times 0.1} = 1 \text{ M}\Omega$$

$$C_{out} = C_{gd,1} + C_{gd,2} + C_{db,1} + C_{db,2} = 0.4 pF$$


AT INPUT $100 k\Omega \ll R_{out}$

$$C_{in} = C_{gs} + 2C_{gd} \approx 1.2 pF$$

MUCH HIGHER FREQ.

$$\omega_{3dB} = \frac{1}{R_{out} C_{out}} = 35 \text{ KRAD/SEC}$$
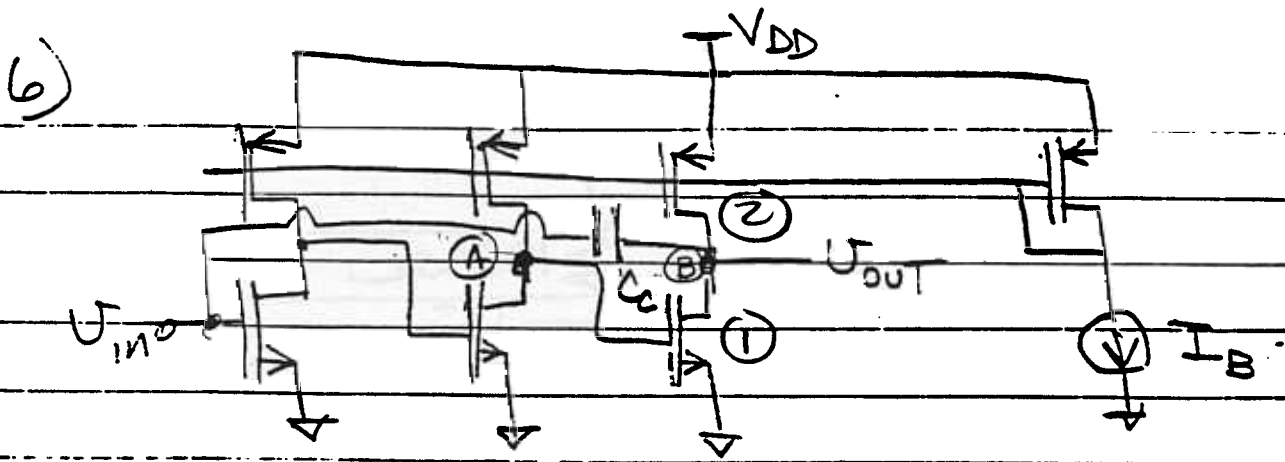
$$70 \times 10^6 \times 0.4 \times 10^{-12} = 35 \times 10^3 \text{ RAD/SEC}$$



$$g_m = 0.01$$

$$r_o = 1 \text{ M}\Omega$$

$$\chi = 0.1$$

$$C_{gs} = 1 \text{ pf}$$

$$C_{gd} = 0.1 \text{ pf}$$

$$C_{db} = 0.1 \text{ pf}$$

$$C_{ds} = 0.1 \text{ pf}$$

d) WHAT IS THE 3db FREQUENCY IF $C_c = 1 \text{ pf}$?
4 kHz/sec


$$C_{OUT} = C_c + C_{GD1} + C_{GD2} + C_{DB1} + C_{DB2} = 1.4 \text{ pf}$$

$$C_m = (0.01) \frac{r_o}{2} C_{gd} = 5 \times 10^3 \times 0.1 \text{ pf} = 500 \text{ pf}$$



$$R_{OUT} = 500 \text{ k} \quad \omega_{3dB} = \frac{1}{500 \text{ k} \times 5 \times 10^{-10}} = 4 \text{ kHz/sec}$$

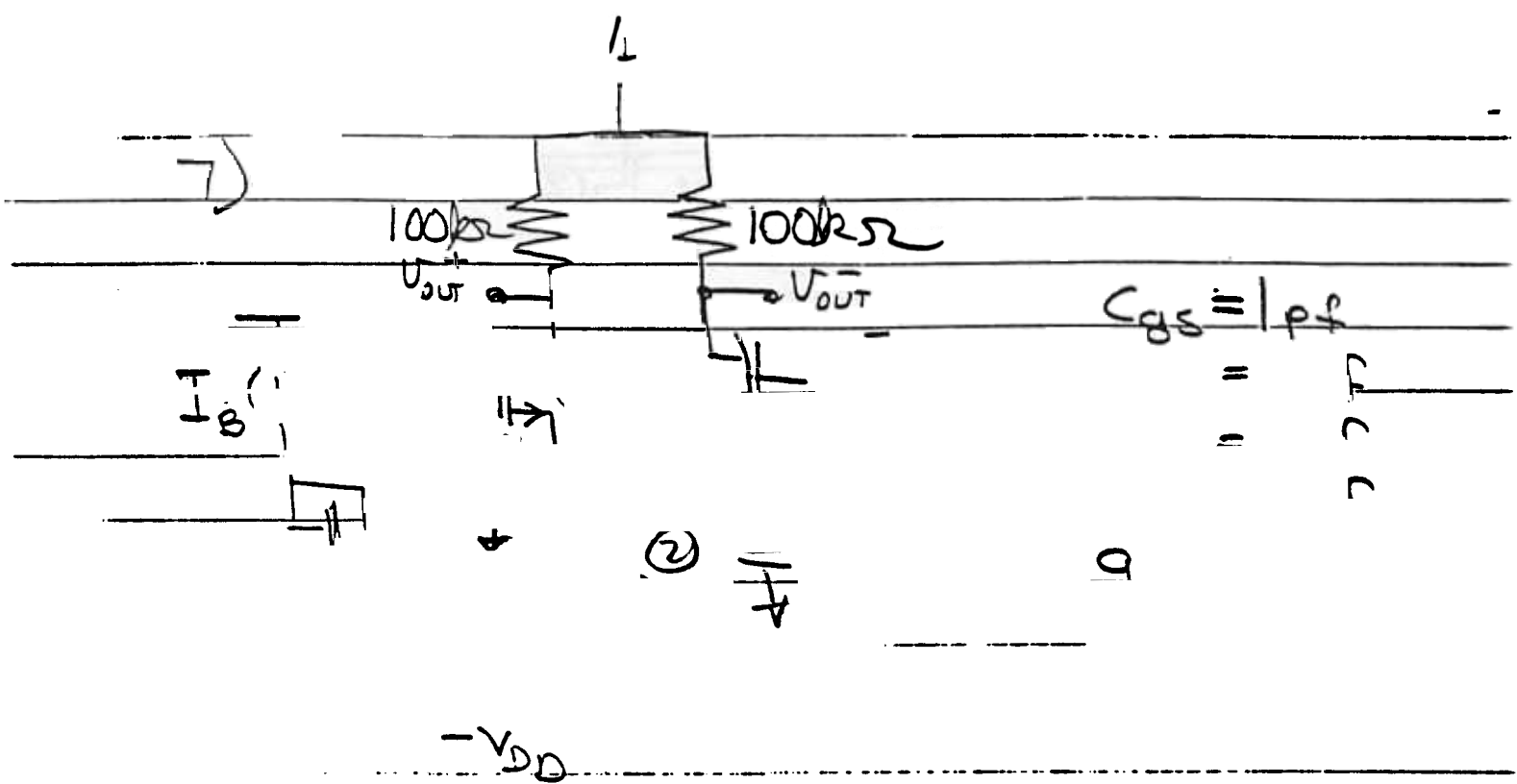
b) IF $C_c = 0 \text{ pf}$ AT WHAT FREQUENCY IS THE PHASE SHIFT OF $U_{OUT}/U_{IN} = -90^\circ$?

4 kHz/sec NODES A & B HAVE
 -45° AT ω_{3dB}



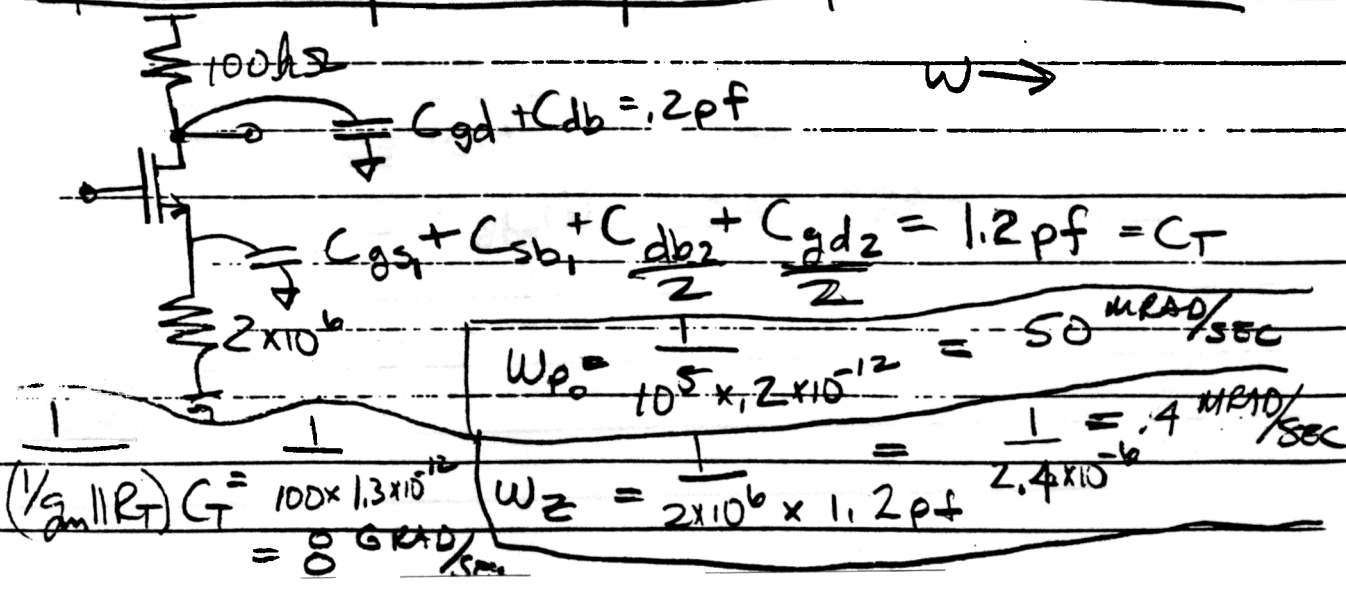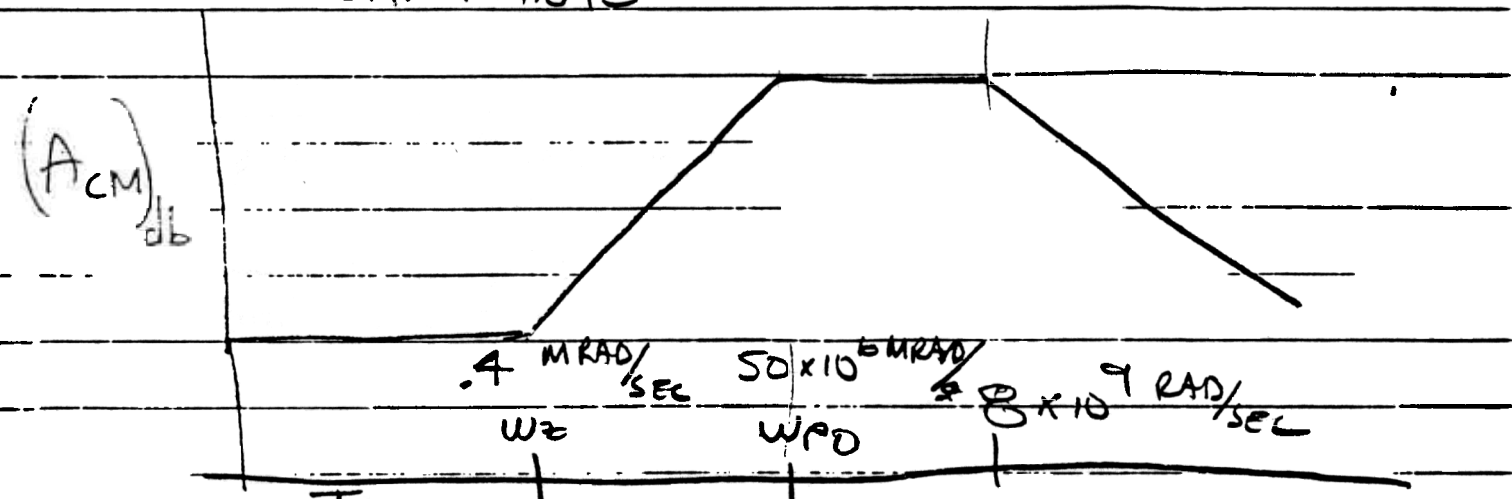PLOT $A_{CM} (db)$ vs. ω AND LABEL THE BREAK POINTS



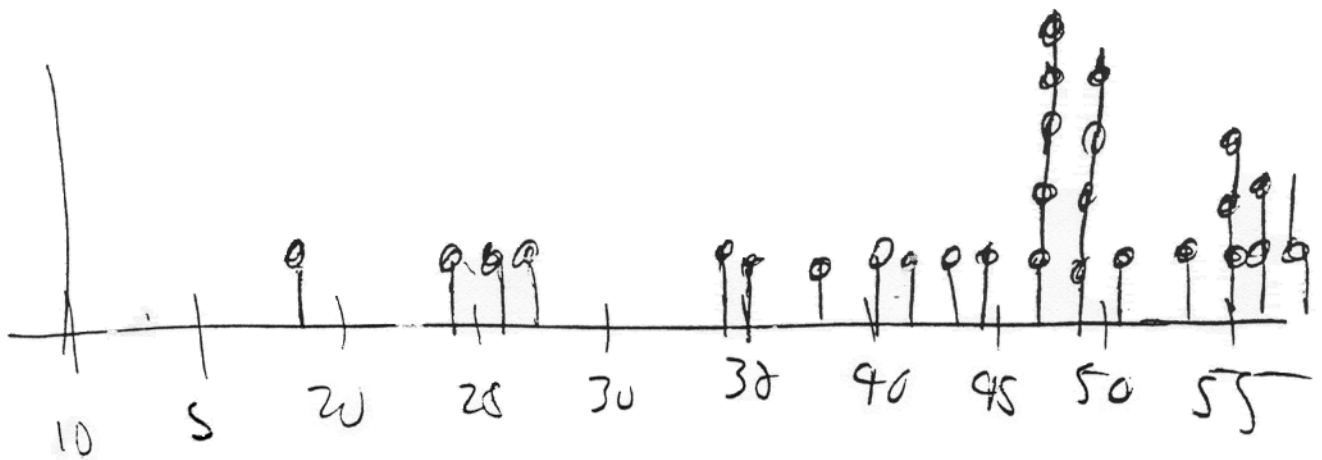

$$\frac{g_m \cdot 10^5 \parallel \frac{1}{j\omega C_{out}}}{+ g_m (R_f \parallel \frac{1}{j\omega C_f})}$$

$$+ g_m R_T = \frac{1 + j\omega R_T C_T}{1 + j\omega R_T C_T + g_m R_T}$$

$$= \frac{1 + j\omega R_T C_T}{1 + g_m R_T \left(1 + \frac{j\omega R_T C_T}{1 + g_m R_T} \right)}$$

x 43
r 2

$$\omega_p = \left[\left(\frac{1}{g_m \parallel R_T} \right) C_T \right]^{-1}$$