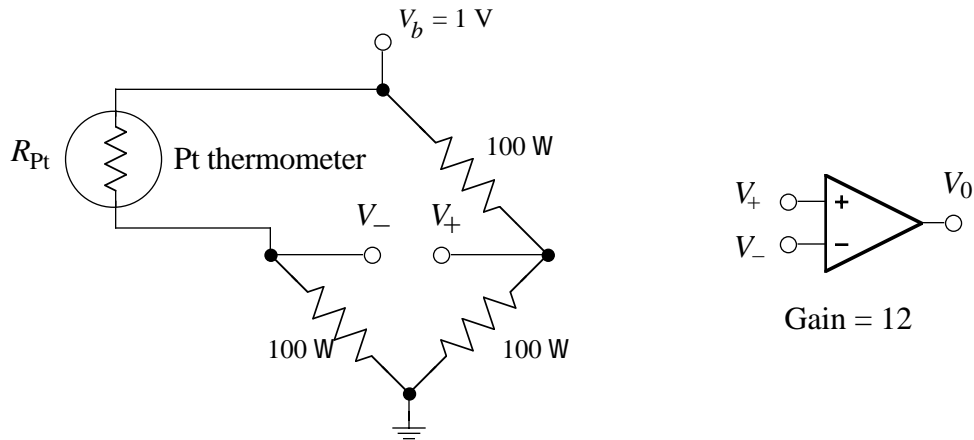


EECS 145L Final Examination Solutions (Fall 2000)

UNIVERSITY OF CALIFORNIA, BERKELEY
 College of Engineering, Electrical Engineering and Computer Sciences Department

1a



$$V_+ - V_- = R/(2R) - R/(2R+DR), R = 100 \text{ W}$$

$$\text{At } 0^\circ\text{C } V_+ - V_- = 0$$

$$\text{At } 100^\circ\text{C } V_+ - V_- = 1/2 \text{ V} - 100/240 \text{ V} = 0.0833 \text{ V}$$

$$\text{For } V_0 = 1.0 \text{ V, need gain} = 1 \text{ V} / 0.0833 \text{ V} = 12.$$

[an alternate solution used $V_b = 12 \text{ V}$. This causes significant self-heating $P = V^2/100 = 0.36 \text{ W}$ but was accepted]

$$1b \quad V_0 = 12 \text{ V} [1/2 - 100/(200 + 0.4T)]$$

$$1c \quad \text{At } 50^\circ\text{C, } V_0 = 12 \text{ V} [1/2 - 100/220] = 0.5454 \text{ V}$$

1d The linear response would be 0.500 V. The voltage deviation is $0.5454 \text{ V} - 0.5000 \text{ V} = 0.0454 \text{ V}$. Since the response slope is 100°C per V , the temperature deviation is 4.54°C .

$$2a \quad R = 3 \text{ V} / 30 \text{ mA} = 100 \text{ W}$$


2b Since the ideal op-amp has infinite input impedance, $I_1 = 0$ and $I_2 = 0$. The virtual short rule gives $V_2 = V_1 = 0$. So $IR = 0$ and since all the current through the op-amp, $I_D = 0$ and $V_0 = 0 \text{ V}$

$$2c \quad I_1 = 0, I_2 = 0, V_2 = 3 \text{ V, } IR = 30 \text{ mA, } I_D = 30 \text{ mA, } V_D = 0.6217 \text{ V, } V_0 = 3.6217 \text{ V.}$$

$$2d \quad I_1 = 0, I_2 = 0, V_2 = 3 \text{ V, } IR = 30 \text{ mA, } I_D = 30 \text{ mA, } V_D = (173/273) 0.6217 \text{ V} = 0.3940, V_0 = 3.3940 \text{ V.}$$


EECS 145L Final Examination Solutions (Fall 2000)

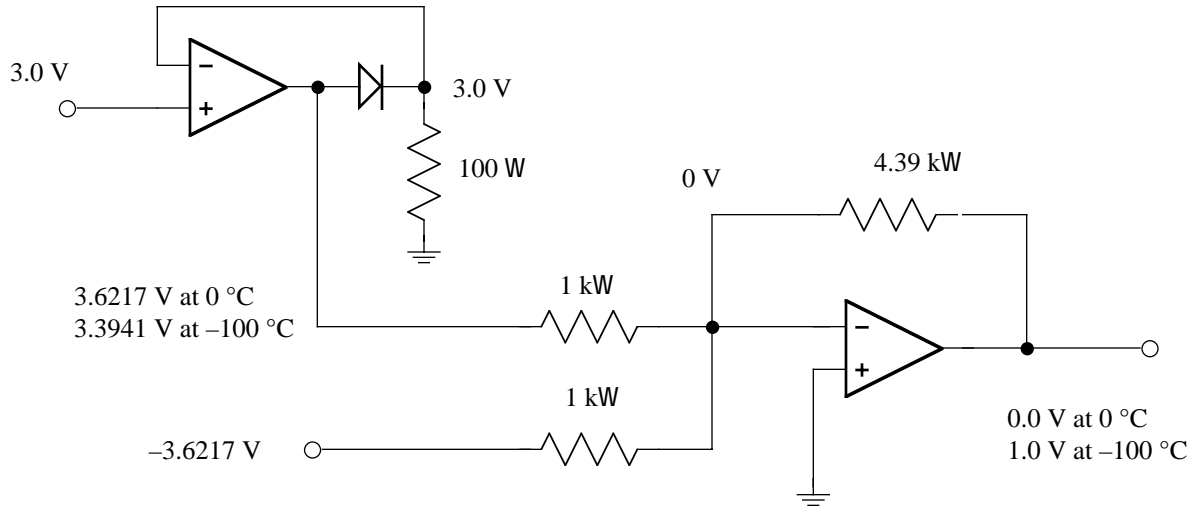- 3 V_0 decreases by 0.228 V from 0°C to -100°C so a gain of -4.39 is needed to produce 0 V at 0°C and 1.0 V at -100°C .




[Either the op-amp adder circuit and the instrumentation amplifier were accepted]

4

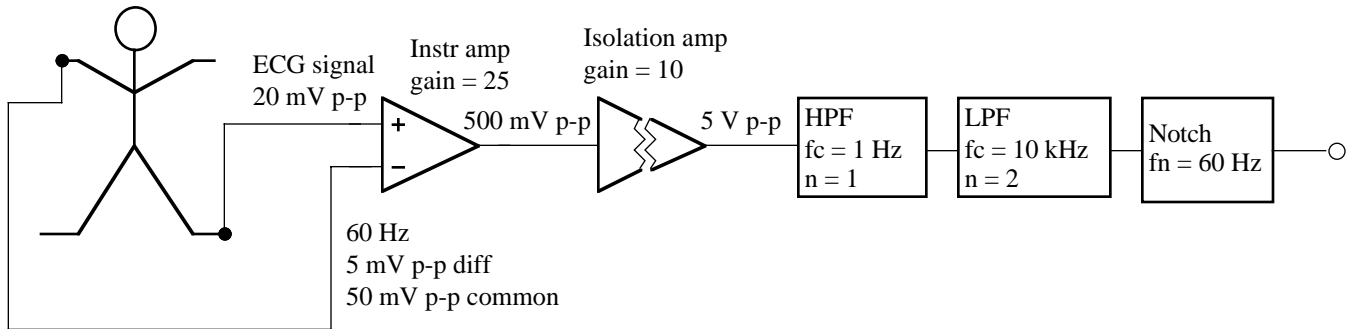

- [5 points off for each element missing]
 [4 points off if filter order not given] [2 points off for excessively large number of filter stages]
 [5 points off if differential ECG signal not amplified in a differential way- isolation amplifier or instrumentation amplifier could come first but not filters]
 [4 points off if 5 V ECG p-p signal not produced] [4 points off for no voltage values]

5a

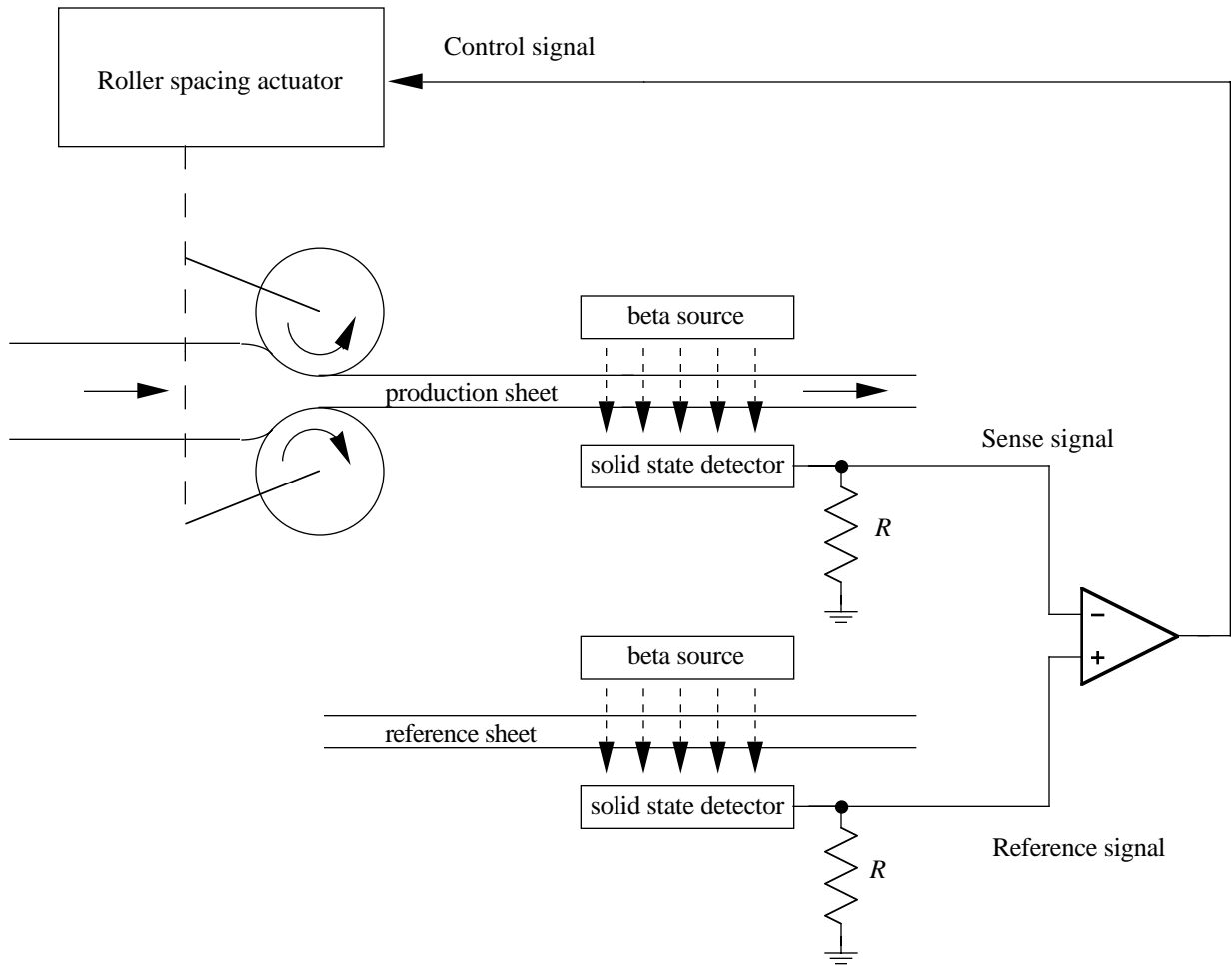

[4 points off if no solid state detector current to voltage conversion]
 [4 points off if sheets are not between beta source and detector]

5b

- 1 The thinner reference sheet absorbs less beta energy
- 2 the reference solid state detector current increases
- 3 This increases the voltage on the positive input of the difference amplifier and increases the error voltage.
- 4 This input to the controller decreases the spacing between the rollers and produces thinner sheets.
- 5 The spacing is stable when the output sheet has the same thickness as the reference sheet.

EECS 145L Final Examination Solutions (Fall 2000)

145L Final Examination score distribution:

101-110	1U	111-120	0	121-130	0
131-140	1U	141-150	0	0151-160	0
161-170	3U	171-180	0	181-190	1U
191-200	6U, 2G				

undergraduate (U) average = 175.3

graduate (G) average = 200

145L Course Grade Distribution

Grade	Undergraduate Scores	Graduate Scores
A+	914	944
A	899, 894	888
A-	877, 860	
B+	831, 830	
B	818	
B-	777, 763, 761	
C+		
C	702	
C-		
Maximum	1000	1000
Average	827	916