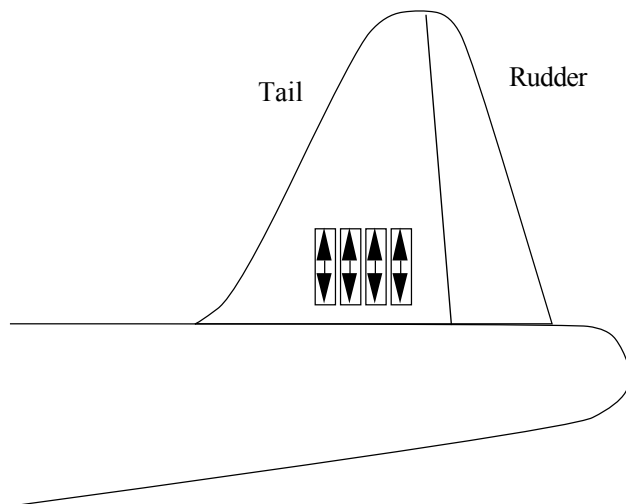


Midterm #2 Solutions – EECS 145L Fall 2001


- 1a** Technical requirements of a ground fault interrupter circuit:
- (i) open both current carrying power conductors (hot and neutral) when the the difference in their currents exceeds 5 mA
 - (ii) provide a reset button
 - (iii) provide a test button
- [5 points off for describing the circuit breaker]
[1 points off each for missing the reset or test features]
- 1b** How the ground fault interrupter circuit functions:
- (i) the difference in currents is converted into a 60 Hz voltage using a differential transformer
 - (ii) this voltage is rectified and amplified
 - (iii) the resulting dc voltage trips two relays which hold both conductors open until reset
 - (iv) the test button sends a 5 mA current through differential transformer
- [1 point off for no test button]
- 2a** Since $R_2/(R_1 + R_2) = R_3/(R_T + R_3)$, $R_2 = R_3$, and $R_T = 10\text{ k}\Omega$ at 20°C the solution is $R_1 = 10\text{ k}\Omega$.
- 2b** $P = V_T^2/R = (0.5\text{ volts})^2/(10\text{ k}\Omega) = 25\text{ }\mu\text{W}$
- 2c** Amplifier output of 0.05 volts means a bridge output $V_+ - V_- = 0.01$ volts. Using the bridge equation (supplied on the equation sheets), we have $R_T = (10000\text{ }\Omega) * (10000\text{ }\Omega - 0.01 * 20,000\text{ }\Omega) / (10000\text{ }\Omega + 0.01 * 20,000\text{ }\Omega) = 9608\text{ }\Omega$
- [1 point off for not dividing by the amplifier gain]
[3 points off for assuming a linear response from 0°C and $0\text{ }\Omega$ to 20°C and $10\text{ k}\Omega$]
- 2d** $T = 20^\circ\text{C} + (9608\text{ }\Omega - 10000\text{ }\Omega) / (-300\text{ }\Omega/\text{C}^\circ) = 21.3^\circ\text{C}$
- 2e** $V_T = 1 - 10000\text{ }\Omega / (10000\text{ }\Omega + 9608\text{ }\Omega) = 0.490$ volts
 $P = (0.490\text{ volts})^2 / (9608\text{ }\Omega) = 24.99\text{ }\mu\text{W}$ ($25\text{ }\mu\text{W}$ was accepted for full credit)
- 2f** Dissipation coefficient = $25\text{ }\mu\text{W} / (21.3^\circ\text{C} - 20^\circ\text{C}) = 19\text{ }\mu\text{W}/^\circ\text{C}$

3a



Midterm #2 Solutions – EECS 145L Fall 2001

3b

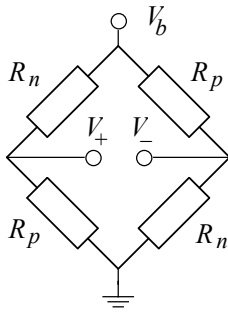

[3 points off if bridge is drawn but gauges are reversed]

$$3c \quad V_0 = \frac{R_p}{R_p + R_N} - \frac{R_N}{R_p + R_N} = \frac{(R + \Delta R_p) - (R + \Delta R_N)}{2R + \Delta R_p + \Delta R_N}$$

$$V_0 = \frac{\Delta R_p / R - \Delta R_N / R}{2 + \Delta R_p / R + \Delta R_N / R} = \frac{20 \Delta L / L}{2 + 20,000(\Delta L / L)^2} = \frac{10 \Delta L / L}{1 + 10,000(\Delta L / L)^2}$$

[a common error was to write down the bridge equation and then plug in terms like

$$R_p = R_0(100 \Delta L / L + 10,000 (\Delta L / L)^2)]$$

3 d For $V_s = 1$ volt, bridge sensitivity is 0.1 mV per μ strain

3 e The Johnson noise in a single 10 k Ω resistor is given by

$$V_{J_{rms}} = 1.29 \times 10^{-10} \text{ V}\Omega^{-1/2} \text{ Hz}^{-1/2} \text{ sqrt}(10 \text{ k}\Omega \text{ 16 Hz}) = 1.29 \times 10^{-10} \times 400 \text{ V} = 5.16 \times 10^{-8} \text{ V}$$

The bias and ground points are at a fixed voltage, so the Johnson noise in two of the resistors adds a Johnson noise voltage in quadrature to V_- and the Johnson noise in the other two resistors adds a Johnson noise in quadrature to V_+ . (Note that the bridge equation describes how external average voltages are distributed to produce V_- and V_+)

$$V_{-rms} = \sqrt{V_{J_{rms}}^2 + V_{J_{rms}}^2} \quad V_{+rms} = \sqrt{V_{J_{rms}}^2 + V_{J_{rms}}^2}$$

The Johnson noise in $V_0 = V_+ - V_-$ is given by adding the noise of the individual components in quadrature:

$$V_{0rms} = \sqrt{V_{+rms}^2 + V_{-rms}^2} = \sqrt{4V_{J_{rms}}^2} = 2V_{J_{rms}}$$

This is 0.103 μ V rms, which corresponds to $\Delta L / L \approx 10^{-9}$ rms.

[2 points off for giving the rms equivalent strain due to the Johnson noise in only one resistor]

[3 points off for giving the rms voltage noise from one resistor but not relating it to rms strain]

[4 points off for writing down the Johnson noise equation and using it improperly or incompletely]

145L midterm #2 undergraduate grade distribution:

| | | | | |
|---------|----------------|--------|---|----|
| Problem | | 31-40 | | |
| 1 | 13.0 (20 max) | 41-50 | 1 | D |
| 2 | 34.9 (40 max) | 51-60 | 1 | C |
| 3 | 29.6 (40 max) | 61-70 | 3 | B- |
| total | 77.4 (100 max) | 71-80 | 8 | B |
| | | 81-90 | 4 | A |
| | | 91-100 | 3 | A+ |