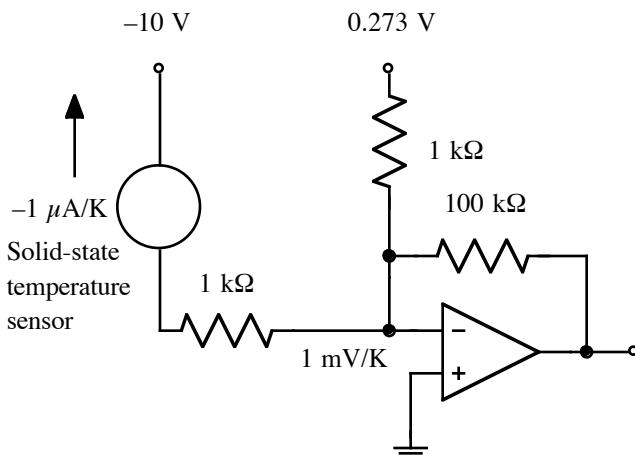


## Midterm #2 Solutions – EECS 145L Fall 2005

- 1a A sensor converts a physical signal into an electrical signal
- 1b The response curve of a sensor is the relationship between the physical input and the electrical output OR the output response after a step change in the input  
[both were accepted]
- 1c The sensitivity of a sensor is the change in electrical output per change in physical input  
[3 points off for ratio of output to input rather than ratio of changes]  
[2 points off if neither ratio is the change in electrical output]
- 2 To calibrate a sensor
- use the sensor on as many accurately known physical quantities as possible, spanning as much of the range as possible
  - Fit a smooth curve through the calibration points
- [5 points off for adjusting the output level to insure agreement at one point]

**3a** Want a sensitivity of 0.1 V/K and a shift of  $-273\text{K}$ . Inverting amplifier sums  $(1 \text{ mV/K}) T + 0.273 \text{ V}$  and amplifies by a factor of  $-100$ .



[3 points off for not converting  $^{\circ}\text{K}$  to  $^{\circ}\text{C}$ ]  
[2 points off for a signal  $> 50\text{V}$ ]  
[2 points off for a sensitivity  $\geq 1\text{V/K}$  or  $\leq 0.01 \text{ V/K}$ ]

**3b** Mount two strain gauges on a membrane cemented to a vacuum tank. The external pressure will cause the membrane to stretch. Place the two resistive strain gauges in a bridge and connect the bridge to an instrumentation amplifier.

Bridge output is

$$V_+ - V_- = V_b \left[ \frac{R + \Delta R}{2R + \Delta R} - \frac{R}{2R + \Delta R} \right] = V_b \left[ \frac{\Delta R}{2R + \Delta R} \right] \approx V_b \frac{\Delta R}{2R}$$


Strain is proportional to pressure:  $\Delta L/L = kP$ , where  $k$  depends on Young's modulus and the membrane geometry  
 $\Delta R/R = 2\Delta L/L = 2kP$

Instrumentation amplifier output  $V_0 = G(V_+ - V_-) = V_b kPG$

Want to choose  $V_b kG = 0.1 \text{ V/mm Hg}$ , so that  $\Delta P = 100 \text{ mm Hg}$  gives  $\Delta V_0 = 10 \text{ V}$

Choose  $R$  so that  $V_+ - V_- = 0$  at  $700 \text{ mm Hg}$ .
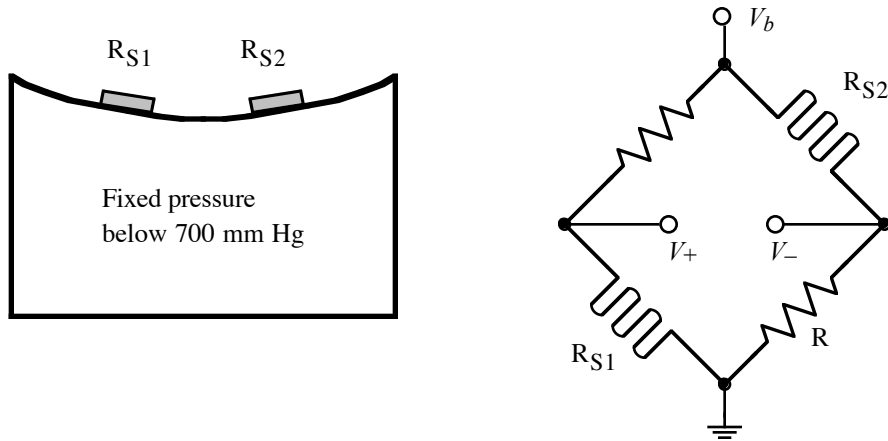
## Midterm #2 Solutions – EECS 145L Fall 2005



[The membrane is under tension on both sides. However, no points off for incorrectly assuming tension on one side, compression on the other side.]

[3 points off for not using a bridge circuit]


[3 points off for not describing what the technician should adjust to get the desired sensitivity of 0.1 V/mm Hg]

[2 points off for  $V_+ - V_- = V_b \Delta R / (2R)$  and no other guidance to the technician]

[2 points off for not mounting the strain gauges on a membrane]

[1 points off for not providing a fixed pressure <700 mmHg on one side of the membrane]

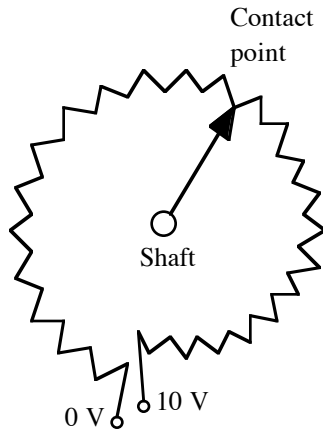**3c** Attach the shaft of a circular resistor to a weathervane that rotates to point in the direction of the wind.



[3 points off for not tracking wind direction]

**3d** Attach four strain gauges to a flexible sheet and measure the force of the wind, similar to measuring the force of the weights in the strain lab. Connect the strain gauge in a bridge and connect the bridge output to an instrumentation amplifier with a gain  $G$ .

$\Delta L/L = kW$ , where  $W$  is wind speed, and  $k$  depends on Young's modulus and the sheet geometry


Bridge output is

$$V_+ - V_- = V_b \left[ \frac{R + \Delta R}{2R} - \frac{R - \Delta R}{2R} \right] = V_b \frac{\Delta R}{R}$$

Instrumentation amplifier output  $V_0 = G (V_+ - V_-) = 2 V_b G k W$

Want to choose  $V_b k G = 1 \text{ V per } 40 \text{ km/hr}$
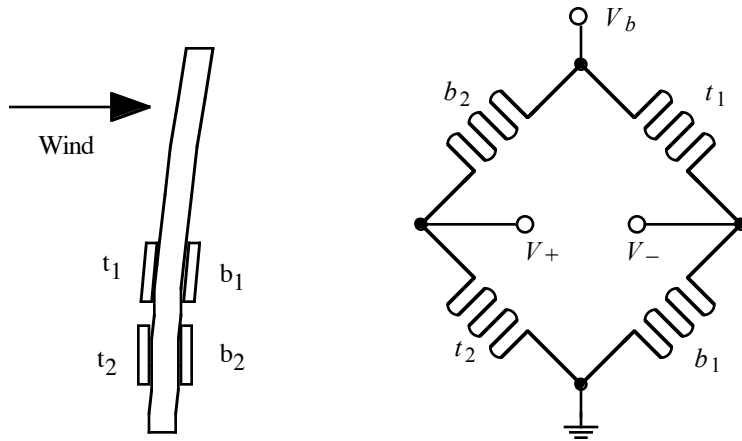
## Midterm #2 Solutions – EECS 145L Fall 2005



[2 points off for not tracking wind direction]


[3 points off for not using a bridge circuit]

[2 points off for not describing what the technician should adjust to get the desired sensitivity of 1 V per 20 km/hr]

[1 points off for  $V_+ - V_- = V_b \Delta R/R$  and no other guidance to the technician]

[2 points off for not mounting the strain gauges on anything]

4a

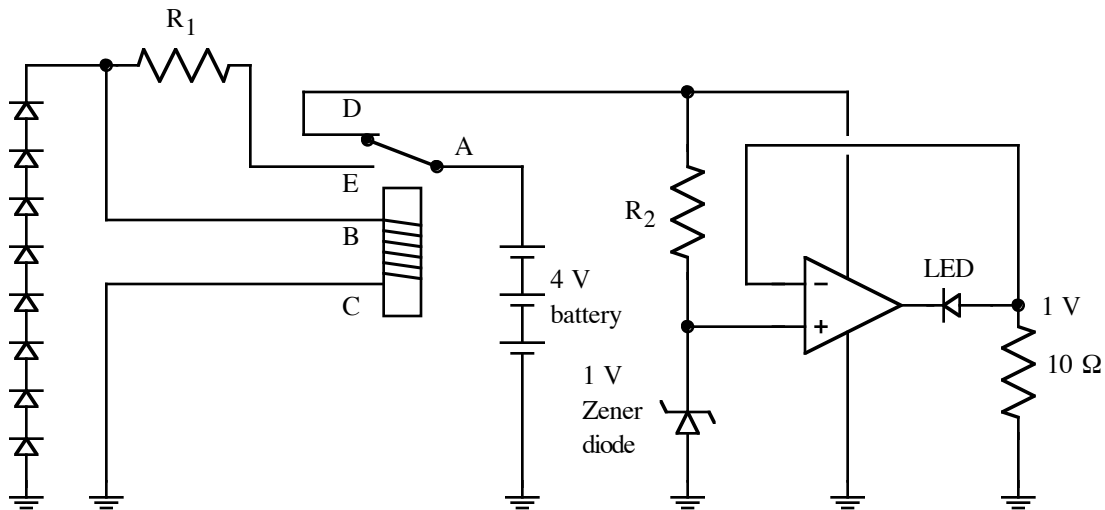

**4b** During daylight the eight photovoltaic cells produce a maximum of 4.8 V across the BC coil, which activates the relay to connect A to E and charge the battery.  $R_1$  is chosen so that during charging the voltage drop across it is only a few  $\times 0.1$  V.

**4c** At night the voltage across the BC coil is below 4 V because of the voltage drop across resistor  $R_1$ , A is connected to D, which connects the battery to the voltage-controlled current driver circuit. The op-amp is powered by the battery and drives 100 mA through the LED, as desired.

## Midterm #2 Solutions – EECS 145L Fall 2005

Alternative accepted designs:

- (1) Use a diode in place of  $R_1$  and a resistor  $R_3 = R_2/3$  in place of the Zener diode.
- (2) Use one photovoltaic panel and an op-amp to drive inputs B and C of the relay and connect the battery (A) to the seven photovoltaic panels during daylight. At night the battery (A) powers to the LED circuit (D).

[3 points off if the op-amp is not powered; in this problem op-amps have 5 leads, just like in the lab]

[3 points off if relay not used to automatically switch between day and night modes]

[2 points off if  $< 50$  mA passes through the LED at night]

[2 points off if photodiode panels are not connected in series to produce  $> 4$  V]

[3 points off if 4 V battery not used]

[2 points off for incorrect LED circuit]

[3 points off if LED is connected to 4V; the forward current will destroy the LED]

[2 points off if 4 V battery, LED, and Zener diode are connected in series;  
this does not control the current at the desired value of 100 mA]

### 145L midterm #2 grade distribution:

	maximum score = 100 average score = 74.0 (11.3 rms)
Problem 1            18.9 (2.2 rms) (20 max) 2            7.1 (2.8 rms) (10 max) 3            26.7 (6.6 rms) (40 max) 4            21.3 (3.8 rms) (30 max)	41-49            0            F 51-59            3            D 61-69            2            C 71-79            7            B 81-89            5            A 91-99            1            A+ 100              0 <div style="text-align: right;">GPA 2.9</div>