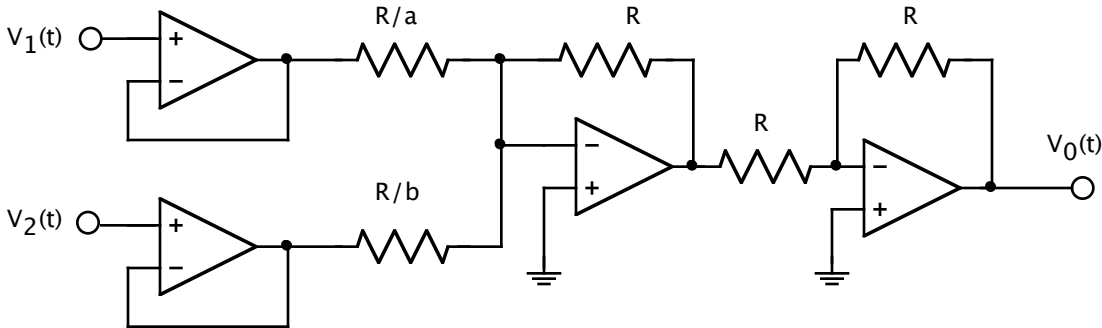


Midterm #1 Solutions – EECS 145L Fall 2007

1



The first stage provides high input impedance, the second stage is a summing amplifier that also inverts the sum, and the final stage re-inverts the signal. The minimal solution requires five resistors and four op-amps.

[20 points off for drawing an instrumentation amplifier, which is designed to take the difference between two signals, not add them]

[5 points off if inputs are not high impedance]

[5 points off if no final inversion after the summing amplifier]

[5 points off for not relating the coefficients a and b to the elements in your circuit]

[3 points off for labeling amplifier gains a and b but not explicitly relating them to the resistor values]

[2 points off for omitting the series resistor in the final inverting amplifier- this connects an op-amp output directly to a virtual ground.

[5 students out of 25 got a perfect score in this problem]

2

- Connect a harmonic generator to both inputs and measure both the input amplitude $V_1(f)$ and the output amplitude $V_0(f)$ for the ten frequencies.
- Compute the common mode gain $G_C(f) = V_0(f)/V_1(f)$
- Leave the generator connected to the + input and ground the – input.
- Measure both the input amplitude $V_1(f)$ and the output amplitude $V_0(f)$ for the ten frequencies

$$V_0(f) = G_C(f) V_1(f)/2 + G_{\pm}(f) V_1(f)$$

- Compute $G_{\pm}(f) = V_0(f)/V_1(f) - G_C(f)/2$

[4 points off for ignoring the common mode output when determining the differential gain.]

[3 points off for using $V_2(t) = -V_1(t)$ without providing a circuit for generating these signals]

[15 students out of 25 got a perfect score in this problem]

3

Frequency ratio $f_2/f_1 = 60 \text{ kHz}/20 \text{ kHz} = 3$

This means that the gain must drop from $G_1 = 0.999$ to $G_2 = 0.0001$ in a factor of 3 in frequency

For $n = 10$ the frequency ratio for G_2 and $G_1 = 2.512/0.733 = 3.43$ (too large a frequency ratio)

For $n = 12$, the frequency ratio = $2.154/0.772 = 2.79$ (okay)

$60 \text{ kHz}/2.154 < f_c < 20 \text{ kHz}/0.772$

The answer is $n = 12$ and $27.9 \text{ kHz} < f_c < 25.9 \text{ kHz}$

[14 students out of 25 got a perfect score in this problem]

Midterm #1 Solutions – EECS 145L Fall 2007

4a The electromagnetic isolation amplifier

- 1) uses the input signal to modulate a higher-frequency carrier wave in the input stage
 - 2) couples the modulated carrier signal to the output stage by electromagnetic induction through the air (this blocks dangerous low frequency voltages)
 - 3) demodulates and amplifies the modulated carrier signal in the output stage to recover an isolated, amplified version of the input signal
- [6 points off for describing the isolation transformer without the carrier, or differential amplification to remove electromagnetic interference, or analog filtering]
 [7 students out of 25 got a perfect score in this problem]

4b The digital angle encoder

- 1) Has digital codes arranged in circular rings on a disk
 - 2) Has sensors to read the digital codes
 - 3) When the disk is rotated, the sensors pick up digital signals that are uniquely related to the angle
- [4 points off if the sensors are not described]
 [8 students out of 25 got a perfect score in this problem]

4c The stepping motor

- 1) Has a permanent magnet with alternating N and S poles that rotates within a circular array of electromagnets
 - 2) Current in the electromagnets causes the permanent magnet to hold its position
 - 3) Changing the currents in the electromagnets causes the permanent magnet to rotate
- [18 students out of 25 got a perfect score in this problem]

5 $R_T = R_1 + R_2$, where R_1 and R_2 are independently random 1 K Ω resistors

$$\sigma_T^2 = (\partial R_T / \partial R_1)^2 \sigma_1^2 + (\partial R_T / \partial R_2)^2 \sigma_2^2 = \sigma_1^2 + \sigma_2^2$$

Since $\sigma_1 = \sigma_2$, we have $\sigma_T = \sqrt{2}\sigma_1$

So the average resistance of the “2 k Ω ” resistors is 2100 Ω and the standard deviation is 141 Ω
 [15 students out of 25 got a perfect score in this problem]

145L midterm #1 grade distribution:

	maximum score = 100 average score = 75.8 (13.2 rms)
Problem	
1	22.4 (5.8 rms) (30 max) 50-59 3 C
2	8.3 (2.3 rms) (10 max) 60-69 7 C+
3	17.4 (3.7 rms) (20 max) 70-79 4 B
4a	5.8 (2.7 rms) (10 max) 80-89 7 B+
4b	5.8 (3.4 rms) (10 max) 90-99 4 A
4c	8.1 (3.4 rms) (10 max) 100 0
5	8.0 (2.5 rms) (10 max) GPA 2.9