

Professor Oldham

Fall 2000

**EECS 40 — MIDTERM #1**

2 October 2000

Name: \_\_\_\_\_  
Last, First

Student ID: \_\_\_\_\_

Signature: \_\_\_\_\_

TA:  Ben  
 Warren  
 Naratip

**Guidelines:**

1. Closed book and notes except 1 page of formulas.
2. You may use a calculator.
3. Do not unstaple the exam.
4. Show *all your work and reasoning on the exam* in order to receive full or partial credit.
5. This exam contains 8 problems and corresponding worksheets plus the cover page.


Problem	Points Possible	Your Score
1	15	
2	15	
3	12	
4	10	
5	15	
6	10	
7	11	
8	12	
<b>Total</b>	<b>100</b>	

$f = 10^{-15}$ $p = 10^{-12}$ $n = 10^{-9}$ $\mu = 10^{-6}$ $m = 10^{-3}$ $K = 10^3$ $M = 10^6$
---




**Prob. 1 Worksheet**

**Problem 2 (15 points)**

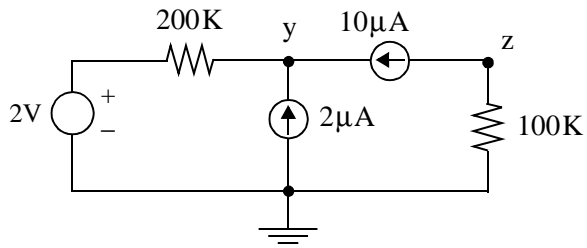

(a) Find  $V_y$ .

$V_y =$

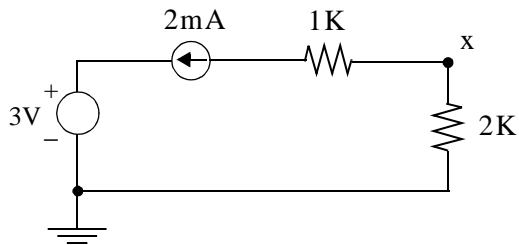

(b) Find  $V_x$ .

$V_x =$

(c) Find power delivered by the voltage source.


$P_3 =$

**Prob. 2 Worksheet**

**Problem 3 (12 points)**

For the circuit below:

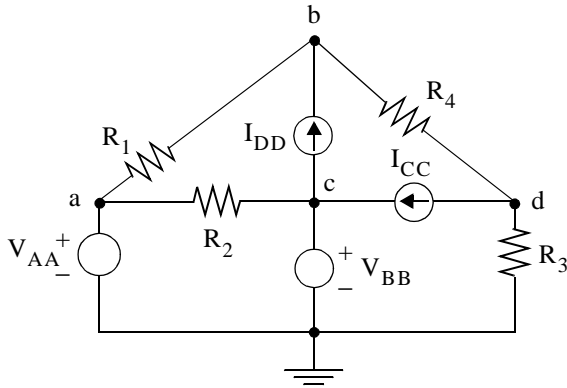- (a) Identify known and unknown node voltages, and
- (b) Write sufficient nodal equations to solve for the unknown node voltages (do not solve).



(a.1) known node voltages:

\_\_\_\_\_

(a.2) unknown node voltages:

\_\_\_\_\_


Nodal Equations:

_____
_____
_____
_____

**Prob. 3 Worksheet**

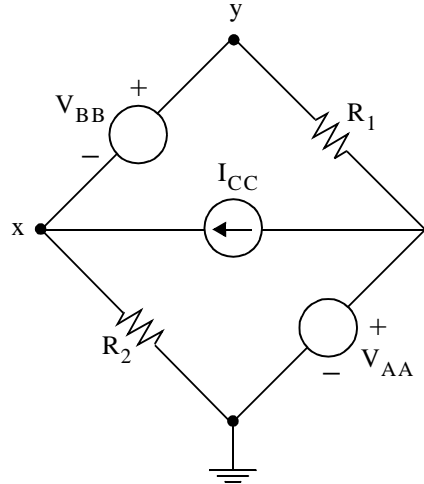**Problem 4 (10 points)**

For the circuit below, using nodal analysis write sufficient equations to find  $V_x$  and  $V_y$ . Do not solve.




Equations:

_____
_____
_____



**Prob. 4 Worksheet**

**Problem 5 (15 points)**

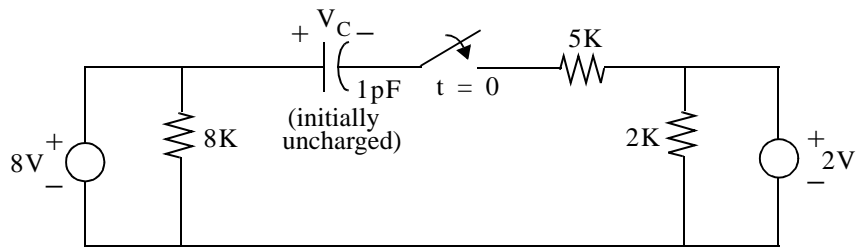


For the circuit above, the capacitor is initially uncharged. The switch closes at  $t = 0$ .

(a) Find  $V_C$  for  $t = 0^+$  and  $t \rightarrow \infty$ .

$$V_C(t = 0^+) = \underline{\hspace{2cm}}$$

$$V_C(t \rightarrow \infty) = \underline{\hspace{2cm}}$$

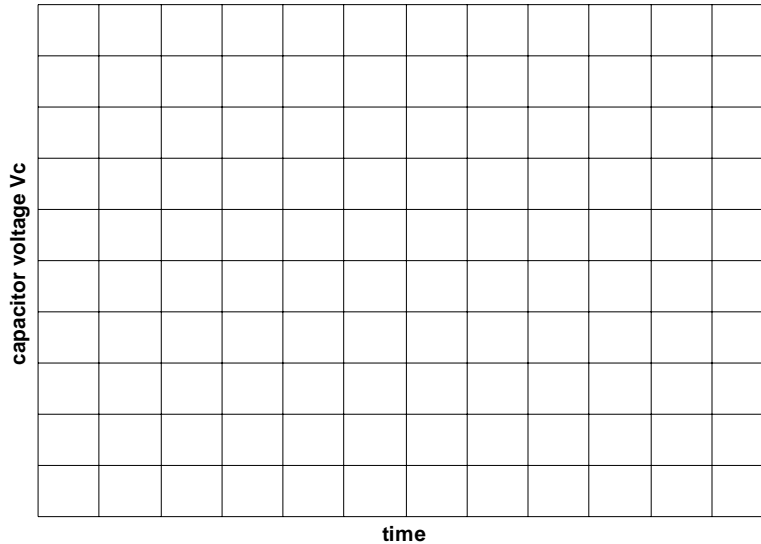(b) Sketch (very neatly and accurately!)  $V_C$  vs.  $t$  on the graph below. You **must** label the axes.




(c) Write an equation for  $V_C(t)$ .

$$V_C(t) =$$

**Prob. 5 Worksheet**

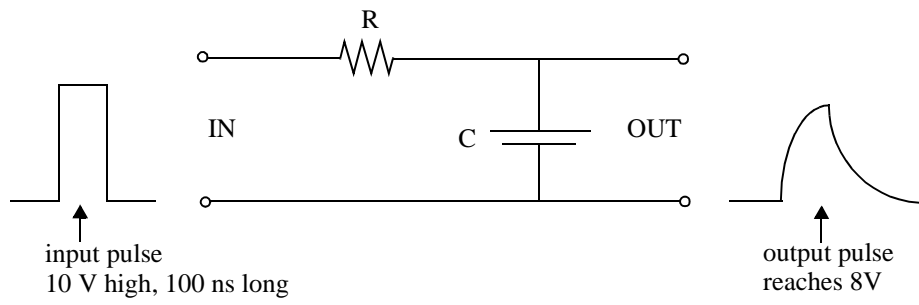**Problem 6 (10 points)**

In the lab on RC circuits, you measure the pulse response of the circuit below.





You know  $R$  is  $2\text{K}\Omega$ . What is the value of  $C$ ?

$C = \underline{\hspace{2cm}}$
--------------------------------

**Prob. 6 Worksheet**

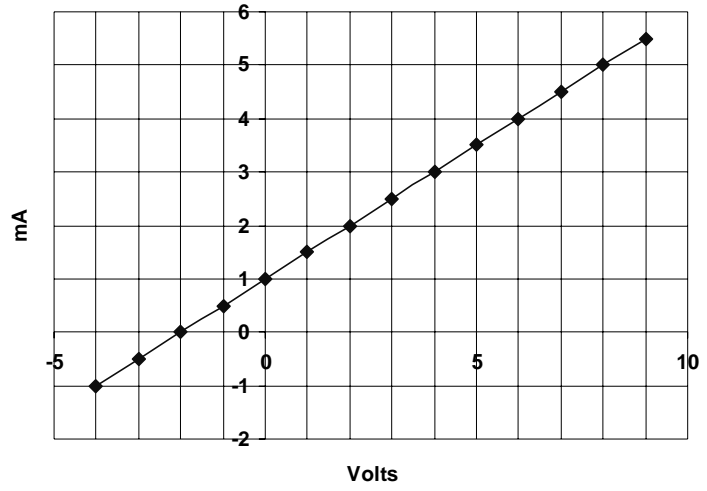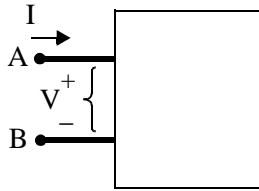**Problem 7 (11 points)**

You measure the I-V graph of a circuit in a “black box” in the lab.




What is a possible circuit that is in the box? Draw here ↓.




**Prob. 7 Worksheet**

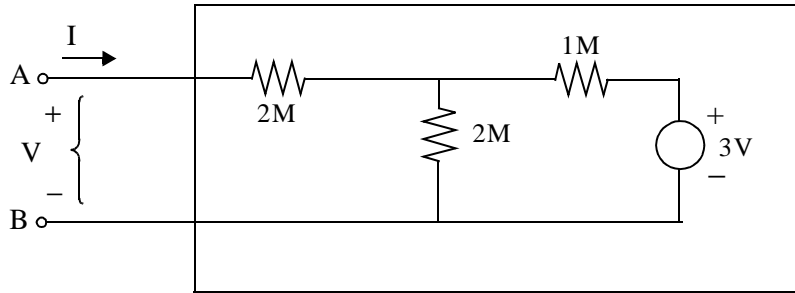**Problem 8 (12 points)**

In this experiment you “peek,” i.e., you open the box before testing it. You see the following circuit:



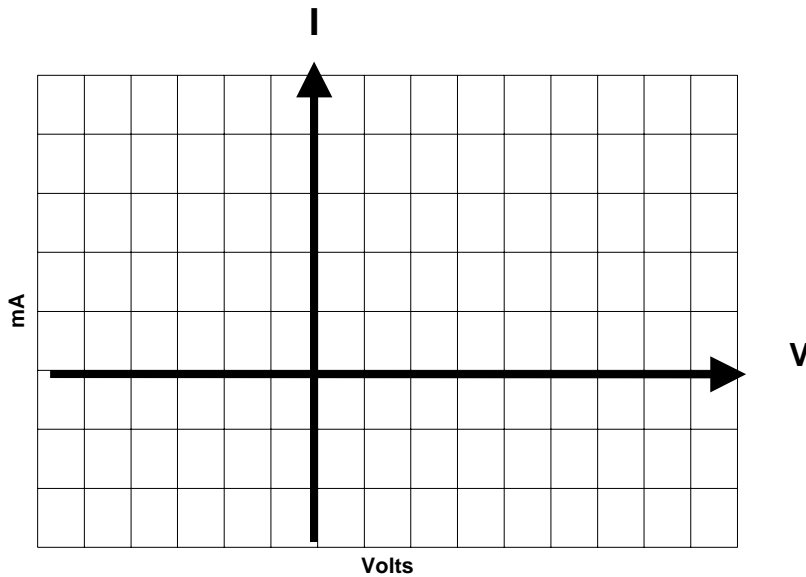What will be the I-V graph you will measure for this circuit? (You must label axes for credit.)





**Prob. 8 Worksheet**