


Electrical Engineering 40/40I/41I

Midterm 1 - Fall 1995


Professors S. Schwarz (40) and R.M. White (40I/41I)

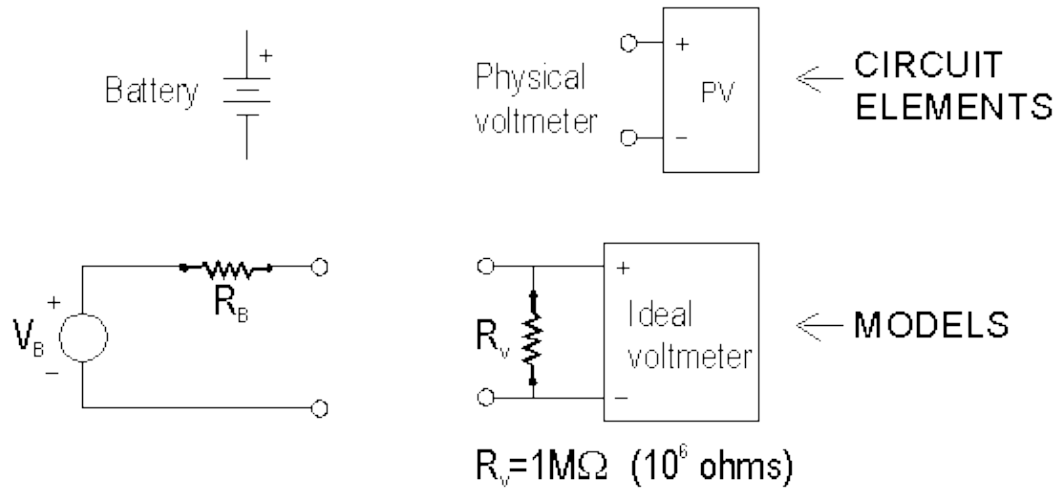Problem 1: [25%]

Circuit models for a battery and a physical voltmeter are shown below:



A circuit is constructed as shown below:

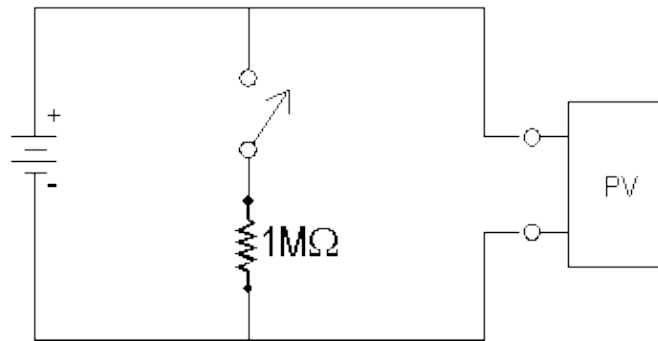


When the switch is open (not connected) the physical voltmeter reads 8 volts. When the switch is closed (connected) the physical voltmeter reads 6 volts. Find R_B and V_B .

$R_B =$ _____ ohms

$V_B =$ _____ volts

Problem 2: [25%]

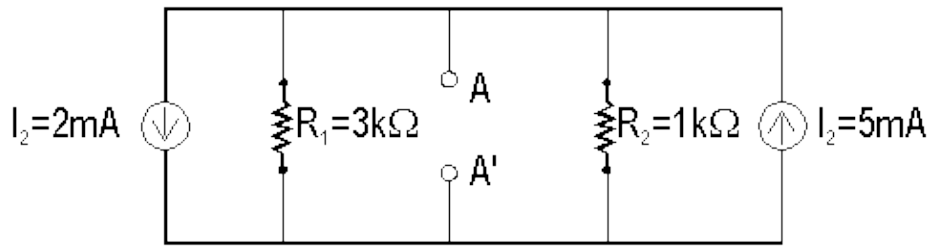


A two-terminal subcircuit is shown with terminals A and A'. Find its Thévenin equivalent, making your method clear. (Label the terminals AA' in your equivalent circuit)

$R_{TH} =$ _____ ohms
$V_{TH} =$ _____ volts

Problem 3: [25%]

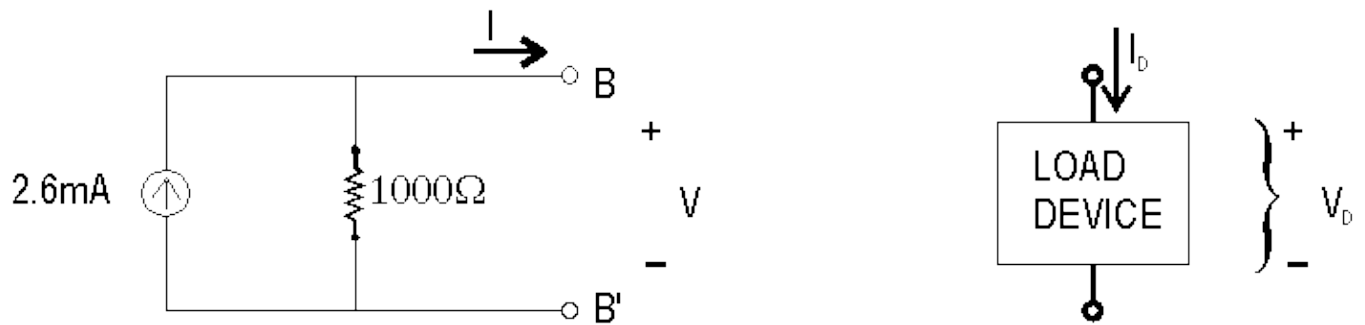
(a) Plot the I-V characteristic of the Norton equivalent circuit having terminals B-B' on the axes below:



(b) The I-V characteristic of a load device is also plotted on these axes. If the load device is connected to terminals B-B', what current, I_D , flows and what voltage, V_D , appears across the load device?


$I_D =$ _____ mA
$V_D =$ _____ V

(c) Under the conditions of part (b), find the power delivered to the load device.

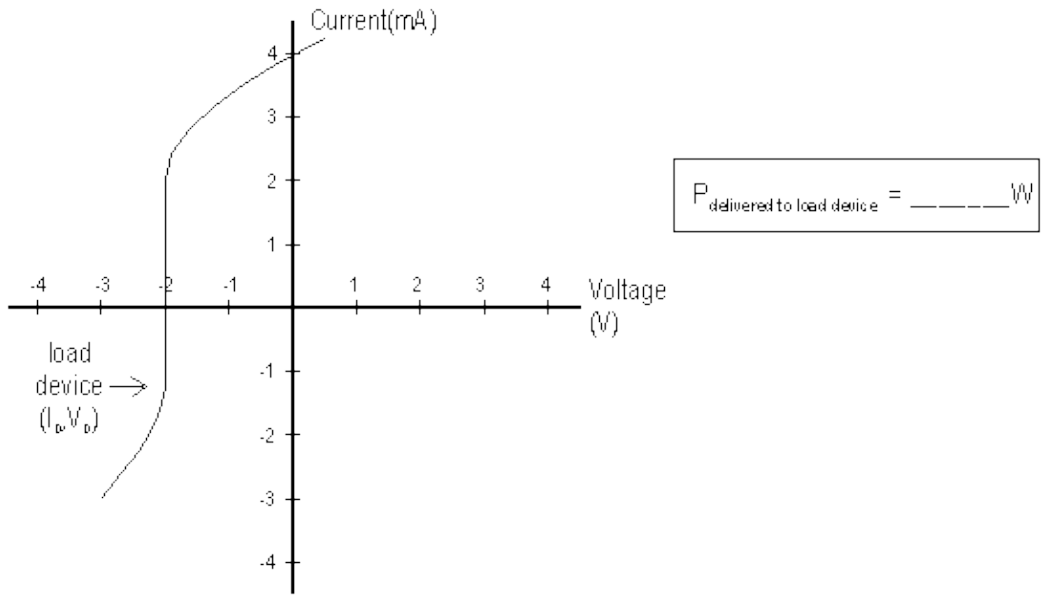

Page 3

Problem 4: [25%]

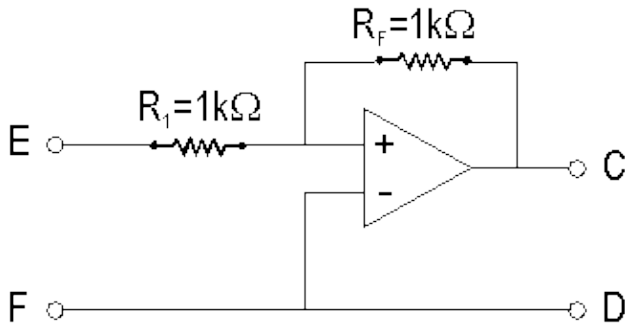

In the above circuit the op-amp has an abnormally low voltage amplification; in fact, $A=5$. Its input resistance $R_i=1M\Omega$ and $R_o=0$. Output terminals C, D, are open-circuited.

(a) Re-draw the circuit with the full op-amp equivalent circuit inserted. (Do NOT use the ideal op-amp technique.)

(b) Find the input resistance looking into terminals E, F. Use the full op-amp model. (Do NOT use the ideal op-amp technique.) Output terminals C, D are open-circuited.

Page 4



Eta Kappa Nu (November 1995)