

EE 40 MIDTERM I SOLUTIONS : SPRING 2001

① a) $v_c(t=0) = 0V = v_c(t=0^+) \Rightarrow i(t=0^+) = \frac{10V - 0V}{5\Omega + 5\Omega + 10\Omega} = 0.5A$


b) $v_c(t) = A + Be^{-t/\tau}$ $\tau = RC = [20\Omega][1\mu F] = 20\text{ps}$
 $t=0^+ \rightarrow v_c(0^+) = A+B=0V$ } $A=10V, B=-10V.$
 $t \rightarrow \infty \rightarrow v_c(\infty) = A = 10V$

$v_c(t) = 10V [1 - e^{-t/20\text{ps}}]$, $t \in (0, 50\text{ps}) \Rightarrow v_c(50\text{ps}) = 10V [1 - e^{-50/20}] = 9.2V$

$\therefore q = CV_c = 1\mu F \cdot 9.2V = 9.2\mu C$

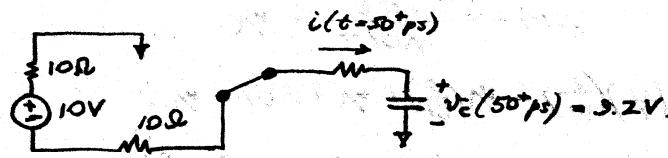c) At $t = 50^+$ ps, current is


$$i(t=50^+\text{ps}) = \frac{-10 - 9.2}{30\Omega} = -0.64A$$




d)

Solution for $v_c(t)$ [$t > 50\text{ps}$] is $v_c(t') = A' + B'e^{-t'/\tau'}$ $\{\tau' = R'C = 80\Omega \cdot 1\mu F = 80\text{ps}$
 $t' = t - 50\text{ps}$
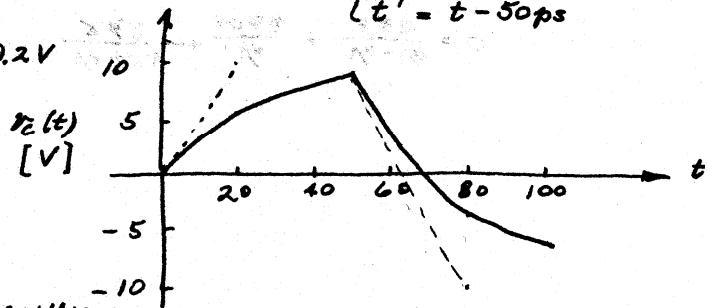
$$\begin{cases} v_c(t=50\text{ps}) = 9.2V = A' + B' \\ v_c(t \rightarrow \infty) = -10V = A' \end{cases} \Rightarrow B' = +19.2V$$



② a)

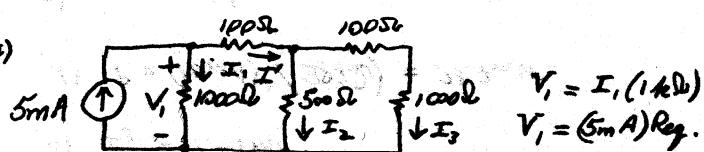

$$R_{eq} = \left\{ \left[\frac{(100+1000)}{1100} \parallel 500 \right] + 100 \right\} \parallel \left(\frac{1000}{1000} \parallel 100 \right) = 144 \parallel 100 = 307\Omega \Rightarrow I_1 = \frac{V_1}{1k\Omega} = \frac{(5mA)(R_{eq})}{1k\Omega} = 1.54mA.$$

b) Find I_2 using a current divider:


$$I' = 5mA - 1.54mA = 3.46mA.$$

$$I_2 = I' \cdot \frac{1100\Omega}{500 + 1100} = 2.38mA.$$

c) $I_3 = I' - I_2 = 3.46 - 2.38 = 1.08mA.$

d) $P = I^2 R_{eq} = (5mA)^2 / 307\Omega = 7.7mW$

③ a)

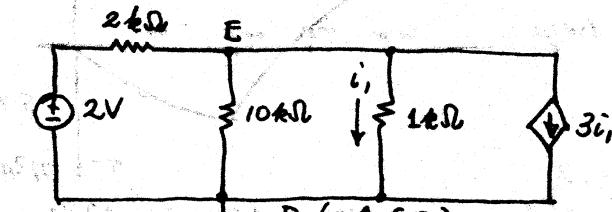

1) KCL at node E: $i_1/10 + i_2 + 3i_1 = i'$

$$\frac{V_E - 2V}{2k\Omega} + \frac{V_E}{10k\Omega} + \frac{V_E}{1k\Omega} + 3 \left[\frac{V_E}{1k\Omega} \right] =$$

$$i_1 \left[\frac{1}{2} + \frac{1}{5} + 1 + 3 \right] = \frac{2V}{2k\Omega} = 5mA$$

$$i_1 = \frac{1mA}{4.6} = 217\mu A.$$


2) KCL at node A: $\frac{V_A + 2V}{2k\Omega} + \frac{V_A}{10k\Omega} + \frac{V_A - V_B}{5k\Omega} = 1$
KCL at node B: $\frac{V_B - V_A}{5k\Omega} + \frac{V_B}{1k\Omega} - 3 \left(\frac{-V_B}{1k\Omega} \right) = -i_1$

$$\therefore V_B - V_A + 5V_A + 15V_B = 0.$$

$$V_B = \frac{V_A}{2} \Rightarrow 5V_A + 10V + V_A + 2V = 1$$

$$V_A = \frac{-10V}{2} = -5V$$

c)

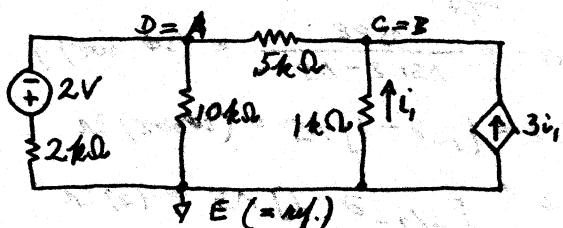

Variant Exam

R. Schaefer
2/28/10


$$\textcircled{1} \text{ a) } i(0t) = \frac{5V}{10\Omega} = 0.125A$$

$$\text{b) } v_c(t) = 5V [1 - e^{-t/\tau}] ; \tau = 10\Omega \cdot 5\mu F = 200\text{ps.}$$

$$v_c(200\text{ps}) = 5V [1 - e^{-1}] = 3.15V \Rightarrow q = (5\mu F)(3.15V) = 15.75\mu C$$

$$\text{c) } i(200+\text{ps}) = \frac{-5V - 3.15V}{30\Omega} = -0.27A.$$
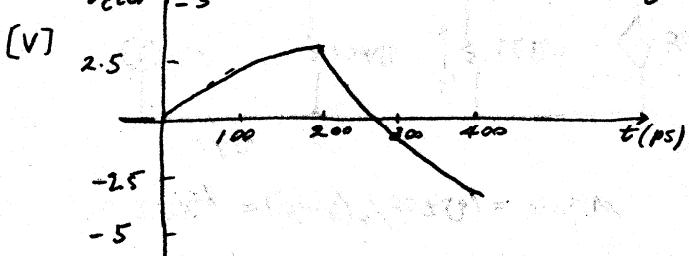
$$\text{d) } v_c(t') = -5V + 3.15V e^{-t'/\tau'} ; \begin{cases} \tau' = 30\Omega \cdot 5\mu F = 150\text{ps.} \\ t' = t - 200\text{ps.} \end{cases}$$



$$\textcircled{2} \text{ a) } I_1 = 10mA \left[\frac{R_{eq}}{500\Omega} \right]; R_{eq} = ((1000 \parallel 750) + 250) \parallel 500 = 287\Omega$$


$$= 5.76mA$$

$$\text{b) } I_2 = (10 - 5.76) \left[\frac{750}{1750} \right] = 1.82mA$$

$$\text{c) } I_3 = 2.42mA$$

$$\text{d) } P = (10mA)^2 (287\Omega) = 28.7mW.$$

\textcircled{3} a) same, b) same

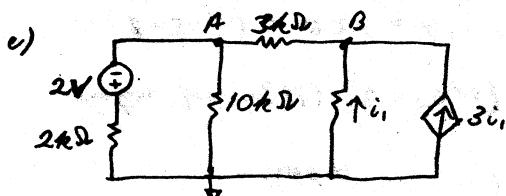

$$\text{d) } \frac{V_A + 2V}{2k\Omega} + \frac{V_A}{10k\Omega} + \frac{V_A - V_B}{3k\Omega} = 0.$$

$$\frac{V_B - V_A}{3k\Omega} + \frac{V_B}{1k\Omega} + \frac{3V_B}{1k\Omega} = 0.$$

$$V_B - V_A + 3V_B + 9V_B = 0 \Rightarrow V_B = \frac{V_A}{13}$$

$$5V_A + 10V + V_A + \left(\frac{10}{3}\right)V_A - \left(\frac{10}{3}\right)\left(\frac{1}{13}\right)V_A = 0.$$

$$V_A = \frac{-10V}{9.07} = -1.1V.$$