

EECS40

Spring 2004  
Professor Sanders**Midterm Exam # 2**  
**April 15, 2004**  
**Time Allowed: 80 minutes**Name: \_\_\_\_\_, \_\_\_\_\_  
Last First

Student ID #: \_\_\_\_\_, Signature: \_\_\_\_\_

Discussion Section: \_\_\_\_\_

This is a closed-book exam, except for use of two 8.5 x 11 inch sheet of your notes. Show all your work to receive full or partial credit. Write your answers clearly in the spaces provided.

Problem #:	Points:
1	/10
2	/20
3	/20
Total	/50

1.

a) (5 points)

A silicon sample is uniformly doped with Boron to a concentration of  $10^{16}$  atoms /  $cm^3$ .

Determine the resistivity of the sample at room temperature.

Use electron mobility =  $\mu_n = 1000$   $cm^2/v\text{-s}$ , hole mobility =  $\mu_p = 400$   $cm^2/v\text{-s}$ ,

$Q = 1.6 \cdot 10^{-19}$  C and  $n_i = 10^{10}$  at room temperature.


b) (5 points)

The same sample is then to be counter doped to a depth of  $5 \mu m$  with Arsenic atoms

to create a resistor technology with resistance of  $100 \Omega/\square$ .

Determine the required Arsenic doping density.


2.

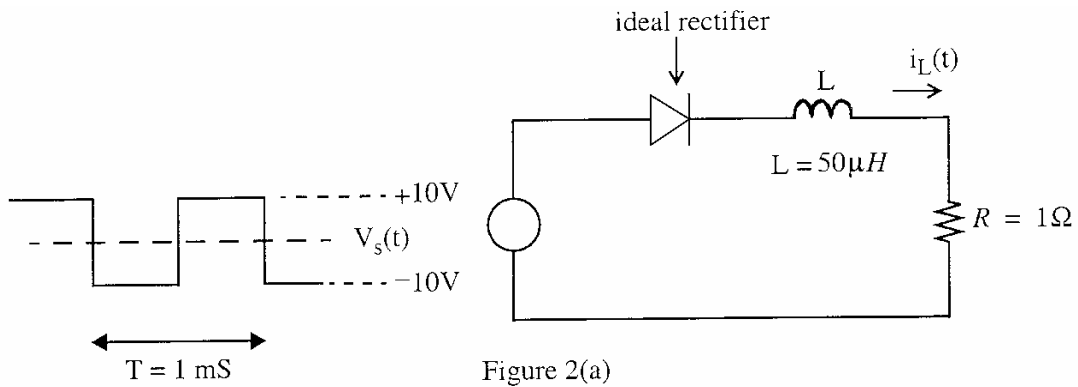

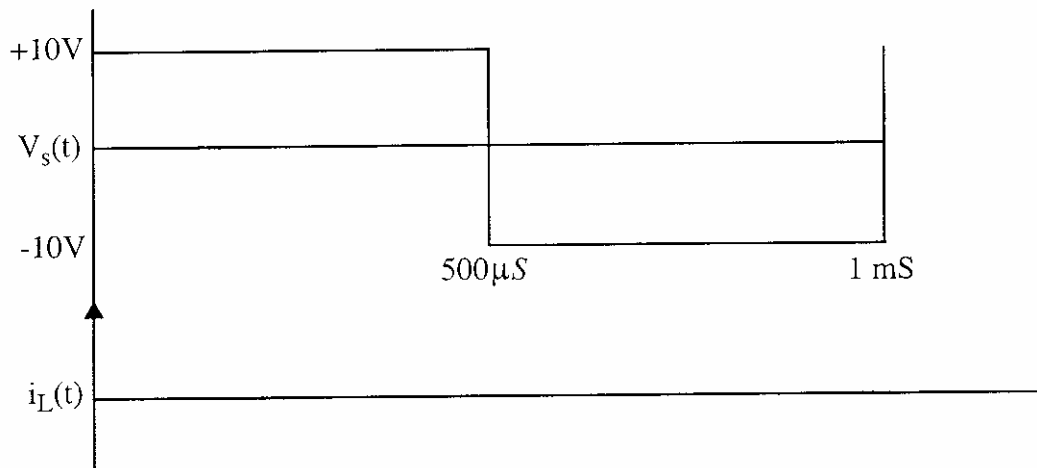a) (10 points)

The diode in Figure 2(a) is ideal. The waveform  $V_s(t)$  is a balanced square wave with amplitude of 10 V and period 1 mS. Take  $L = 50 \mu\text{H}$  and  $R = 1 \Omega$ .

The circuit operates in a periodic steady state. Sketch and carefully dimension one period of the  $i_L(t)$  waveform on the axes below. Make reasonable approximations.



b) (10 points)

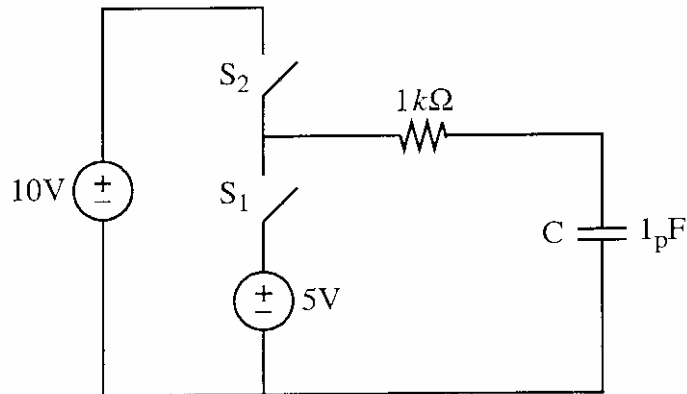


Figure 2(b)

In the circuit of Figure 2(b), switch  $S_1$  is initially closed and switch  $S_2$  is initially open and the circuit is in equilibrium. Switch  $S_1$  is then opened and switch  $S_2$  is closed for a sufficiently long time so that the circuit can be considered to be in equilibrium. How much energy is dissipated in the  $1\text{ k}\Omega$  resistor during the transient?

**Hint:** Think in terms of net charge and energy flow. Detailed transient analysis is **NOT** needed.

3.

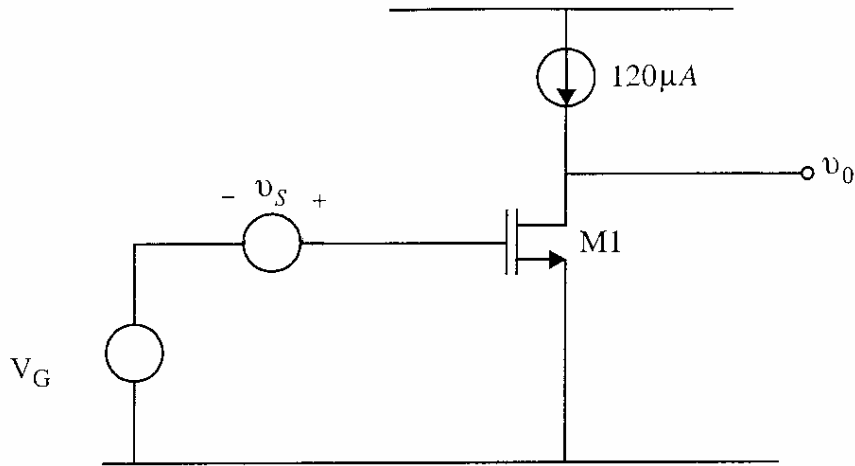


Figure 3

$$\lambda = 0.1 \text{V}^{-1}$$

$$V_T = 0.5 \text{V}$$

$$k' = 100 \mu\text{A}/\text{V}^2$$

$$\frac{W}{L} = 2$$

Mosfet M1 in Figure 3 is modeled by  $i_D = \frac{1}{2} k' \frac{W}{L} (v_{GS} - V_T)^2 (1 + \lambda v_{DS})$  in saturation with parameters listed in Figure 3.

a) (5 points)

Determine the required bias voltage  $V_G$  so that M1 is biased in saturation with  $V_{DS} = 2 \text{V}$ . Take  $v_S = 0$

b) (10 points)

Draw the small signal model for this circuit. Compute the parameters of this small signal model.

c) (5 points)

Determine the small signal gain  $A_v = \frac{v_0}{v_s}$ .