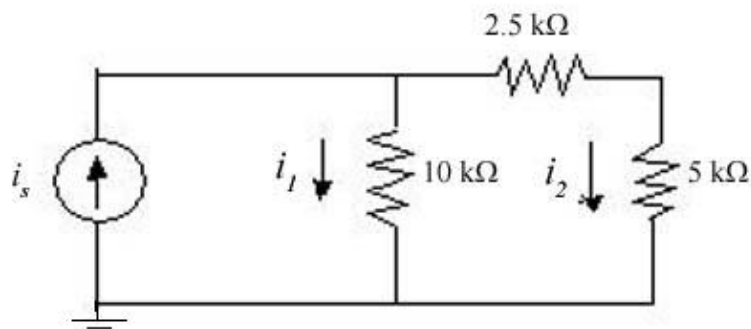


UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering and Computer Sciences
A.M. Flynn, R.T. Howe and R.M. White


Midterm 1: EECS 40/40I/41I
February 22, 1996

1. Closed book exam - no books, programmed calculators, etc. One 8.5" x 11" sheet of notes allowed.
2. Do your calculations on this exam. **MAKE YOUR METHODS CLEAR TO THE GRADER.**
3. Print and sign your name on this page and CHECK YOUR SECTION in the box above.
4. There are 4 problems. Make sure you have them all.
5. All exams are not identical.


1. Circuit analysis [25 points]



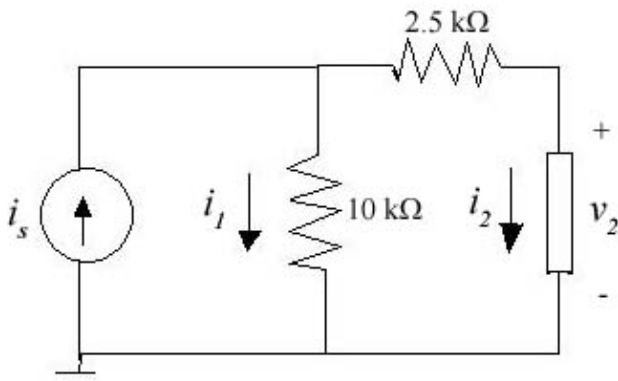
- a) [7 pts] What is the numerical value of the current i_2 in the above circuit, for the case when $i_s = 1.5$ mA?







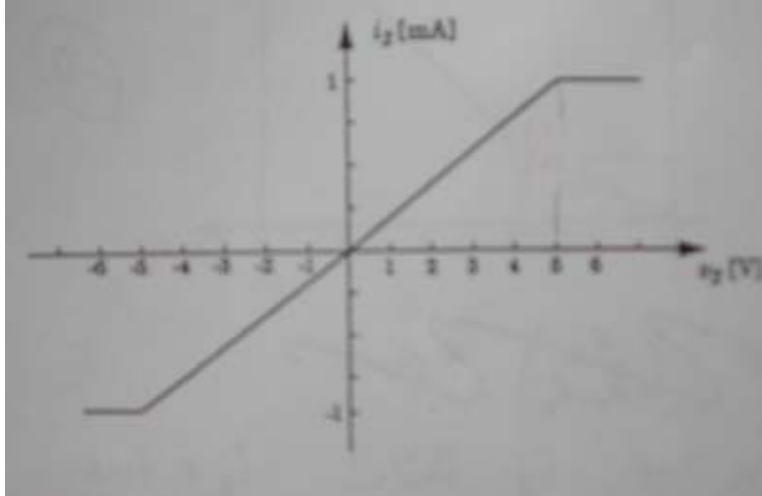
b) [8 pts] The 5 kOhms resistor is replaced with a non-linear circuit element having i_2 vs. v_2 characteristics given in the graph below. What is the numerical value of the current i_2 for the case when $i_s = 1.5$ mA? *Hint:* consider what this element is equivalent to over its linear range.




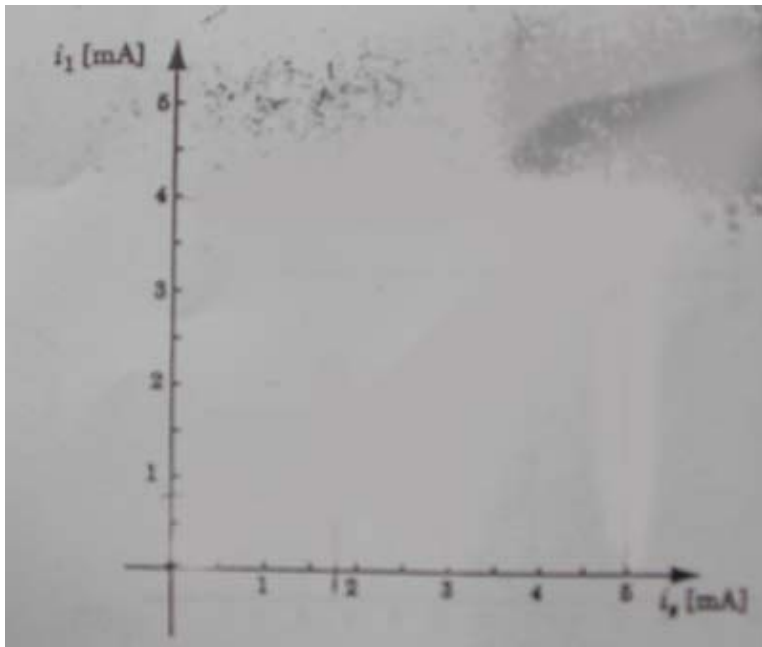c) [10 pts] Plot the current i_1 , the current through the 10 kOhms resistor, as a function of the source current i_s for $i_s = 0$ to 5 mA on the graph provided below.




2. Power [25 points]

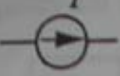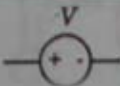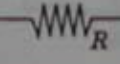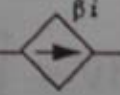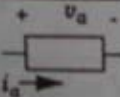Circuit Element	Power delivered may be positive	Power delivered may be negative	Power delivered may be zero	Brief justification
				
				
				
				
 see i_a vs. v_a below				

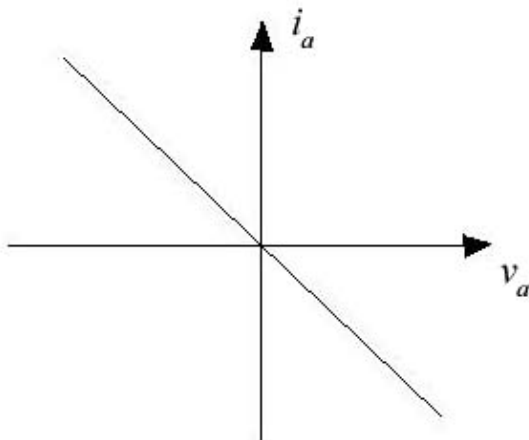

For each of the five circuit elements, check the correct statements regarding the sign and value of the power delivered to the element ($P = iv$), which is consistent with the convention that positive power in an element corresponds to dissipation and a negative power corresponds to generation. If you check the "may be zero" box, give a brief justification for your answer. [5 pts per element]

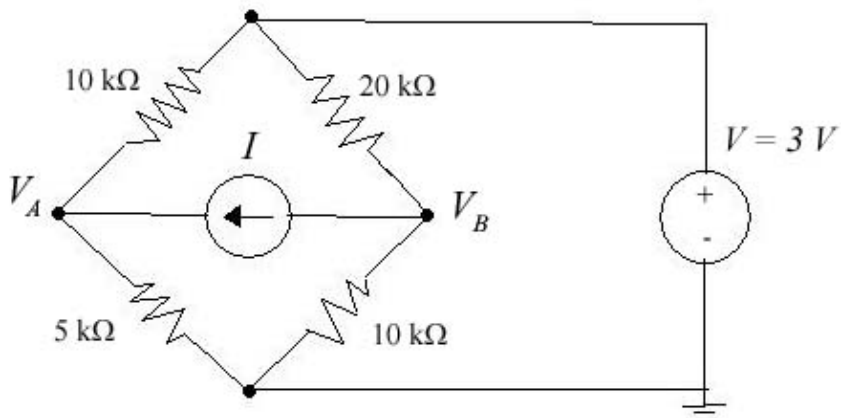3. Bridge circuit with multiple sources [25 points]




a) [7 pts] For $I = 0$ in the above circuit, find the numerical value of the voltage V_B (with respect to ground)

b) [8 pts] For $I = 0$, what is the power delivered to the circuit by the 3 V voltage source?

4. [25 points]

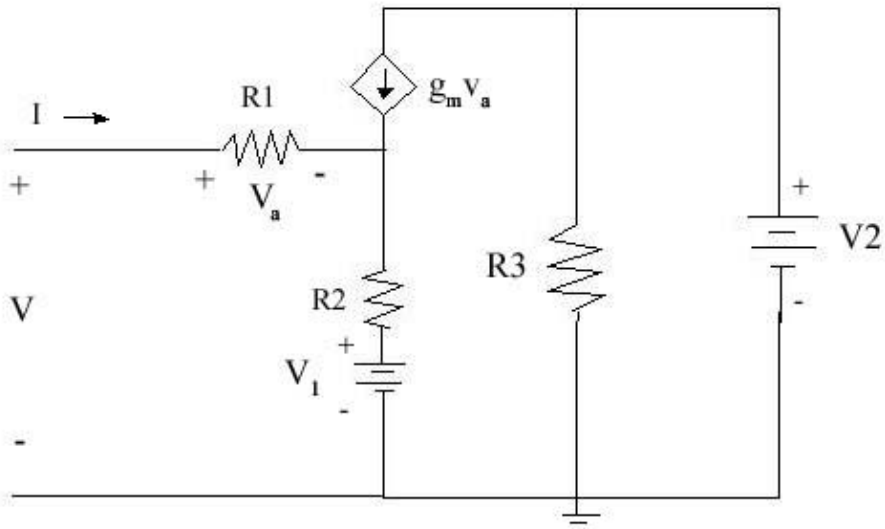a) [15 pts] Find the Thevenin equivalent circuit, of the circuit below, seen looking into the terminals at left.



$V_{th} =$

$R_T =$

b) [10 pts] What is V_o as a function of V_1 and V_2 ? Use ideal op-amp assumptions. Find an expression for V_o , symbolically and then plug in values for the resistors:

- $R_1 = 5 \text{ KOhms}$
- $R_2 = 10 \text{ KOhms}$
- $R_3 = 60 \text{ KOhms}$
- $R_4 = 60 \text{ KOhms}$

$V_o =$

$V_o =$

c) [10 pts] For $I = 100 \text{ uA}$, find the numerical value of the voltage V_B . *Hints:* superposition is probably useful; your answer to part (a) may be helpful.